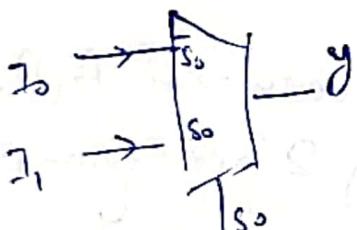


Multiplexer (Mux)

- ↳ Many to one converter.
- ↳ Universal logic
- ↳ And-or logic.

Design a 2x1 MUX.

Step 1.



Step 2


$S_0 \rightarrow 0$	$y$
$I_0$	
$I_1$	

Step 3


$$y = \overline{S_0} I_0 + S_0 I_1$$

Step 4: already minimized

Step 5.

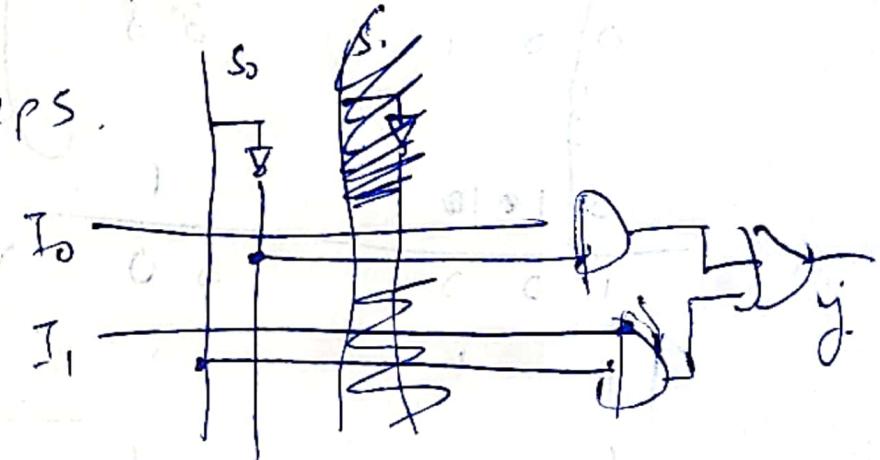


4x1 MUX

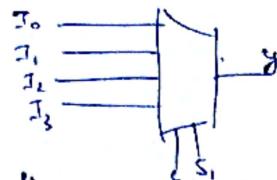

	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	I <sub>0</sub>
0	1		I <sub>1</sub>
1	0		I <sub>2</sub>
1	1		I <sub>3</sub>
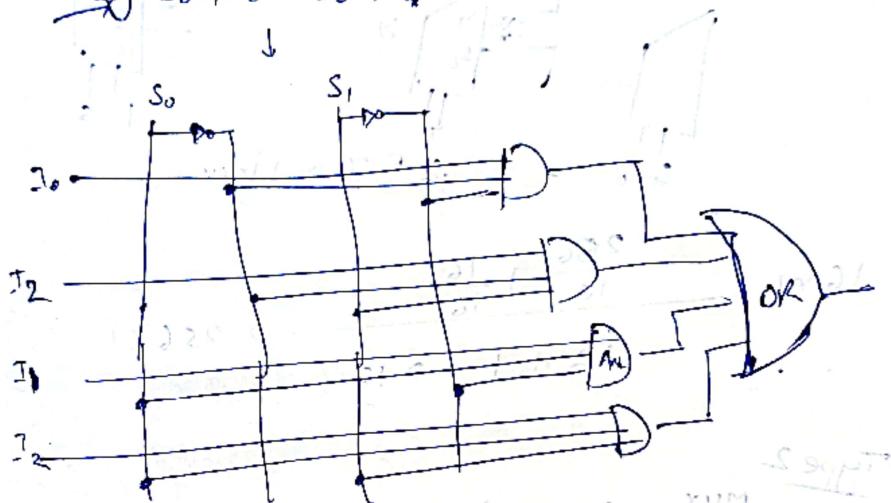
$$Y = \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + \bar{S}_0 S_1 I_2 + S_0 S_1 I_3$$



Probable pattern of


Question -

Type 1  
Design 4x1 MUX using 2x1 MUX.


$$\begin{aligned} 2 \times 1 & \xrightarrow{\frac{4}{2} + \frac{2}{2}} \\ = 2+1 & = 3 \end{aligned}$$

Total 3 2x1 MUX required.
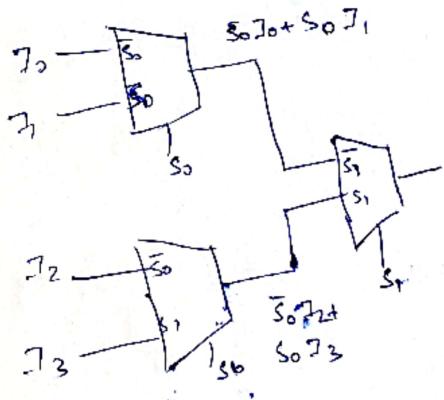
$$\begin{array}{c} 4 \times 1 \xrightarrow{\frac{4}{2} + \frac{2}{2} \rightarrow 2} \\ \text{Ans} \end{array} \quad \begin{array}{l} \text{undiluted} \\ \text{unless 1 or 0.} \end{array}$$



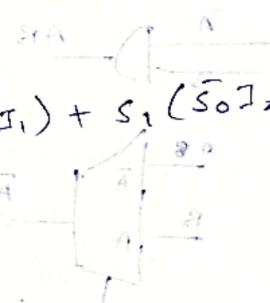
$$\bar{S}_1 (\bar{S}_0 I_0 + S_0 I_1) + S_1 (\bar{S}_0 I_2 + S_0 I_3)$$




$$\begin{array}{c} 2 \times 1 \xrightarrow{\frac{8}{2} + \frac{4}{2} + \frac{2}{2}} 8 \times 1 \\ 4+2+1=7 \\ S_0 \ S_1 \ S_2 \end{array} \quad \begin{array}{c} 2 \times 1 \rightarrow 2^n \times 1 \\ 2^n-1 \text{ MUX req.} \end{array}$$
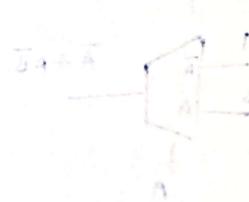
$$\begin{array}{c} 4 \times 1 \xrightarrow{\frac{16}{4} = \frac{4}{4}} 16 \times 1 \\ 4+1=5 \end{array}$$


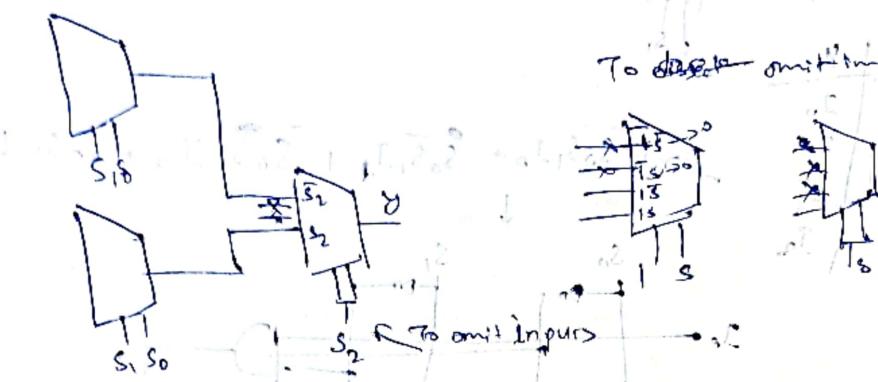
$$4 \times 1 \text{ Mux} \xrightarrow{\frac{8}{4} + \frac{2}{4}} 8 \times 1$$



$$\frac{256}{16} + \frac{16}{16} \rightarrow 256 \times 1$$


$16 + 1 \rightarrow 12$

Type 2  
MUX as a Universal logic


1. Not gate




2. And gate


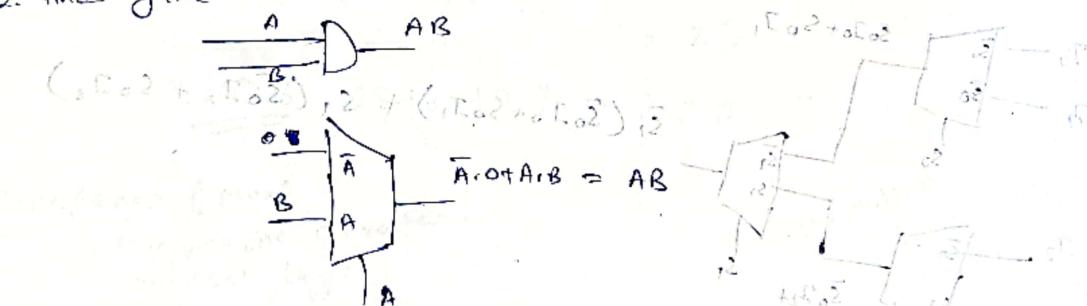


3. OR gate

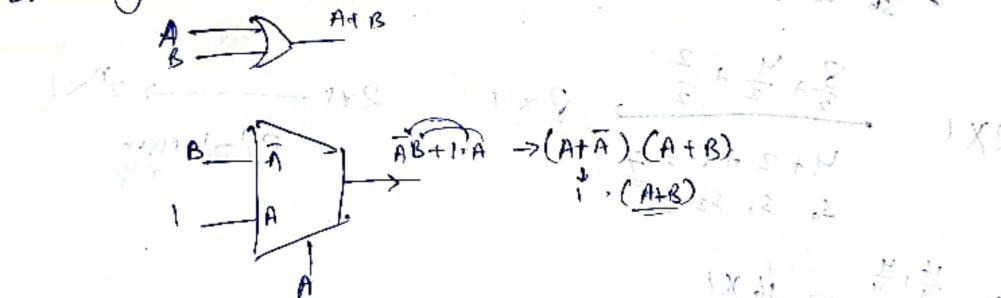


4. NAND gate

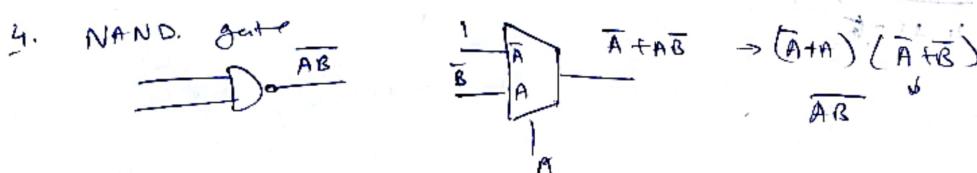

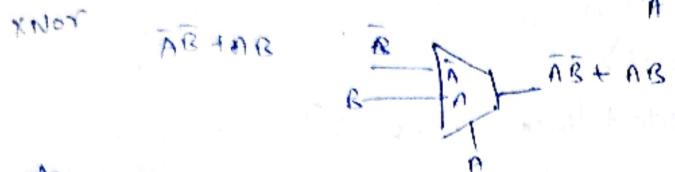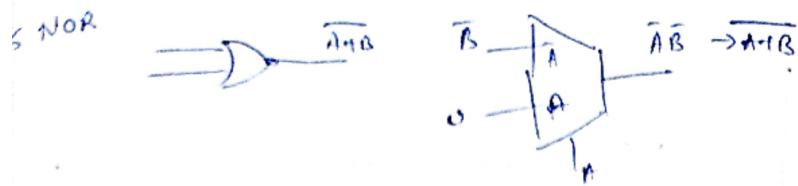


\* NOT, AND, OR  $\rightarrow$  1 2x1 MUX req.

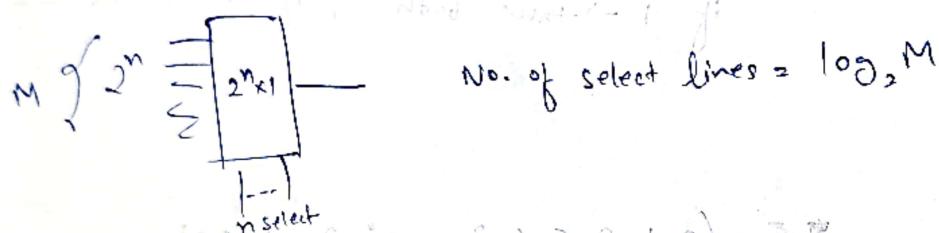NAND, NOR, XOR, X-NOR  $\rightarrow$  2 2x1 MUX req.  
Because of making Bar  $\bar{B}$




### TYPE 3 Minimization.

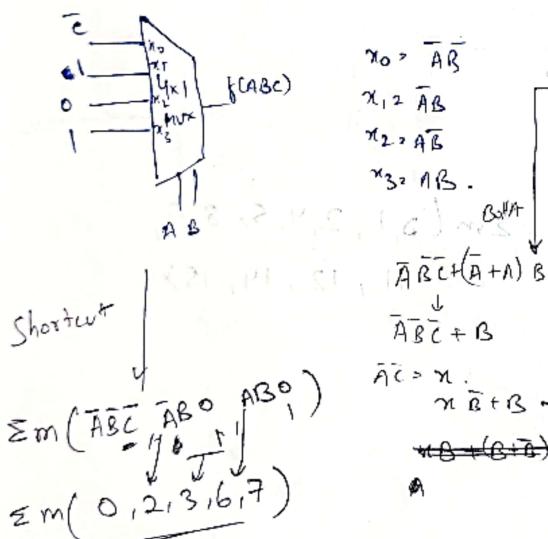

$$\begin{aligned}
 x_0 &= \bar{A}\bar{B} \\
 x_1 &= \bar{A}B \\
 x_2 &= A\bar{B} \\
 x_3 &= AB \\
 f(A, B, C) &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B} \cdot 1 + \bar{A}\bar{B} \cdot 0 + A\bar{B} \cdot 1 \\
 &\stackrel{\text{canonical form}}{=} \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B} + A\bar{B} \\
 &\stackrel{\text{Karnaugh Map}}{=} \sum m(0, 2, 3, 6, 7) \\
 &\stackrel{\text{K-MAP}}{=} \bar{A} + \bar{A}\bar{C}
 \end{aligned}$$
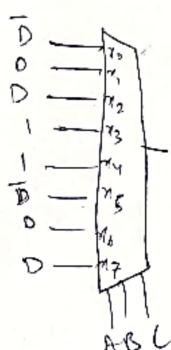
$$\begin{aligned}
 \bar{A}\bar{C} &= x \\
 \bar{A}\bar{B} + B &\rightarrow (B+x)(\bar{B}+B) \\
 \cancel{x(B+\bar{B})} &\rightarrow B+x \rightarrow B + \bar{A}\bar{C}
 \end{aligned}$$



$$\begin{aligned}
 x_0 &= \bar{A}\bar{B}\bar{C} \rightarrow \bar{D} \\
 x_1 &= \bar{A}\bar{B}\bar{C} \rightarrow 0X \\
 x_2 &= \bar{A}\bar{B}\bar{C} \rightarrow D \\
 x_3 &= \bar{A}\bar{B}\bar{C} \rightarrow 1, 0 \\
 x_4 &= \bar{A}\bar{B}\bar{C} \rightarrow 1, 0 \\
 x_5 &= \bar{A}\bar{B}\bar{C} \rightarrow \bar{D} \\
 x_6 &= \bar{A}\bar{B}\bar{C} \rightarrow 0X \\
 x_7 &= \bar{A}\bar{B}\bar{C} \rightarrow 0
 \end{aligned}$$


$$\begin{aligned}
 f(D, A, B, C) &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} \\
 &\quad + A\bar{B}\bar{C}\bar{D} + ABCD \\
 &= \sum m(0, 5, 6, 7, 8, 9, 10, 15)
 \end{aligned}$$

U.MAP

AB	$\bar{D}$	D	$\bar{D}$	D	$\bar{D}$	D	$\bar{D}$	D
AB 00	1		1		1		1	
$\bar{A}B$ 01		1		1		1		1
AB 11			1			1		1
$A\bar{B}$ 10	1	1	1	1	1	1	1	1

$$\begin{aligned} & A\bar{C}\bar{D} + A\bar{B}\bar{C} + A\bar{B}\bar{D} \\ & + \bar{A}BD + \bar{A}BC + BCD \end{aligned}$$

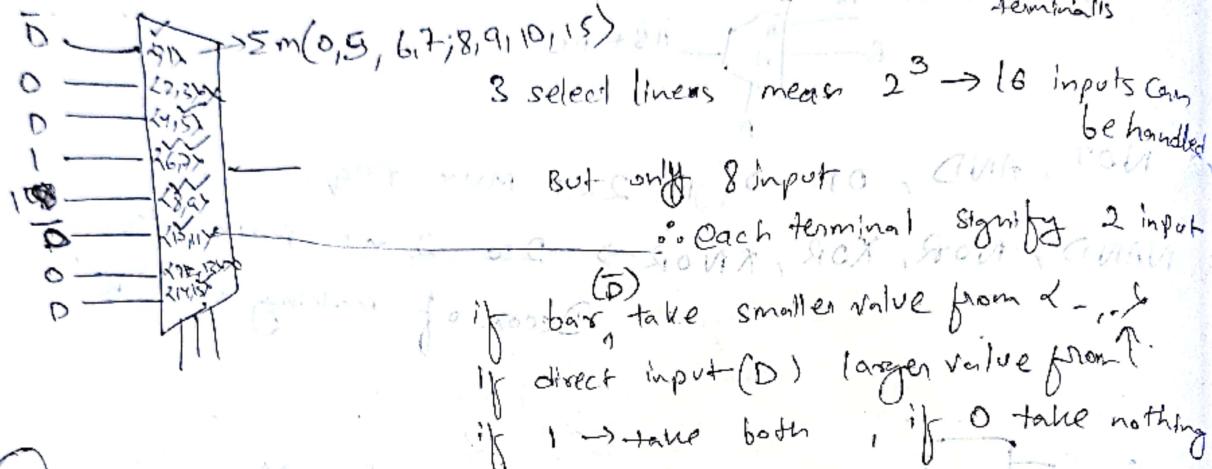Shortcut to find Sm. ( ) Only applicable when f(A, B, C) LSB is in input terminals



①

$$1 \rightarrow x_0(0,1)$$

$$\bar{S} \rightarrow x_2(2,3)$$

$$S \rightarrow x_3(4,5)$$

$$1 \rightarrow x_6(7)$$

$$0 \rightarrow x_8(9)$$

$$1 \rightarrow x_{10}(11)$$

$$\bar{S} \rightarrow x_{12}(13)$$

$$1 \rightarrow x_{14}(15)$$

1 1 1

PQ R

$$\sum m(0,1,2,4,5,6,7,10,11,12,14,15)$$

f(PQRS) → ~~1111~~

(2) 1 → x\_3(4,5)

S → x\_6(12,13)

S → x\_8(10,11)

S → x\_9(8,9)

0 → x\_3(6,7)

1 → x\_0(0,1)

$$\sum m(0,1,2,4,5,8,9,11,12,14,15)$$

$$S = x_2(3)$$

$$S = x_4(5)$$

$$S = x_6(12)$$

$$S = x_8(10)$$

$$S = x_9(9)$$

$$S = x_0(0,1)$$

$$3x_0(0,1) + 3x_2(3) + 3x_4(5) =$$

$$3x_0(0,1) + 3x_6(12) + 3x_8(10) =$$

$$3x_0(0,1) + 3x_9(9) + 3x_0(0,1) =$$

$$(3x_0(0,1) + 3x_9(9)) + (3x_0(0,1) + 3x_6(12)) + (3x_0(0,1) + 3x_8(10)) =$$

$$3x_0(0,1) + 3x_2(3) + 3x_4(5) =$$


$$3x_0(0,1) + 3x_6(12) + 3x_8(10) =$$

$$3x_0(0,1) + 3x_9(9) + 3x_0(0,1) =$$


$$(3x_0(0,1) + 3x_9(9)) + (3x_0(0,1) + 3x_6(12)) + (3x_0(0,1) + 3x_8(10)) =$$




#### Type 4. Cascading of MUX.

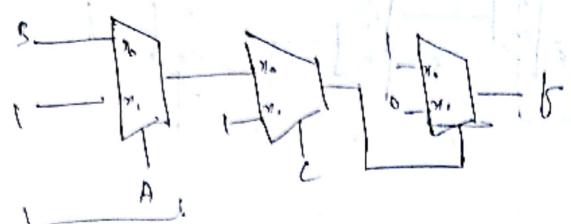

$$\begin{aligned}
 & \overline{AB} + A \\
 & (\overline{AB} + A)C + C \\
 & \overline{ABC} + AC + C \\
 & (\overline{ABC})(\overline{AC})(\overline{C}) \\
 & (A + \overline{B} + \overline{C})(\overline{A} + C)(\overline{C}) \\
 & A\cancel{A} + AC + \cancel{B}\cancel{A} + \cancel{B}C + \cancel{A}\cancel{C} + \cancel{C}\cancel{C} \\
 & A + B + C \\
 & \overline{A} + \overline{B} + \overline{C} \\
 & \overline{ABC} = \overline{A + B + C}
 \end{aligned}$$

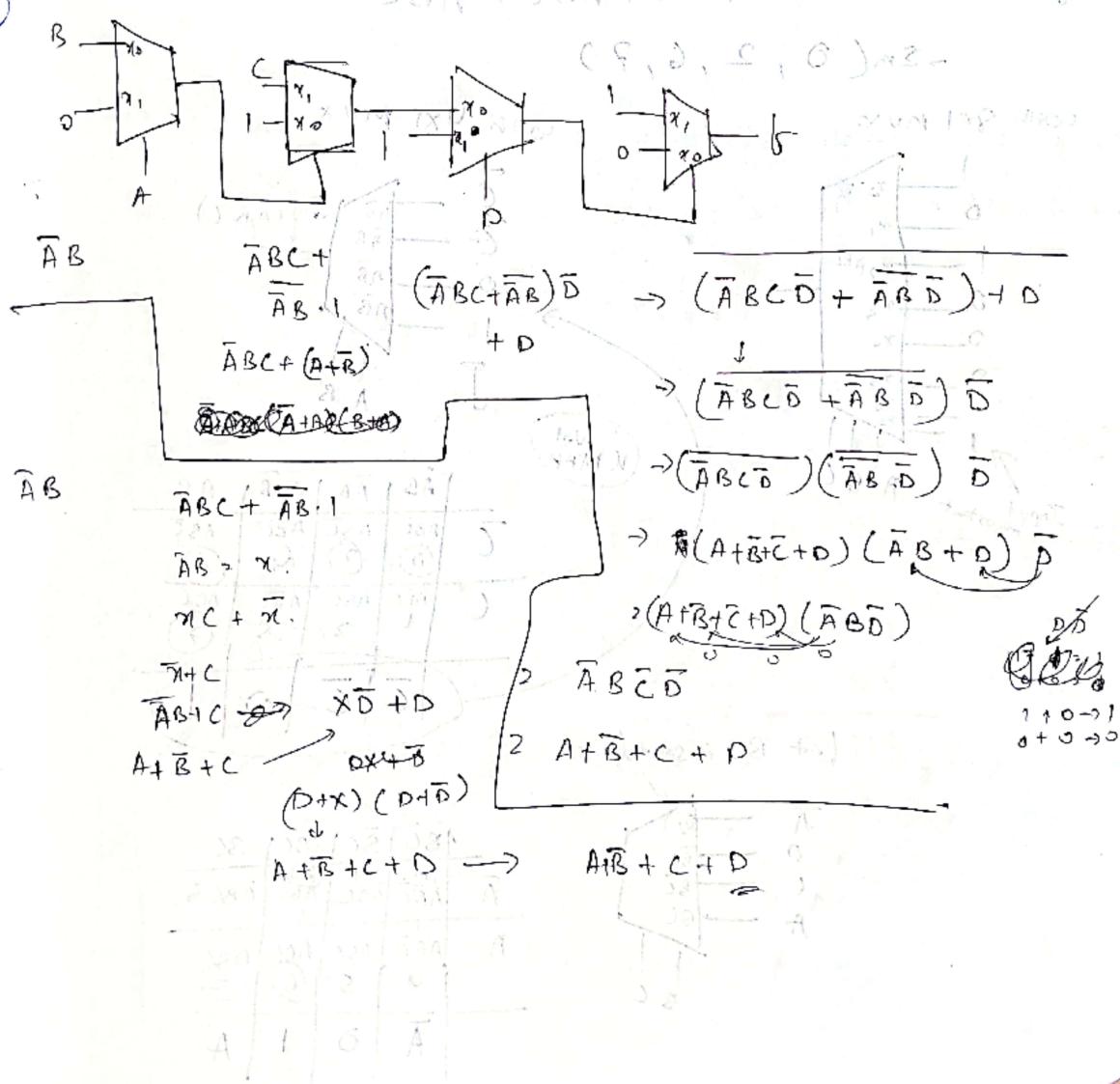

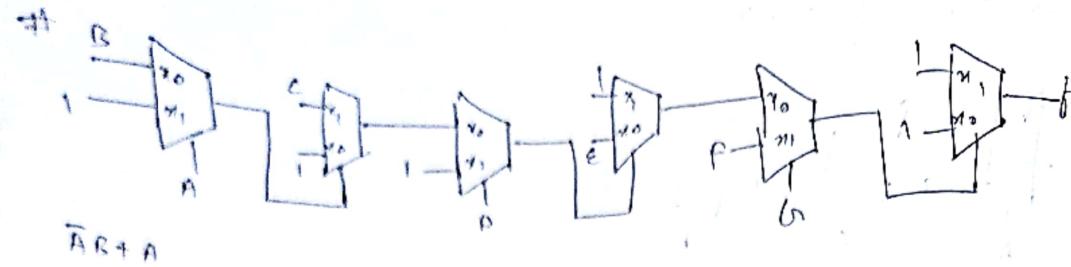

$$\bar{A}B + A$$

$$(A \cdot \bar{B}) \cdot (B \cdot \bar{C})$$

$$A \cdot B \rightarrow \bar{x}C + \bar{x}$$

$$(x_1 \cdot \bar{x}_2) \cdot (x_2 \cdot \bar{x}_3)$$

$$C + \frac{1}{A+B}$$

$$C + \bar{A}\bar{B}$$

$$\bar{D}x + D$$

$$\bar{D}x + D$$

$$C + \bar{A}\bar{B} + D$$

$$Dx + \bar{x}E$$

$$E + x$$

$$E + C + \bar{A}\bar{B} + D$$

$$C + J$$

$$x\bar{G} + FG$$

$$(\bar{x} + \bar{x}) \rightarrow 1 \text{ Ans}$$




$$1 = \bar{x} + \bar{x}$$

Type - 5 Implementation of function.

$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$


$$\rightarrow \Sigma m(0, 2, 6, 7)$$

with 8x1 MUX:

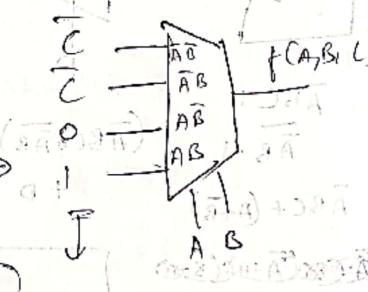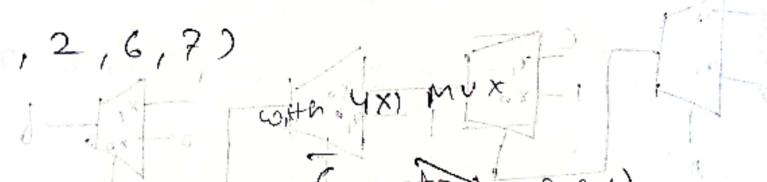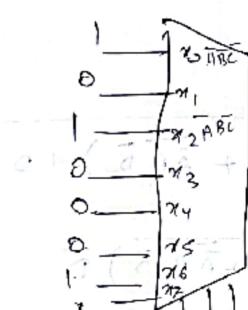


$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}$	0	2	4
C	1	3	5
	6	7	

Let BC is select line

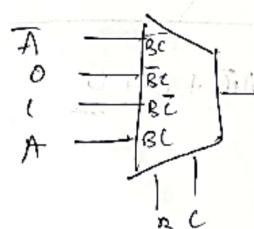


$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	0	1	2
A	3	4	5
	6	7	

with 2x1 MUX

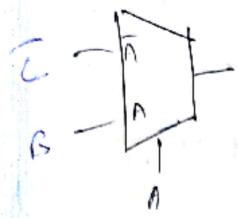


	A	A	
$\bar{B} \bar{C}$	$\bar{A} B \bar{C}$ 0	$\bar{A} \bar{B} \bar{C}$ 4	
$B \bar{C}$	$\bar{A} \bar{B} C$ 1	$\bar{A} B C$ 5	
$B \bar{C}$	$\bar{A} B \bar{C}$ 2	$\bar{A} \bar{B} C$ 6	
$B C$	$\bar{A} B C$ 3	$\bar{A} \bar{B} \bar{C}$ 7	
	$\bar{B} \bar{C} + \bar{B} C$	$\bar{B} \bar{C} + B C$	
	$\bar{C}$	$B$	

Let B as selected

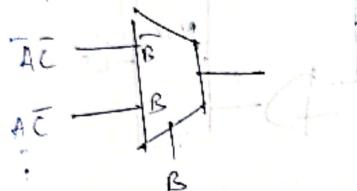


	B	B
$\bar{A}C$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$
$\bar{A}C$	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$
$A\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$AB\bar{C}$
$AC$	$\bar{A}\bar{B}C$	$AB\bar{C}$
<hr/>		
	$\bar{A}C$	$\bar{A}\bar{B}C$

~~Type-6~~ Delay

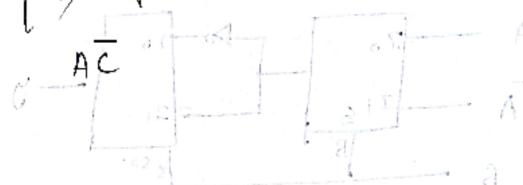


$$\text{MUX} = 2 \mu\text{s}$$

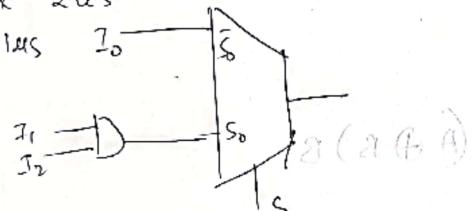

$$S_0 > 0 \quad J_0 \text{ delay} = 20 \text{ s (min)}$$

$$S_0 = 1 \quad I_1, I_2 \quad \text{delay} > 3 \mu\text{s (max)}$$
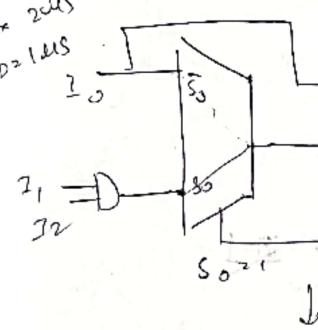
$$\begin{aligned} Mv &= 2 \text{ MS} \\ AND &= 1 \text{ MS} \end{aligned}$$



$$S_0 = 0 \quad T_0 = 200\text{ns} + \frac{2}{2000/\mu\text{A}} 200\text{ns}$$

$$S_0 = 0, \quad I_0 = 2\mu S, \quad 2\mu S > 4\mu S$$

$$S_0 > 1 \left[ 1\mu S + 2\mu S \right] + 2\mu S \sqrt{S} = 2\mu S \quad \text{at } \frac{d}{a} = \frac{2\mu S}{\mu S}$$

X

only  
depends  
on  $I_0$


$(S+2)(S+2)$

Note: The propagation delay of the NOR gate, AND gate multiplexer (MUX) in the circuit shown in the figure are 4ns, 2ns, 1ns. If all the inputs P, Q, R, S, T are applied simultaneously and held constant the max. propagation delay of the circuit is :-


$$S = 0 \\ \text{xor} = 4\text{ns} \\ + 1\text{ns} \\ \underline{\quad 5\text{ns}}$$

$$S = 1 \\ \text{AND} = 2\text{ns} \\ + 2\text{ns} \\ + 2\text{ns} \\ \underline{\quad 5\text{ns}}$$

PQ	AND,	2ns
		+ 1ns
		3ns
		+ 1ns
		4ns
	MUX	1ns
		+ 2ns
		3ns
		+ 1ns
		4ns
		+ 2ns
		6ns

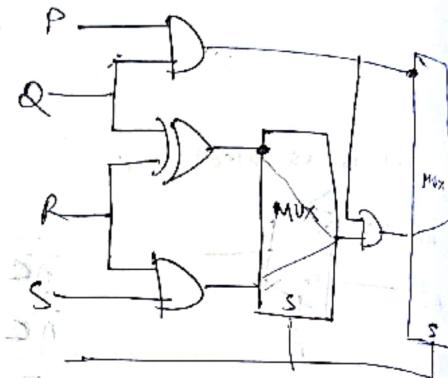

Ans 6ns.

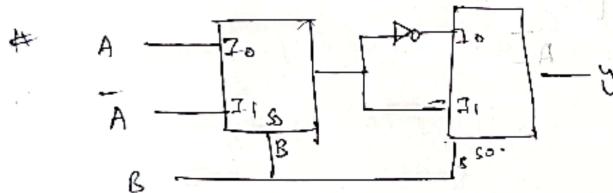



$$\bar{B}A + \bar{A}B \quad | \quad y = \bar{B}A + \bar{A}A$$

$$A \oplus B \quad | \quad (\bar{A} \oplus B)\bar{B} + (A \oplus B)B$$

$$\bar{A}\bar{B} + A\bar{B}/\bar{B} + \bar{A}B/\bar{B} + A\bar{B}/B$$

$$\bar{A}\bar{B} + \bar{A}B \rightarrow \bar{A}(\bar{B} + B)$$

$\bar{A}$

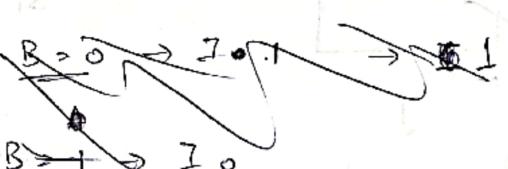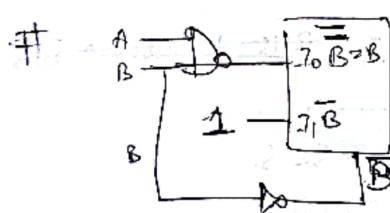


$$\bar{B} \rightarrow \bar{B}$$

$$B \rightarrow \bar{A}B \rightarrow \bar{B}$$

$$\begin{aligned} & \rightarrow (\bar{A} + \bar{B})\bar{B} \\ & \rightarrow \bar{A}\bar{B} + \bar{B} + \bar{B} \\ & \rightarrow \bar{A}\bar{B} \end{aligned}$$
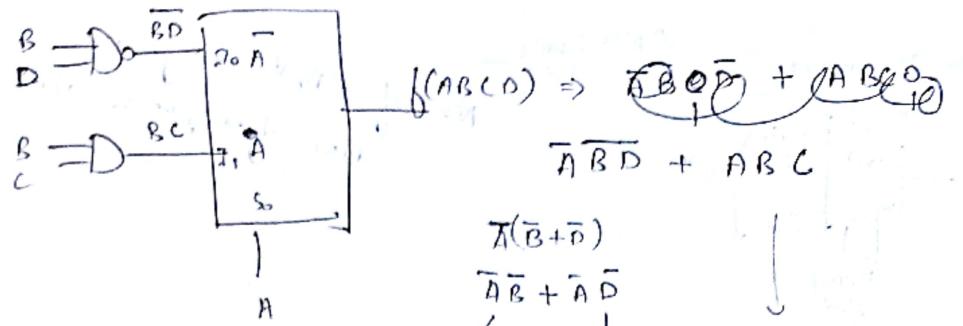
$$\begin{aligned} & \bar{A}\bar{B} + \bar{B} \\ & (\bar{A}B + \bar{B})(B + \bar{B}) \\ & \downarrow \\ & \bar{A} + \bar{B} \end{aligned}$$






$$\begin{aligned} & f(ABCD) = \overline{ABD} + ABC \\ & \overline{ABD} + ABC \\ & \overline{A}\overline{B} + \overline{A}\overline{D} \\ & \downarrow \\ & A \text{ 4 combo } \quad \overline{A} \text{ 4 combo } + 2^2 \\ & \overline{AB}00 \rightarrow 0 \quad \overline{A}00 \overline{D} \rightarrow 0 \\ & 01 \rightarrow 1 \quad 01 \rightarrow 2 \\ & 10 \rightarrow 2 \quad 10 \rightarrow 4 \\ & 11 \rightarrow 3 \quad 11 \rightarrow 6 \end{aligned}$$

$$ABC0 \rightarrow 14$$

$$1 \quad 15.$$
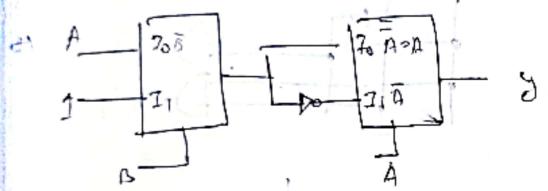
$$\therefore \Sigma_m(0, 1, 2, 3, 4, 6, 14, 15)$$



$$\rightarrow \overline{BA} + B$$

$$A+B$$

$$AX + \overline{A}X$$

$$A(A+B) + \overline{A}(\overline{A}+B)$$


$$\begin{aligned} & A + AB + \overline{A}B \\ & A[1+B] \\ & 1 \rightarrow A \end{aligned}$$

$$A + AB + \overline{A}B$$

$$AB + A\overline{B} + A\overline{B} + \overline{A}\overline{B}$$

$$AB + A\overline{B} + \overline{A}\overline{B}$$

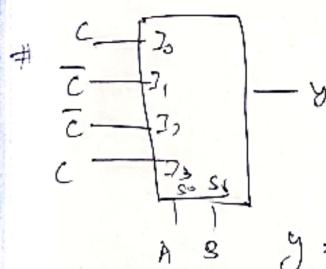4. Other Boolean functions obtained from  $\Sigma_m(0, 1, 2, 4, 7)$



$$y = \overline{AB}C + \overline{AB}\overline{C} + \overline{AB}\overline{C} + ABC$$

$\overline{A}$	$\overline{B}$	$C$	$\overline{C}$	$\overline{C}$	$C$
0	0	0	1	1	0
1	0	1	0	0	1

$$\begin{aligned} & \overline{B} + A \rightarrow \overline{A}\overline{B} \\ & \overline{A}\overline{B} \rightarrow \overline{A} + \overline{B} \rightarrow A + \overline{B} \end{aligned}$$

$\overline{B}$	$\overline{C}$	$B$	$C$	$\overline{B}$	$\overline{C}$	$B$	$C$
0	0	0	0	1	1	1	0
1	0	1	0	1	0	0	1


$$\Sigma_m(1, 2, 4, 7)$$



$$A \oplus B \oplus C$$

$$\begin{aligned} & (\overline{AB} + AB)C + (\overline{AB} + AB)\overline{C} \\ & = C + (A \oplus B)C \end{aligned}$$

$$= \Sigma(1, 2, 4, 7)$$

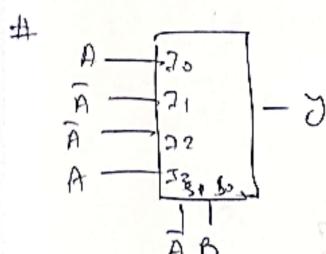


$$\begin{aligned} & 1 + \overline{A} = 1 \text{ for all } A \\ & \overline{B} + 0 + \overline{A}\overline{B} + 0 \end{aligned}$$

$$\overline{B}(1 + \overline{A}) \rightarrow \overline{B}$$



## B De-MUX


↳ Data Distributor.

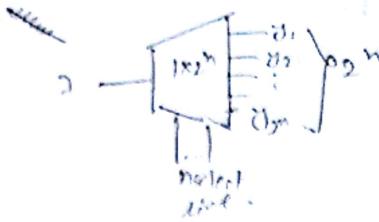

AND logic

No. of AND logic =  
No. of output in Dem.


Design a  $1 \times 2$  Demux?

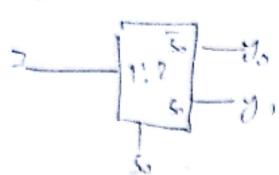



$S_0$	$Y_0 \cdot I$
0	$I \cdot 0 = 0$
1	$I \cdot 1 = I$

$$Y_0 = \overline{S}_0 I$$

Already minimized.

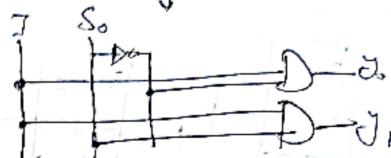

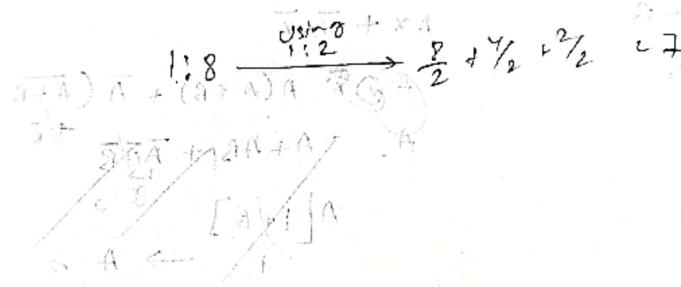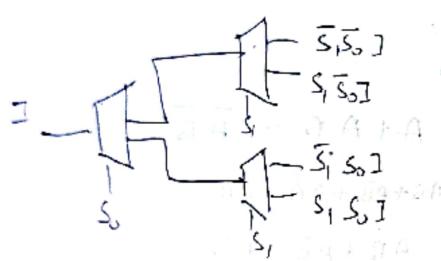$1 \times 2$  Demux  $\frac{1}{2} + \frac{1}{2} \xrightarrow[2+1=3]{} 1 \times 4$  Demux.



## Encoder

↳ Any  $\xrightarrow{\text{Convert}}$  Coode to Binary.

4x2 Encoder [Equal to Binary Encoder]

8x3  
16x4.



Complement

$(\bar{x})$ 's complement  $\xrightarrow{\text{Convert}}$   $(x)$ 's complement.

Base 2      1's

2's

Base 8      7's

8's

Base 10      9's

10's

Base 16      E's

F's

## $\bar{x}$ -1's complement

Subtract from most digit  $\xrightarrow{1}$

Base 2      Complement of 0 =  $1 - 0 = 1$

$$\begin{array}{r} 111 \\ - 101 \\ \hline 010 \end{array} \quad 1 + 1 + 1 = 3 \quad 1 + 1 + 1 = 3 \quad 1 + 1 + 1 = 3$$



Base 8      7's complement

$$373 \xrightarrow{-373} \frac{404}{404}$$



Base 10 → also a weighted code  

$$\begin{array}{r} 9 \\ -1 \\ \hline 8 \end{array}$$

$$\begin{array}{r} 9 \\ -2 \\ \hline 7 \end{array}$$
 self complement

RCD → Binary Coded Decimal (Also a weighted code) But not self complemented

↳ Each decimal no. are represented by 4 bits

$$Ex: 2 \rightarrow 0010$$

$$4 \rightarrow 0100$$

$$9 \rightarrow 1001$$

$$\begin{array}{r} 1 \\ \downarrow \\ 0 \\ \hline 0001 \quad 0000 \end{array}$$

$$\begin{array}{r} 1 \\ \downarrow \\ 1 \\ \hline 0001 \quad 0001 \end{array}$$

Excess-3 (Not a weighted code) But a self complemented.  
 ↳ It means the value is added with 3.

$$Like: 0 + 3 = 3 = 0011$$

$$7 + 3 = 10 = 1010$$

4221 code. → weighted and self complemented

$$0 \rightarrow 0000$$

$$1 \rightarrow 0001$$



$$2 \rightarrow 0010$$

$$2 \rightarrow 0100$$

$$3 \rightarrow 0101$$

### Encoder

4x2 encoder.

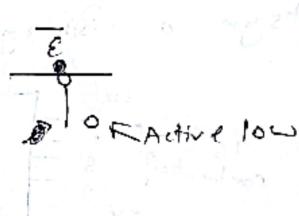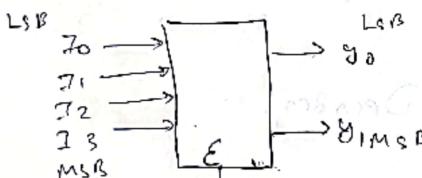


Truth table -

when $E = 1$				$Y_1$	$Y_0$
MSB $I_3$	$I_2$	$I_1$	$I_0$		
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$Y_0 = I_1 + I_3 \quad Y_1 = I_2 + I_3$$

No minimization possible

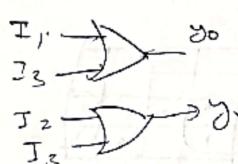




Priority Encoder.				Last LSR Priority Encoder.				MSB priority encoder	
in	in	in	in	in	in	LSR		000X	01
X	X	X	1	0	0	0			
X	X	1	0	0	0	1			
X	1	0	0	0	0	1			

## Decoder

Circuit which converts Binary into any other code.  
~~No. of AND gate req. = No. of output~~


1. 2x4 Decoder

$3 \times 8$   
 $4 \times 16$  . . .

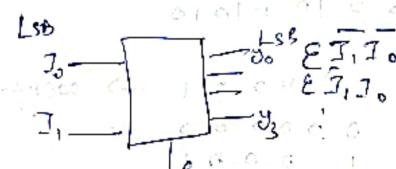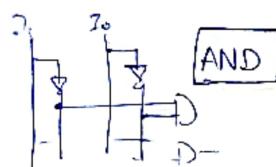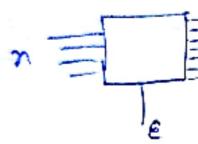

J <sub>1</sub>	J <sub>0</sub>	y <sub>3</sub>	y <sub>2</sub>	y <sub>1</sub>	y <sub>0</sub>
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	0	1	0	0

Design a Binary to Decimal Decoder?

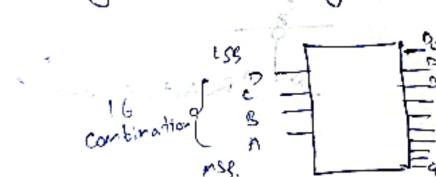

Address of 10 digits  $\rightarrow n = \log_2 M$

$$n = \log_2 10A$$

$$n = 4.$$

$2^{n-m}$  address of 10 digits  $\rightarrow n = \log_2 M$

0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111

For 0-9, 10 different K-MAP

D <sub>0</sub>	00	01	11	10
D <sub>1</sub>	00	01	11	10
D <sub>2</sub>	00	01	11	10
D <sub>3</sub>	00	01	11	10

D <sub>1</sub>	00	01	11	10
D <sub>2</sub>	00	01	11	10
D <sub>3</sub>	00	01	11	10
D <sub>4</sub>	00	01	11	10


$\bar{A} \bar{B} \bar{C} \bar{D}$

D <sub>7</sub>	00	01	11	10
BCD	00	01	11	10
D <sub>8</sub>	00	01	11	10
AD	00	01	11	10

D <sub>8</sub>	00	01	11	10
AD	00	01	11	10
D <sub>9</sub>	00	01	11	10
D <sub>10</sub>	00	01	11	10



Standard in 1 HMP

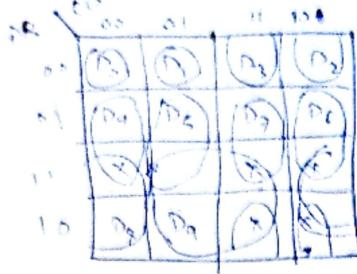


nachen Do resistance 0. ABID

bis B&D

Do = AD

Then Design.

Design 3x8 Decoder by using 2x4 Decoder.

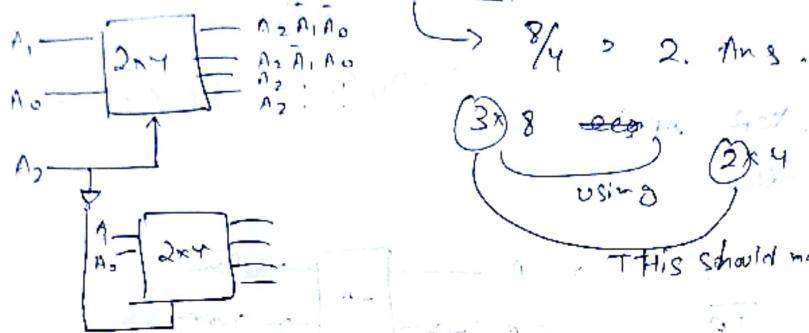





~~(3x8)~~ using ~~(2x4)~~ This should not be double.


$$2 \times 4 \xrightarrow{8/4=2} 3 \times 8$$

$$2 \times 4 \xrightarrow{8/4=2} 4 \times 16$$
  
Double  $16/4 + 4/4 \Rightarrow 4+1=5$ .


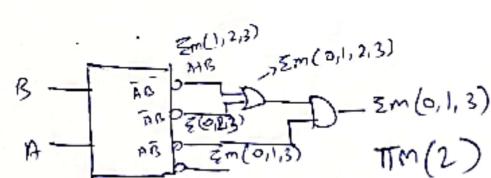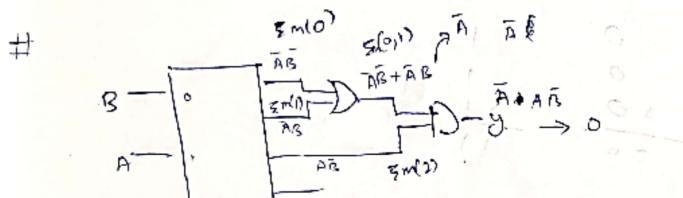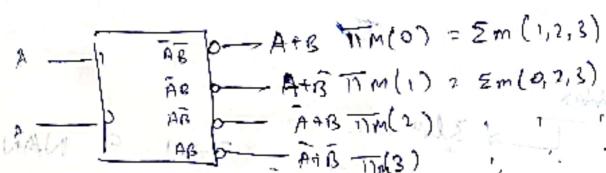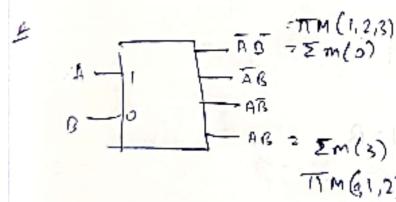
$$3 \times 8 \xrightarrow{64/8 + 8/8} 8+1=9$$



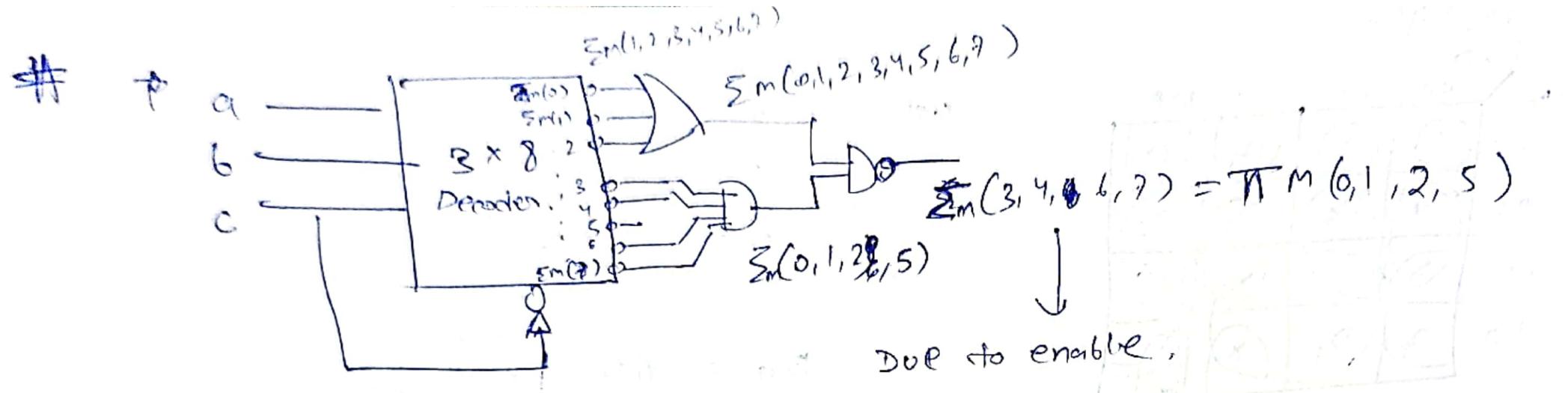

$$y_2 = \overline{C} \sum_m (3, 4, 6, 7)$$

$$\Rightarrow \overline{C} [\overline{ABC} + A\overline{B}\overline{C} + AB\overline{C} + ABC]$$

$$\overline{ABC} + A\overline{B}\overline{C}$$

$$= \sum_m (4, 6) = \overline{Z_M(0,1,2,3,5,7)}$$