

Digital Logic

Logic Gate \rightarrow NOT, AND, OR, NAND, NOR, X-OR, X-NOR

Minimization \rightarrow Boolean Algebra, K-MAP

Combinational Circuit \rightarrow (without memory) Comparator, MUX, DE-MUX, Encoder, decoder, Half Adder, Subadder, Half sub, Full sub, Serial adder, Full adder,

Sequential Circuit \rightarrow (with memory) Latches, Flip flop, Registers, Counters.


Number System \rightarrow Base conversion, Magnitude Representation, Look ahead carry adder, Multiplier, code converter.

Lec-1


Byte \rightarrow 8 bit, Nibble \rightarrow 4 bit

LSB \rightarrow Least Significant bit
MSB \rightarrow Most Significant bit

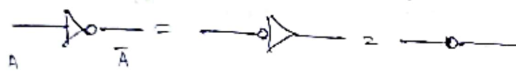
1. NOT gate [Inverter, Negation, Complement logic]




$T_{PD} \rightarrow$ Propagation Delay

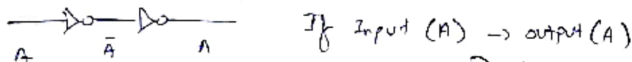


Buffer \rightarrow To provide delay

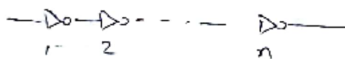

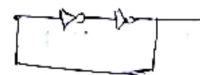If $n = \text{odd} = \text{inverter}$
 $n = \text{even} = \text{buffer}$




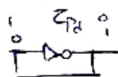
- 1) Basic memory element
- 2) Bistable multi vibrator
- 3) DC generator



$0 \rightarrow 1 \rightarrow 0 \rightarrow \dots$

- 1) Astable Multivibrator
- 2) Square wave generator
- 3) clock generator
- 4) Free Running circuit
- 5) Ring Oscillator

$$f = \frac{1}{T} = \frac{1}{2T_{PD}}$$

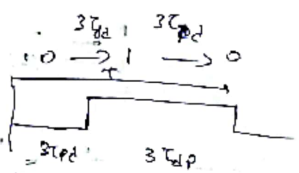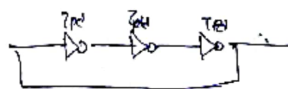


$$f = \frac{1}{6T_{PD}} = \frac{1}{2 \times 3T_{PD}} = \frac{1}{2NT_{PD}}$$

Here N must be odd


If N is even $f \neq \text{OHZ}$

If all the NOT gates are identical

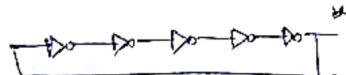

& having $T_{PD} = 2 \mu s$. Find the frequency
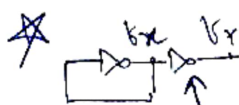
$$f = \frac{1}{2 \times 5 \times 2 \times 10^{-6}} \text{ Hz} = \frac{10^6}{10 \times 2} \text{ Hz} = \frac{50 \times 10^3}{10 \times 2} = 50 \text{ KHz}$$



freq. of X = freq. of Y

$$T_{PD} = 5 \mu s \rightarrow 10^{-12}$$

This will give no impact on frequency, it is just a time delay

AND (Intersection)



$$\begin{aligned} 0 \cdot 0 &= 0 \\ 0 \cdot 1 &= 0 \\ 1 \cdot 0 &= 0 \\ 1 \cdot 1 &= 1 \\ 1 \cdot A &= A \\ A \cdot A &= A \\ A \cdot 0 &= 0 \\ A \cdot \bar{A} &= 0 \end{aligned}$$

$$\begin{aligned} 1 + A &= 1 \\ A + 1 &= 1 \end{aligned}$$

$$\begin{aligned} A \cdot 0 &= 0 \\ A + 0 &= A \end{aligned}$$

OR (Union)





$$\begin{aligned} 0 + 0 &= 0 \\ 0 + 1 &= 1 \\ 1 + 0 &= 1 \\ 1 + 1 &= 1 \\ 1 + A &= 1 \\ A + 0 &= A \\ A + 1 &= 1 \\ A + \bar{A} &= 1 \end{aligned}$$



Floating Terminal
control input
strobe

Enable / Disable

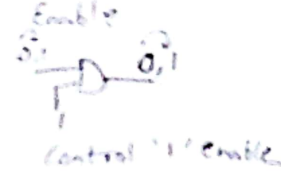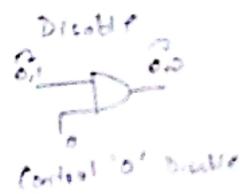

Commutative law

$$A \cdot B = B \cdot A$$

Associative law

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

OR gate

$$A + B = B + A$$

$$(A + B) + C = A + (B + C)$$




TTL = Transistor Transistor Logic

This is empty
always means 1 High



ECL - Emitter Coupled Logic

Floating terminal = 0 Low

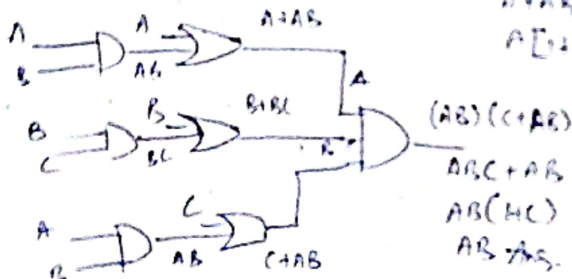



$$\begin{aligned} A + AB &= A \\ A + (A + B) &= A + 1 \end{aligned}$$

NAND

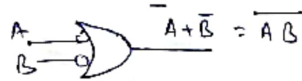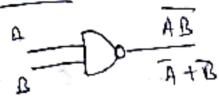

Bubbled OR gate = NAND


0 0	1
0 1	1
1 0	1
1 1	0

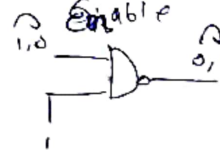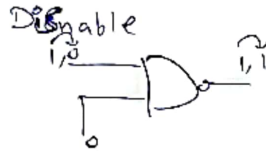



Follows Commutative law.

But Doesn't follow Associative law.

NOR

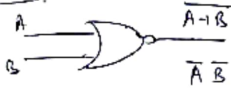

0 0	1
0 1	0
1 0	0
1 1	0

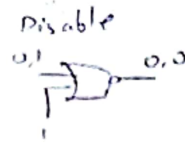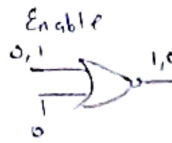


Follows Commutative law


NAND, NOR are called Universal logic

NAND


OR

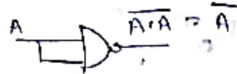

OR

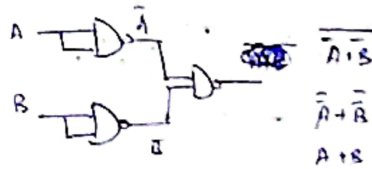


AND

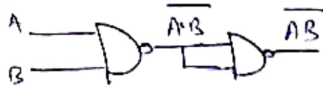

X-OR

$$A \oplus B = \bar{A}B + A\bar{B}$$

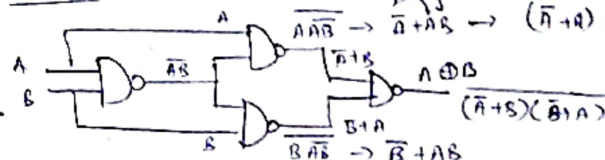

$$(\bar{A}+B)(\bar{B}+A)$$

$$(\bar{A}+B) + (\bar{B}+A)$$

$$(A+B) + (\bar{A}+\bar{B})$$


$$(A+B) + (\bar{A}+\bar{B})$$

$$(A+B) + (\bar{A}+\bar{B})$$

$$A\bar{B} + \bar{A}B$$

X-NOR.

$$A \odot B = \overline{A \oplus B}$$

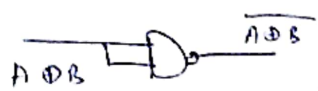

5.



NOT	NAND	NOR
	1	1
AND	2	3
OR	3	2
X-OR	4	5
X-NOR	5	4
NAND	1	4
NOR	4	1

NAND if 1 option to be chosen

4 Case 1


$$A \cdot B \cdot \bar{C} \cdot D \dots$$

$n =$ Total no. of variables

$k =$ Total no. of complement variables

NAND	NOR
$(2n-2)+k$	$(3n-3)-k$

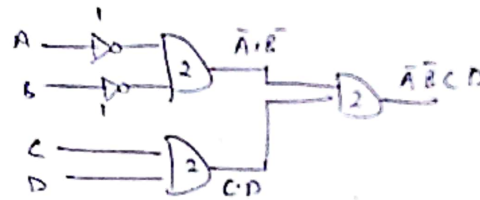
$$\bar{A} \cdot \bar{B} \cdot C \cdot D$$



3 Nand

$$(2 \times 4 - 2) = 6$$

NAND

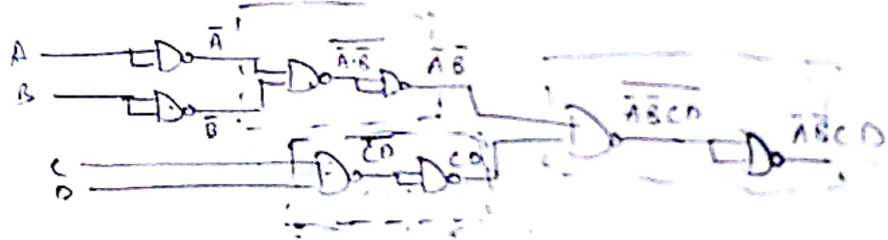

$$\bar{A} \cdot B \cdot C$$

NOR



$$(3 \times 3 - 3) = 6$$

$$6 - 1 = 5$$

Case 2 $\bar{A} + B + \bar{C} + \bar{D} + \dots$

NAND	NOR
$(3n-3)-K$	$(2n-2)+K$

$f_1 = \bar{A}\bar{B}\bar{C}D$ $f_2 = \bar{A}\bar{B}\bar{C}D + \bar{B}$
 The no. of NOR gate req.

$f_1 = (3 \times 4 - 3) - 3$
 $= 12 - 6$
 $= 6$

$f_2 = \bar{B} [\bar{A}\bar{C}D + 1]$
 $= \bar{B} [1]$
 $= \bar{B}$

$1 \cdot 0 = 1$
 $0 \cdot 1 = 1$


$\therefore f_1 - f_2 = 6 - 1 = 5$

$f = A + A\bar{B}C + ABC$
 Min. NAND gate req.

$A \rightarrow (2 \times 2 - 2) + 0$
 $= 2$


$A[1 + \bar{B}C + BC]$
 $A \rightarrow (2 \times 1 - 2) + 0 = 0$ Ans

$A + \bar{A} = 1$
 $A \cdot \bar{A} = 0$

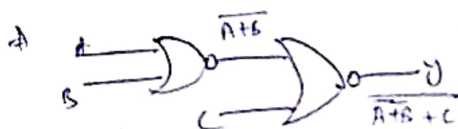

How many nand gates.

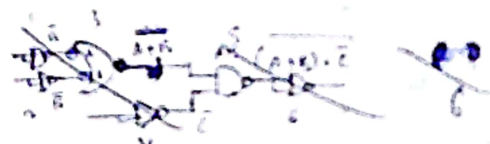$\bar{A} + B + C$
 $\bar{A} + B + \bar{C}$
 $(A + B) \cdot \bar{C}$
 $A\bar{C} + B\bar{C}$



5

CASE 3

$f = AB + CD$



$\therefore 3$ NAND

AND \rightarrow OR
 NAND \rightarrow NAND

$f = AB + C$
 $= AB \cdot CC$




SOP \rightarrow sum of product
 POS \rightarrow product of sum

$f = A\bar{B} + C$




$AB + CD + E$
 \times
 $xx + EE$

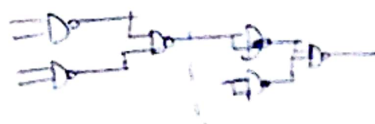

$$\# AB + BC + CD + DA$$

$$B(A+C) + D(A+C)$$

$$Bx + Dx$$

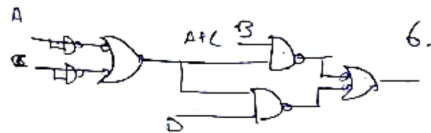


Case 4

4


$$\bar{A}B + A\bar{B} = A \oplus B$$

$$(A+B)(\bar{A}+\bar{B})$$

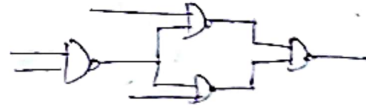


$$(A+B)(C+D)$$

NOR?

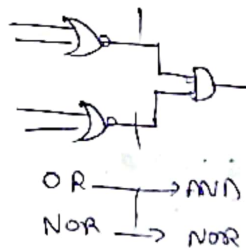

OR → AND
NOR → NOR

XOR

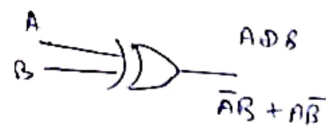

0	0	0
0	1	1
1	0	1
1	1	0

$$\sum m(1, 2, 4, 7)$$

↑
3 inputs = A ⊕ B

$$A = B \quad y = 0$$

$$A \neq B \quad y = 1$$

$$A \oplus A = 0$$

$$A \oplus 0 = A$$

$$A \oplus \bar{A} = 1$$


$$A \oplus 1 = \bar{A}$$

$$A \oplus A = 0$$


$$A \oplus A \oplus A = A$$

Odd	A = A
Even	A = 0


6

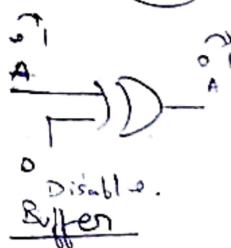

Disable Buffer

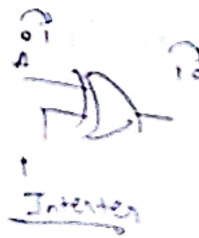

Interferer

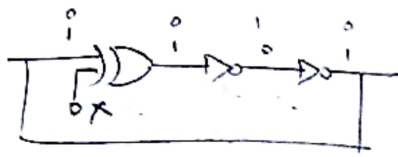

Astable Multivibrator x=1
Bistable


XOR follows. Commutative & Associative

$$A \oplus B \oplus C = \sum m(1, 2, 4, 7)$$


0	0	1
0	1	0
1	0	0
1	1	1



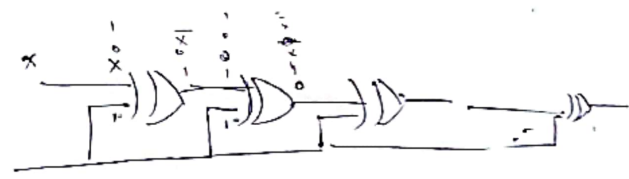$n = \text{even} = 1$
 $n = \text{odd} = 0$



odd = 1
 even = 0

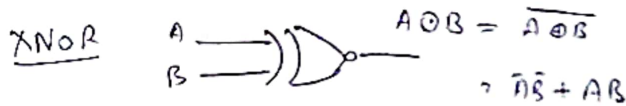

0 0 1
 0 1 0
 1 0 0
 1 1 1

Even parity detector.
 even = 1
 odd = 0
 coincidence





Commutative Δ Associative

$$A \oplus B \oplus C = (A \oplus B) \oplus C$$

For even input in XNOR = 1
 odd = 0

$$A \oplus A = 0$$

$$A \oplus 0 = A$$

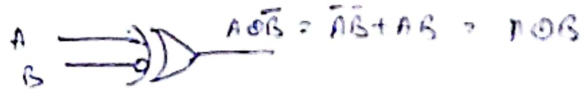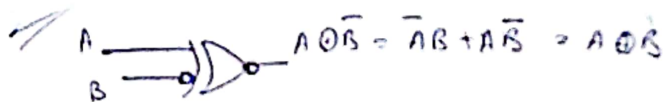

7) $f(A, B) = A \oplus B \oplus AB$

• OR gate


And OR gate seq. 3 NAND implement

8) $Y = A \oplus (A + B)$

$\overline{A} \cdot B$

A	B	A ⊕ B	A ⊕ B ⊕ AB
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

A	B	A ⊕ B	A ⊕ B ⊕ AB
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

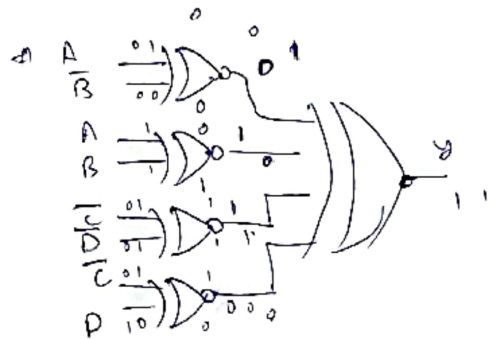

A	B	\bar{A}	\bar{B}
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

Minimization

Boolean Algebra

Boolean function,

→ combination of inputs on which output will depend

SOP

Sum of product
(min-term)

POS

Product of sum
(max-term)

min-term = max-term

$$f(A, B) = \bar{A}\bar{B} + AB$$

1 min-term

$$f(A, B) = (\bar{A} + B)(A + \bar{B})$$

max-term

Literals → combination of
A → A, \bar{A}
B → B, \bar{B}

$$f(A, B, C) = \bar{A}\bar{B} + \bar{C} + A\bar{B}$$

4 literals

Decimal	ABC	Min-term	Max-term
0	000	$\bar{A}\bar{B}\bar{C}$	$A + B + C$
1	001	$\bar{A}\bar{B}C$	$A + B + \bar{C}$
2	010	$\bar{A}B\bar{C}$	
3	011	$\bar{A}BC$	
4	100	$A\bar{B}\bar{C}$	
5	101	$A\bar{B}C$	
6	110	$AB\bar{C}$	
7	111	ABC	$\bar{A} + \bar{B} + \bar{C}$

Min-term means. A=1 \bar{A} =0

Max-term means A=0 \bar{A} =1

0	00	$\bar{A} \bar{B}$	$A+B$	1
1	01	$\bar{A} B$	$A+B$	0
2	10	$A \bar{B}$	$A+B$	0
3	11	AB	$A+B$	1

Standard Canonical
Contains all the form of variable.

SOP
 $f(A,B) = \bar{A}\bar{B} \cdot 1 + \bar{A}B \cdot 0 + A\bar{B} \cdot 0 + AB \cdot 1$
 Variables + $\bar{A}\bar{B} \cdot 0 + AB \cdot 1$

$\bar{A}\bar{B} + AB = m_0 + m_3$
 $= \sum m(0,3)$

POS
 $F(A,B) = (A+B+1)(A+B+0)(\bar{A}+B+0)(\bar{A}+\bar{B}+1)$
 $(A+B)(\bar{A}+B)$

$\Pi M(1,2)$

Practice Sheet

1. $f = (A+B)(A+C)(A+E)$
 $= (A+B)(A\bar{A} + A\bar{C} + AC + C\bar{C})$
 $= (A+B)(A + A\bar{C} + AC)$
 $= (A+B)A(1 + \bar{C} + C)$
 $= AA + AB$
 $= A(1+B)$
 $= A + AB$

Distribution Law

$(A+B)(A+C)(A+E)$
 $(A+B)(A+C)$
 $(A+B)(A+C)(A+E)$
 $(A+B)(A+C)$
 $(A+B)A$

2. $f(A,B,C) = BC[A + B\bar{C} + \bar{B}CD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}]$

$BC\bar{C}$
 $= AB\bar{C} + B\bar{C}D + \bar{A}\bar{B}\bar{C}$
 $= [A + B + \bar{A}] B\bar{C}$
 $= B\bar{C}$

4. $f(A,B,C) = (A+B)(\bar{B}+C)(A+C)$

$= (A+B)(\bar{B}+C)(A+C)$
 $= (A+B)(\bar{B}+C)$
 $= \bar{A}\bar{B} + B\bar{C} + \bar{A}C$

Considers theorem. \rightarrow If 2 variables will repeat in 3 terms and the one having both forms of literal is the ans.

Example
 $AB + \bar{A}C + BC$
 Ans. $AB + \bar{A}C$

$AB + \bar{A}C + BCD$
 Ans. $AB + \bar{A}C$

Transpose Theorem.

$$\begin{aligned} & \star (A+B)(\bar{A}+C) \\ & \quad \underline{A\bar{A}+BC+\bar{A}B+AC} \\ & \quad \quad \underline{BC+\bar{A}B+AC} \\ & \quad \quad \quad \bar{A}B+AC \end{aligned}$$

So

$$\begin{aligned} & (A+B)(\bar{A}+C) \\ & \quad \underline{AC+\bar{A}B} \end{aligned}$$

$$\begin{aligned} & (\bar{A}+B)(A+B) \\ & \quad \underline{\bar{A}B + A\bar{B} = A \oplus B} \end{aligned}$$

$$5. \{ (A, B, C, D) = AB + \bar{A}\bar{C}D + B\bar{C}D$$

$$\begin{aligned} & \quad \quad \quad \text{C-ABCD} \\ & \quad \quad \quad \text{C-ABCD} \\ & \quad \quad \quad \rightarrow AB + (\bar{A} + \bar{B})CD \\ & \quad \quad \quad \quad \downarrow \\ & \quad \quad \quad \rightarrow \underbrace{AB}_X + \underbrace{\bar{A}\bar{B}}_{\bar{X}} CD \\ & \quad \quad \quad \rightarrow X + \bar{X}CD \\ & \quad \quad \quad \quad \downarrow \\ & \quad \quad \quad \rightarrow (X + \bar{X})(X + CD) \\ & \quad \quad \quad \quad \downarrow \\ & \quad \quad \quad \rightarrow AB + CD \end{aligned}$$

$$6. \{ (A, B, C) = \bar{A}\bar{B} + \bar{A}BC + A\bar{B}C$$

$$\begin{aligned} & \quad \quad \quad \rightarrow \bar{A}\bar{B} + (\bar{A}C + \bar{A}\bar{C})AB \\ & \quad \quad \quad \rightarrow \bar{A}\bar{B} + \bar{A}B \\ & \quad \quad \quad \rightarrow \bar{A}(\bar{B} + B) \\ & \quad \quad \quad \rightarrow \bar{A} \end{aligned}$$

$$\Rightarrow \overline{AB + A\bar{B}} = (\overline{AB})(\overline{A\bar{B}}) = (A+B)(\bar{A}+\bar{B})$$

$$\begin{aligned} \overline{AB\bar{C}D} &= \bar{A}\bar{B} + CD \\ &= \bar{A} + \bar{B} + CD \end{aligned}$$

$$\begin{aligned} \overline{A\bar{B}C} &= \bar{A}B + \bar{C} \\ &= (A+\bar{C})(\bar{B}+\bar{C}) \end{aligned}$$

$$\# A \oplus \bar{B} = A \odot B = \bar{A} \oplus B \quad \star$$

$$\overline{A \oplus B} = A \odot B = A \oplus B$$

$$\overline{\bar{A} \odot \bar{B}} = \bar{A} \oplus \bar{B} = A \oplus B \quad \checkmark$$

1 bar remove \rightarrow sign changes.

$$\overline{\bar{A} \oplus \bar{B}} = \bar{A} \odot \bar{B} = A \odot B$$

Duality

$$A \cdot B \rightarrow A + B$$

$$A \oplus B \rightarrow A \odot B$$

$$\overline{AB} \rightarrow \overline{A+B}$$

$$\bar{A} \rightarrow \bar{\bar{A}}$$

$$A \rightarrow A$$

2 variable $\rightarrow 4$
3 " $\rightarrow 8$
n " $\rightarrow 2^n$

Total expression = $2 \cdot 2^n$

$$\hookrightarrow 2^{2^n-1}$$

\rightarrow Self Dual

\rightarrow minimization technique.

If $f^D = f$ \rightarrow Duality
than self dual $A \rightarrow A$

$$f = AB + BC + AC$$

$$f^D = (A+B)(B+C)(A+C)$$

$$= (A+BC)(B+C)$$

$$= AB + AC + BCB + BCC$$

$$= AB + AC + BC \rightarrow \text{Self Dual.}$$

