

Digital logic

12/7/22

Number System

$$N = \sum a_i x^i$$

Example

$$(340)_{10} = 3 \times 10^2 + 0 \times 10^1 + 0 \times 10^0$$

[for decimal,
 $x=10$,
 $a_i = \text{Digits}]$

$$(1010)_2 = 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 8 + 2 = (10)_{10}$$

Bit (Binary digit)

$$x = 2 \quad [x = \text{Radix / Base}]$$

1) $(0.43)_{10} = 4 \times 2^{-1} + 3 \times 2^{-2}$

$$(0.43)_{10} = (0.75)_{10}$$

2) $(0.11)_{10} = 1 \times 2^{-1} + 1 \times 2^{-2} - 2$

$$(0.11)_{10} = \frac{1}{2} + \frac{1}{4} = 0.5 + 0.25 = (0.75)_{10}$$

[Binary \rightarrow Decimal]
 $N_2 = (0.75)_{10}$

3) $(0.101)_2 = 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3}$

$$(0.101)_2 = (0.625)_{10}$$

$b-1 = 1$
 $b-2 = 0$
 $b-3 = 1$

Octal system ($x=8$)

Digits $\rightarrow 0-7$

$$(127.4)_8 = 1 \times 8^2 + 2 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1}$$

$$(127.4)_8 = (87.5)_{10}$$

Decimal $\rightarrow 0-9$
Binary $\rightarrow 0-1$
Hexadecimal $\rightarrow (0-9), A, B, C, D, E, F$
($x=16$)
 $A=10, B=11, C=12, D=13$
 $E=14, F=15$
 $00_{NB} = (0)_{10}$

$$(e_1)_{16} = (12 \times 16^1 + 1 \times 16^0)_{10}$$

$$(d_1 d_0)_{16} = (193)_{10}$$

[Hexadecimal
decimal]

$$N_{10} \\ N_2 = ()_{10}$$

$$N_8 = ()_{10}$$

$$N_{16} = ()_{10}$$

$$N_{32} = ()_{10}$$

$$N_{16^2} \cup N_{10}$$

$$[0xAbcd \text{ &abcdH}]$$


$$\begin{aligned} ① i) (110101)_2 &= 2^5 + 2^4 + 2^2 + 2^0 \\ &= (53)_{10} \end{aligned}$$

Binary \longleftrightarrow Decimal

$$ii) (53)_{10} = (110101)_2$$

$$\begin{array}{r} 2 | 53 \\ 2 | 26 - 1 \\ 2 | 13 - 0 \\ 2 | 6 - 1 \\ 2 | 3 - 0 \\ \hline & 1 - 1 \end{array}$$

$$= (110101)_2$$

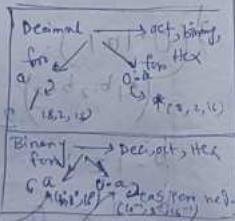

$$\begin{aligned} ② i) (0.101)_2 &= 2^{-1} + 2^{-3} \\ &= (0.625)_{10} \end{aligned}$$

$$\begin{aligned} ii) (0.625)_{10} &= (0.101)_2 \\ 0.625 \times 2 &= 0.25 - 1 \\ 0.25 \times 2 &= 0.5 - 0 \\ 0.5 \times 2 &= 1 - 1 \end{aligned}$$

$$③ (53.625)_{10} = (110101.101)_2$$

Decimal \longleftrightarrow octal

$$④ i) N_{10} = ()_8$$

$$(153)_{10} = (231)_8$$

$$\begin{array}{r} 8 | 153 \\ 8 | 19 - 1 \\ 8 | 12 - 3 \\ \hline & & 2 \\ & & 3 \end{array} \quad (231)_8$$

$$(0.513)_{10} = (0.40651)_8$$

$$0.513 \times 8 = 0.0 \cdot 104$$

$$0.104 \times 8 = 0.832$$

$$0.832 \times 8 = 0.656$$

$$0.656 \times 8 = 0.248$$

$$0.248 \times 8 = 0.384$$


$$0.384 \times 8 = 0.872$$

$$0.872 \times 8 = 0.872$$

Hexadecimal \longleftrightarrow
Decimal

For Integer Part $\rightarrow \frac{\square}{\square}$

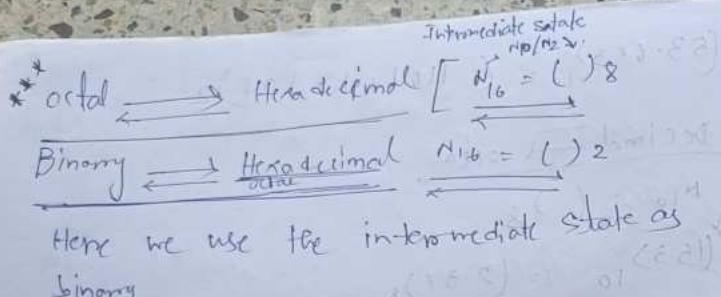For Fractional Part $\rightarrow \times 16$



4 bit binary	Decimal value	Octal
Range: 8 4 2 1	1	0 0
0 0 0 0	2	0 1
0 0 0 1	3	0 2
0 0 1 0	4	0 3
0 0 1 1	5	0 4
0 1 0 0	6	0 5
0 1 0 1	7	0 6
0 1 1 0	8	0 7
0 1 1 1	9	1 0
1 0 0 0	10	1 1
1 0 0 1	11	1 2
1 0 1 0	12	1 3
1 0 1 1	13	1 4
1 1 0 0	14	1 5
1 1 0 1	15	1 6
1 1 1 0	16	1 7
1 1 1 1	17	

[In decimal tree, value of 15 is equal to the value of 17 in octal (or binary)]

* $(157)_8 \quad [(157)_8 = (17)_8 \quad \text{Hexadecimal}]$

① $(157)_8 = (001101111)_2 \quad [3 \text{ bit}]$

Octal \rightarrow Binary

② $(A2C)_{16} = (101000101100)_2 \quad [4 \text{ bit}]$

Hexadecimal \rightarrow binary

③ $(0.125)_8 = (00010101)_2$

④ $(0.D2)_6 = (11010010)_2$

⑤ $(0.111100)_2 \rightarrow (0.74)_8 \quad [\text{Binary} \rightarrow \text{octal}]$

⑥ $(530010)_2 \rightarrow (0.11110010)_2 = (F2)_{16} \quad [\text{Hexadecimal} \leftarrow \text{Binary}]$

* $B \leftarrow 0 / +$
3 bit 4 bit
reflected replace
group group

$(157)_8 = (?)$

① $(157)_8 = (001101111)_2 \quad \text{Binary}$

Octal intermediate state
 $(06F)_{16} \quad \text{Hexadecimal}$

② $(6B.F2)_{16} = (01101011 \cdot 11110010)_2$
Before the DP After the decimal point

$(53.744)_8$

③ $(53.74)_8 = (0101011 \cdot 11100)_2$
 $= (2.B.F)_{16}$

12 $\rightarrow 8+4=12 \rightarrow 1100$
14 $\rightarrow 8+4+2=14 \rightarrow 1110$
13 $\rightarrow 8+4+1=13 \rightarrow 1101$

* 1's Complement

msb LSB
00001010 1' 9 $\rightarrow (11110101)_2$

(4 bit)
bit of width
on 12 bits
 $[01 \rightarrow 1, 1 \rightarrow 0]$

$(2r) = 1$

If intermediate part \rightarrow decimal

$$(1)_8 \rightarrow (1)_4$$

$$(1)_8 \rightarrow (1)_{10} \rightarrow (1)_{16}$$

$$\text{Ex: } (251)_8 \rightarrow \frac{2}{2} \frac{3}{1} \frac{1}{0} = 2 \times 8^2 + 3 \times 8^1 + 1 \times 8^0$$

$$\begin{aligned} &= 2 \times 8^2 + 3 \times 8^1 + 1 \times 8^0 \\ &= 128 + 24 + 1 \\ &= (153)_{10} \end{aligned}$$

$$\begin{array}{r} 153 \\ \times 16 \\ \hline 918 \\ 153 \\ \hline 153 \end{array}$$

$$(153)_{10} \rightarrow 16 \overline{)153} \quad (99)_{16}$$

$$\begin{array}{r} 153 \\ \times 16 \\ \hline 918 \\ 153 \\ \hline 153 \end{array}$$

$$(1)_{16} \rightarrow (1)_{10} \rightarrow (1)_8$$

$$\begin{aligned} (99)_{16} &= 9 \times 16^0 + 1 \times 16^1 \\ &= (99)_{10} \end{aligned}$$

$$(153)_{10} = 8 \overline{)153} \rightarrow (231)_8$$

A
B
C

2's Complement

$$\begin{array}{r} 1111010 \\ +1 \\ \hline 1111011 \end{array}$$

$\downarrow 2^{\text{s}}$

$$(00001010)_{2^{\text{s}}} \quad | 1^{\text{s}} + 1 = 2^{\text{s}}$$

$$\begin{array}{r} 1111010 \\ \downarrow 2^{\text{s}} \quad \text{copy direct} \\ 1111010 \end{array}$$

[LSB : Least Significant Bit]
[MSB = most " "]
[copy the first 1 until it appears copy the 0's also]

$$\begin{array}{r} 100001000 \\ \downarrow 2^{\text{s}} \quad \text{other process} \\ 1111011 \\ +1 \\ \hline 1111000 \end{array}$$

[copy the 0's until the first 1 appears]

$$\begin{array}{r} 00000001 \\ \downarrow 2^{\text{s}} \quad \text{other process} \\ 11111110 \end{array}$$

Uses

Signed numbers	→ Signed magnitude
	→ 2's complement
	→ Signed 2's complement

Sign bit = MSB

MSB = +ve
(1 = -ve)

How to identify the sign no.

Rest point

MSB	↓	1 magnitude
Sign bit		

→ 8 bit magnitude format

$(-1) = 1000001$

$(+1) = 0000001$

Signed magnitude

$(-1)_{1^{\text{s}}} \rightarrow 00000001 \rightarrow$ 8 bit magnitude

$\rightarrow (11111110)_{1^{\text{s}}}$

$(+1)_{1^{\text{s}}} = 00000001$

(11111110)

Signed 1's

(00000001) magnitude

To take the mag we have to get 1's complement
get 1's complement

$(+1) = 00000001$

$(-1) = 11111110$

Signed 2's

(11111110) signed 2's

$\downarrow 2^{\text{s}}$

(00000001) magnitude

To take the mag we have to get 2's complement

get

(11111000) signed 1's

$$\begin{array}{r} 11111000 \\ - 00000111 \\ \hline \text{magnitude?} \end{array}$$

$$\begin{array}{r} 10000000 \\ - 10000000 \\ \hline 00000000 \end{array} = (00000000)_2$$

$$\begin{array}{r} 10000000 \\ - 10000000 \\ \hline 00000000 \end{array} = (00000000)_2$$

(11111011) signed 2's

$$\begin{array}{r} (-00000100) \\ + 10000000 \\ \hline \text{magnitude} \end{array}$$

$$10000000 = (10000000)_2$$

$(-12) = (\quad)$ Signed 1's

$(-14) = (\quad)$ Signed 2's

① $00010010 = -12$

$$\begin{array}{r} 00010010 \\ - 00010010 \\ \hline 00000000 \end{array}$$

$\downarrow 1's$

(11110110) signed 1's

$(Ans - 11110011)$

② $-00010100 = -14$

$$\begin{array}{r} -00010100 \\ + 14 \rightarrow 00010100 \\ \hline 00000000 \end{array}$$

$\downarrow 2's$

(11110101) signed 2's

$(Ans - 11110010)$

Not those terms

Binary coded decimal (BCD)

$$(185)_{10} = (000110000101)_BCD$$

$$185 \rightarrow (000100101000)_2$$

$$0-9 \rightarrow (10111001)_2$$

By weightage binary no

self complementing code
excess 3 code

	BCD	(242)
0	0011	8421
1	0100	0000
5	1000	0001
6	1001	0101
7	1010	0110
8	1011	0111
9	1100	1000

84-2-1 (weightage) \Rightarrow use Fp. 6(185)10
 $= (1011001)_2$

from reverse check
the upper bound should be above one and those up per bounds which are coming if they will add one to another

(reverse check by using weightage)
 $256, 128, 64, 32, 16, 8, 4, 2, 1$

• self complementing code
excess 3 code

$v = 19$ 0.0213

1's

1's

~~1's~~
~~0~~ $-12 = (2)_{1's}$

$$\begin{array}{r} 12 = 0 \\ - \quad \quad \quad 0 \quad 0 \\ \hline 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \end{array}$$

\downarrow 1's complement

010

1's

+12

~ 12 111100011

0101
simd

1's - 1111001

② $-14 = (?)_{213}$

00010

$$\begin{array}{r} 14 = 0 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 1 \\ - \quad \quad \quad 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \end{array}$$

11111110

$$1's - 11110010$$

$\sim 14 = 11110010$ $-14 = (11110010)_2$

another

(Reverse check using weights)

ASCII character code - 7 bit format

#	$\rightarrow 0100011$	0100001	1010	$\rightarrow 0100011$	$(^81)$
0	$\rightarrow (011) 0000$	\rightarrow			
	$(011) 0001 \rightarrow 1$				
	$(011) 1000 \rightarrow 8$				


No. system

$$\left. \begin{array}{l} (X \text{ AND } Y) = X \cdot Y \\ (X \text{ OR } Y) = X + Y \\ (\text{NOT } Y) = \bar{Y} = Y' \end{array} \right\} \text{Binary operation}$$

x, y binary variable

$x \cdot y$	$x + y$	\bar{y}
0 0	0 0	1
0 1	0 1	0
1 0	1 1	0
1 1	1 1	1


• AND gate

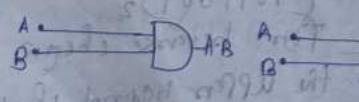


• OR gate




• NOT gate

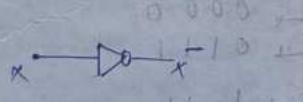

• NAND gate

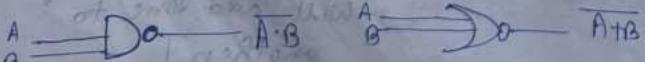

• NOR gate

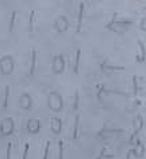

• XOR (exclusive OR) \oplus

• XNOR (exclusive NOR) \ominus

XOR \rightarrow

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

[Even no. of 1 = 0]
[Odd no. of 1 = 1]

XNOR

x	y	$x \odot y$
0	0	1
0	1	0
1	0	0
1	1	1

[Even no. of 1 = 1]
[Odd = 0]

Ques

$$1 \text{ bit} = 2^1 = 2, [0, 1]$$

$$2 \text{ bit} = 2^2 = 4, [00, 01, 10, 11]$$

$$3 \text{ bit} = 2^3 = 8, [000, 001, \dots, 111]$$

$$4 \text{ bit} = 2^4 = 16$$

$$1 \text{ byte} = 2^{10} = 1024 = 1 \text{ KB}$$

$$2 \text{ byte} = 2^{20} = 1048576 = 1 \text{ mega}$$

$$3 \text{ byte} = 2^{30} = 1 \text{ G}$$

$$1 \text{ GB} = 2^{30} \text{ bytes}$$

$$= 2^{30} \times 8 \text{ bit}$$

$$1 \text{ MB} = 2^{23} \text{ bit}$$

4 bit = unsigned $\rightarrow 0-15$ [0000 to 1111]
 (14 active echo)

* Signed magnitude - 0,000 1,111 $\rightarrow -7$
 $1,000 0,111 \rightarrow +7$
 $(+7 \text{ to } -7)$

Signed 1's Comp form - 0000 (+0)
 $(+7 \text{ to } -7)$ 1111 ($\overline{1}^{\text{S}}$)
 [16 combination including +0 and 0]

0000	1000
1111	0111
↓ (-7)	

Signed 2's Comp form -
 [in this we don't have -0] [only 0 is included]
 $(+7 \text{ to } -8)$ 1111 (+1) 1000
 $1000 \rightarrow (-8)$

Formula for signed 2's Comp - $((-2^{n-1}) \text{ to } (2^{n-1} - 1))$

Boolean Algebra


$x, y, 1, 0$, AND, OR, NOT
 $(+) \quad (') / (\bar{ })$

[Binary variable and operations, logic operations]

$$\begin{array}{|c|c|} \hline x & y \\ \hline 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \\ \hline \end{array}$$

AND gate (Binary multiplication)

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

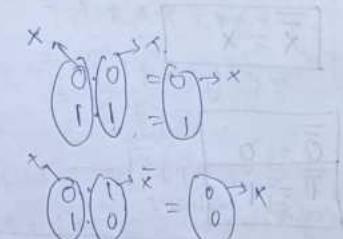

Identity laws

$$\begin{aligned} 0 \cdot x &= 0 \\ 1 \cdot x &= x \\ x \cdot x &= x \\ x \cdot \bar{x} &= 0 \end{aligned}$$

OR gate (Binary addition)

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{array}{|c|c|} \hline x & y \\ \hline 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \\ \hline \end{array}$$

Identity laws

$$\begin{aligned} 0 + x &= x \\ 1 + x &= 1 \\ x + x &= x \\ x + \bar{x} &= 1 \end{aligned}$$

NOT gate

$$\bar{x} = x$$

$$\begin{cases} \bar{0} = 0 \\ \bar{1} = 1 \end{cases}$$

$$x + (y + z) = (x + y) + z \rightarrow \text{Associative Law}$$



$$x \cdot (y \cdot z) = (x \cdot y) \cdot z \rightarrow \text{Commutative Law}$$

[AND gate supports OR gate supports]

$$\begin{cases} x \cdot y + y \cdot x \\ x \cdot y = y \cdot x \end{cases}$$


$$x \cdot (y + z) = x \cdot y + x \cdot z \rightarrow \text{Distributive Law}$$

(OR and AND gate both supports)

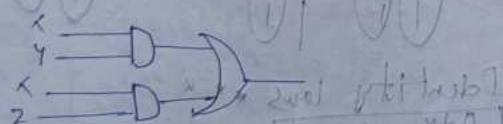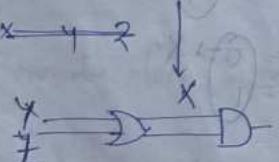

Exclusive law
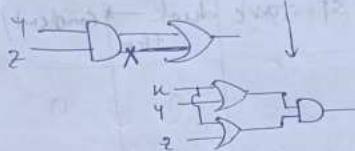
$$x + y \cdot z = (x \cdot \bar{y}) + (\bar{x} \cdot y)$$



$$\begin{aligned} &= x \cdot \bar{y} + \bar{x} \cdot y \\ &= x + x \cdot z + \cancel{x \cdot y} + \cancel{y \cdot z} \\ &= x(1 + z + y) + yz \\ &= x + yz \end{aligned}$$

$$(+) \rightarrow [1+0-0=1] \quad \because \text{Boolean algebra}$$

$$x + (y \cdot z) = (x + y) \cdot (x + z) \rightarrow \text{Exclusive Law}$$

(AND & OR gate both supports)

Duality

$$x \cdot (y + z) = x \cdot y + x \cdot z$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

$$\begin{matrix} \text{AND} & \rightarrow & \text{OR} \\ \text{OR} & \rightarrow & \text{AND} \end{matrix} \rightarrow \text{duality}$$

Operator's Precedence

AND > OR

() > () ! > () > (+)

(.) > () ! > () > (+) x

1st > NOT > AND > OR

Board

Absorption

$$x + (x \cdot y) = x \cdot (1 + y) = x$$

$$x \cdot (x + y) = x + (x \cdot y) = x$$

$$x \cdot (x + y) = x$$

$$\Rightarrow x \cdot x + x \cdot y =$$

$$x \cdot (x + y) = x + x \cdot y ; = x(1 + y) = x$$



De Morgan's theorem / [rule of complement]
 [1st take dual then complement]

$$\begin{aligned} \overline{(x+y)} &= \bar{x} \cdot \bar{y} \\ \overline{(x \cdot y)} &= \bar{x} + \bar{y} \end{aligned}$$

Dual $\rightarrow (+) \leftrightarrow (\cdot)$

Complement $0 \leftrightarrow 1$
 of a fraction
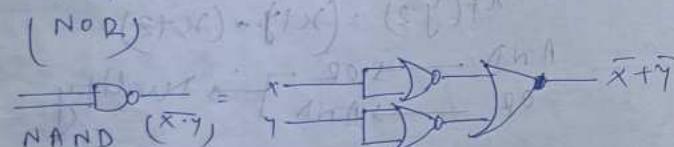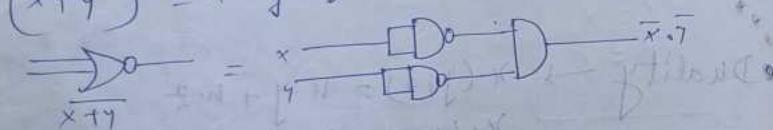
$$\overline{(x+y)} = \bar{x} \cdot \bar{y}$$



$$\overline{(x \cdot y)} = \bar{x} + \bar{y}$$

Prove $(\bar{x} + \bar{y}) = \bar{x} \cdot \bar{y}$ (Truth table)

x	y	$(x+y)$	$(\bar{x}+\bar{y})$	x	\bar{y}	$\bar{x} \cdot \bar{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$$\text{we can see } (\bar{x} + \bar{y}) = \bar{x} \cdot \bar{y}$$

$$x = 1 \cdot 1 \cdot x \\ x = 1 \cdot x \\ x = x$$

Prove $(\bar{x} \cdot \bar{y}) = \bar{x} + \bar{y}$ (Truth table)

x	y	$(x+y)$	$(\bar{x} \cdot \bar{y})$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	1
1	0	1	0	0	1	1
1	1	1	0	0	0	0

$$\text{we can see } (\bar{x} \cdot \bar{y}) = \bar{x} + \bar{y}$$

D.M theorem by function

$$(\bar{x} + \bar{y}) = \bar{x} \cdot \bar{y}$$

F1 \rightarrow F2

$$F_1 = \bar{x} + \bar{y}, \quad F_2 = \bar{x} \cdot \bar{y}$$

Method of evaluation [Referred]

x	y	\bar{x}	\bar{y}	$\bar{x} \cdot \bar{y}$	$\bar{x} + \bar{y}$
0	0	1	1	0	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

$(x + (y \cdot z))$
 AS REA procedure

$$\begin{aligned} &= \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}yz + xy\bar{z} + xy\bar{z} \\ &= \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} \\ &= \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} \end{aligned}$$

$$② F_2 = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + xy\bar{z} + xy\bar{z}$$

$$= \bar{y}(x+\bar{x})$$

x	y	z	$\bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}yz$	$x+y+z$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$= \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z$$

= $\bar{x}\bar{y}(2+\bar{z})$ [Shorthand calculation]

$$= \bar{x}\bar{y} \cdot 1$$

$$= \bar{x}\bar{y}$$

other process

$$F_2 = \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}y$$

$$= \bar{x}z(\bar{y}+y) + \bar{x}y$$

$$= \bar{x}z + \bar{x}y$$

$$= \bar{x}z + \bar{x}y$$

Reduction
X literal
here 8 literal
reduced in 4

(Production)

Hence Production
reduced in 2

Reduction \rightarrow Literal
 \rightarrow Production

$$\text{Q.E.D.} \quad ① x(x+y) = xy$$

$$② x + \bar{x}y = x+y$$

$$\Rightarrow (x+\bar{x})(x+y) = x+y \quad [\because x+\bar{x} = (x+y)(x+y)]$$

$$③ (x+y)(x+y) = x+x+y + xy \quad \text{[Q.E.D.]}$$

$$= x + xy$$

$$= x(1+y)$$

$$④ x^2 + x^1z + yz = x((x^2 + x^1z) + yz)$$

$$= x^2 + yz$$

$$= y(x+z)$$

$$= x^2 + yz$$

$$= x^2 + x^1z + x^1z + yz$$

$$= x^2(1+y) + x^1z(1+y)$$

$$= x^1z + xy$$

$$⑤ (x+y) \cdot (x^1+z) \cdot (y+z) = (x^1+z) \cdot (x+y)$$

$$\Rightarrow [(x^1+z)(y+z)](x+y)$$

$$= x^1yz + x^1y^2 + yz + x^1z^2 + x^1yz + yz$$

$$= x^1z^2 + yz + x^1z + x^1y$$

$$= YZ(1+x) + xz + x'y \\ = YZ + xz + x'y \quad (\text{by } 1)$$


$$(x' + z)(x + y) \quad (\text{PITS}) \\ = xz + yx' + yz$$

$2+3 = \text{PITS}$ (PMD).

* Complement of a function

$$(A + B + C)' = (A + x)' \quad [\text{if } B + C = x]$$

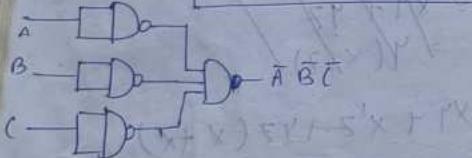
$$\begin{aligned} &= A' \cdot x' \\ &= A' \cdot (B + C)' \\ &\downarrow \\ &[(A + B + C)' = A' \cdot (B' \cdot C')] \end{aligned}$$



$$(A + B + C + D)' = A' B' C' D'$$

$$A'BC = \overline{A} + \overline{B}\overline{C} \quad [\text{if } BC = x]$$
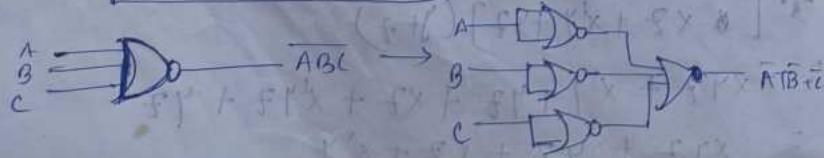
$$\begin{aligned} &= \overline{A} + \overline{B}\overline{C} \\ &\boxed{\overline{A}BC \rightarrow \overline{A} + \overline{B}\overline{C}} \end{aligned}$$



$$F_1 = x'y'z' + x'y'z$$

$$F_1' = (x'y'z' + x'y'z)^1$$

$$= x'(yz)$$

$$= [x'y'z(x+y)]' = \overline{x'y'z} \cdot \overline{x+y} \quad [\bar{A} \cdot \bar{B}] \\ = (x+y)' = (x+y+z) \cdot (x+y+z')$$

$$A' = (x'y'z')' = (x' + y + z)$$

Similarly

$$B' = (x'y'z)^1 = x+y+z$$

$$F_1 = [(x'y'z') + (x'y'z)]$$

in one step

$$= (x+y+z)[(x+y+z) \cdot (x+y+z')]$$

$$F_2 = x(y'z' + yz)$$

$$= x'y'z' + xyz$$

$$F_2' = [(\overline{x'y'z'}) + (\overline{xyz})]$$

$$= (x+y+z) \cdot (x'+y'+z')$$

$$= x'y'z' + yz$$

$$= x'y'z' + x'y'z + x'yz + xy'z + xyz$$

$$= x'(y'z' + yz) + yz + y'z \\ = x'(y'z' + yz) + yz = x'y'z + yz$$

a function

$$A+x) \cdot (B+x)$$

$A+x)^1$: F1, then

$$\begin{matrix} A^1 \cdot x^1 \\ A^1 \cdot (B^1) \end{matrix}$$

others

Process

$$F_2 = x(y^1 z^1 + y^2)$$

$$F_2^1 = [x(y^1 z^1 + y^2)]'$$

$$= x^1 + (y^1 z^1 + y^2)'$$

$$= x^1 + (y^1 z^1) \cdot (y^1 + z^1)$$

$$= x^1 + y^1 z^1 + z^1 y^1$$

in one step, $[x(y^1 z^1 + y^2)]' = x^1 + (y^1 z^1) \cdot (y^1 + z^1)$

$$= x^1 + y^1 z^1 + z^1 y^1$$

$$(x^1 + y^1 + z^1) \cdot (x^1 + y^1 + z^1)$$

$$\begin{array}{l} x \cdot 0 = 0 \\ \bar{x} + 1 = 1 \end{array}$$

↓
identity

Pr min term

x	y	z	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	0	1	2	3	4	5	6	7
0	0	1	0	1	2	3	4	5	6	7
0	1	0	0	0	1	2	3	4	5	6
0	1	1	0	0	1	2	3	4	5	6
1	0	0	1	0	1	2	3	4	5	6
1	0	1	1	0	1	2	3	4	5	6
1	1	0	1	1	0	2	3	4	5	6
1	1	1	1	1	1	0	1	2	3	4

Base = 1
Dased(') = 0

Fun can be represented in sum of min term

$$F = \sum m_i = \sum_m (0, 2, 4, 6)$$

(Any combination)
↓
this min terms are in the F function

Im

max term = complement of min term

max term

$$\begin{array}{l} M_0 = \bar{m}_0 = (x^0 y^0 z^0) = m_4 = \bar{m}_4 = x^1 y^1 z^1 \\ M_1 = \bar{m}_1 = (x^0 y^0 z^1) = m_5 = \bar{m}_5 = x^1 y^1 z^0 \\ M_2 = \bar{m}_2 = (x^0 y^1 z^0) = m_6 = \bar{m}_6 = x^1 y^0 z^1 \\ M_3 = \bar{m}_3 = (x^0 y^1 z^1) = m_7 = \bar{m}_7 = x^1 y^0 z^0 \end{array}$$

base = 0
dased = 1

max prime = If prime then 1

$$\prod_M (1, 3, 5, 7)$$

Fun can be represented in product of max term.

x	y	z	F	G
0	0	0	1	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

Sum \leftrightarrow POM
P & F \rightarrow G

$$F = G, \text{ when } F = \sum m(0, 2, 4, 6)$$

$$G_1 = \prod_M (1, 3, 5, 7)$$

$$F = \bar{G}, \text{ when } F = \sum m(0, 2, 4, 6)$$

$$G_2 = \prod_M (0, 1, 5, 6)$$

$$F = \bar{G}$$

IF same index

$$G_1 = \prod_M (0, 2, 4, 6)$$

$$F = \sum m(0, 2, 4, 6)$$

$$G_2 = \prod_M (1, 3, 5, 7)$$

$$F = \bar{G}$$

$$F = \sum_m (1, 2, 3, 4)$$

$$\bar{F} = \prod_M (1, 2, 3, 4)$$

If we keep \prod_M and exclude $(1, 2, 3, 4)$ then

$$\bar{F} = F = \prod_M (0, 1, 5, 6, 7)$$

How to convert Sum \leftrightarrow POM

max term.

x	y	z	F_b	\bar{F}_b
0	0	0	1	0
1	0	0	0	1

m_0 [min term 0]

m_1 [min term 0]

m_2 [0, 1, 2]

m_3 if for

m_5

m_6

m_7

$$F = \bar{F} \text{ when } \bar{F} = \sum_m (1, 2, 3, 4)$$

$$F = F[\bar{F}] \text{ when } F = \sum_m (1, 2, 3, 4)$$

$$F = \prod_m (0, 5, 6, 7)$$

ex

→ 4) b)

→ 4) b)

→ 4) b)

→ 4) b)

$$F = \sum_m (1, 2, 3, 4) \quad \text{① find } \bar{F} = F^I, F^I = \prod_m (1, 2, 3, 4)$$

$$\bar{F} = \prod_m (1, 2, 3, 4) \quad \text{② find } F = F^I, F^I = \prod_m (0, 5, 6, 7)$$

$$\therefore \bar{F} = \prod_m (1, 2, 3, 4)$$

$$\bar{F}(F) = \prod_m (0, 5, 6, 7)$$

$$\therefore \text{If } \bar{F} \text{ given, } F = ? \text{ then, } \bar{F} = \prod_m (1, 2, 3, 4)$$

$$\text{F} = \sum_m (1, 2, 3, 4) \quad \text{[Result in S]}$$

$$\text{③ } \bar{F} = F^I = \prod_m (0, 5, 6, 7) \quad \text{[Result in P]}$$

$$\therefore \bar{F} = F^I = \prod_m (0, 5, 6, 7) \quad \text{then}$$

element of

∴

$$m_4 = 3y$$

$$m_5 = 2x + 2y + 2z$$

$$\bar{F} = F^I = \prod_m (0, 5, 6, 7)$$

$$\begin{aligned} m &= \sum_m (1, 3, 5) \\ G_1 &= \sum_m (1, 2, 5) \\ \bar{G}_1 &= \sum_m (0, 2, 4, 6, 7) \end{aligned}$$

Pom \rightarrow Som

$\rightarrow [Sop \rightarrow Som]$

$$① F = A + \bar{B}C \quad [\text{Sum of Product term}] / [Som]$$

$$F = \sum_m (1, 4, 5, 6, 7) \rightarrow \text{Som} = m_1 + m_4 + m_5 + m_6 + m_7$$

$$F = \sum_m (0, 2, 3) \rightarrow \text{Pom} = m_0, m_2, m_3$$

$$\begin{aligned} F(A, B, C) &= A(B\bar{C}) + (\bar{C}C) + \bar{B}C(A + \bar{A}) \\ &= A[B\bar{C} + B\bar{C} + \bar{B}C + \bar{B}\bar{C}] + \\ &\quad \bar{B}C[A + \bar{A}] \\ &= ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \\ &\quad A\bar{B}C + A\bar{B}\bar{C} \end{aligned}$$

$$= m_7 + m_6 + m_5 + m_4 + m_3 = 9$$

$\rightarrow [Sop \rightarrow Pom]$

$$② F = xy + xz \quad [\text{Sum of max terms}] / [Som] / [Pom]$$

$$F(x+y+z) = xy(z+z') + xz(y+y') =$$

$$= xyz + xyz' + xzy + x'yz$$

$\rightarrow [Pom \rightarrow Som]$

$$\begin{aligned} & (xy+x') + (xy+z) \quad [\text{Applying distributive law}] \\ &= (x'y) + (x'z) + (y+z)(y+z') \\ &= (x'y + z + z') + (x'z + y + z') + (y + z)(y + z') \end{aligned}$$

$$= (x'y + y + z)(x'z + z + z') + (y + z)(y + z')$$

$$= m_0 M_4, M_5, M_2, M_3$$

Sum of min term (Som)

2/8/22

$$f(x, y) = \sum_m (1, 2, 3) = \text{OR gate } m_1 + m_2 + m_3$$

$$x = y \quad f(x, y) = 01$$

$m_0 = \bar{x}\bar{y}$	00	0	[Present=0]
$m_1 = \bar{x}y$	01	1	[Present=1]
$m_2 = xy$	10	1	[Present=1]
$m_3 = x\bar{y}$	11	1	[Present=1]

Product of max term (Pom)

$$F(x, y) = \prod_m (0, 3) = m_0, m_3$$

$$F = \bar{F} = \sum_m (1, 2)$$

$(x, y) = 00$	0	[Present=0]	
$(x, y) = 01$	1		
$(x, y) = 10$	1		
$(x, y) = 11$	0	[XOR gate]	

• Canonical form \rightarrow Som
Pom

• Sop (Sum of Product) \rightarrow standard form
pos (Product of sum)

$$\begin{aligned} F &= (x'y)(x'z)(y'z) \\ &= (x'y + z)(x'z + y)(y'z + x) \\ &= (x'y + z)(x'z + y)(y'z + x)(y'z + x) \\ &= (x'y + z)(x'z + y)(y'z + x)(y'z + x) \\ &= (x'y + z)(x'z + y)(y'z + x)(y'z + x) \end{aligned}$$

$$G = M_m(1, 3, 5)$$

Since the procedure to get

SOP \rightarrow SOM and POS \rightarrow POM is same
different. So, if the m is

SOP \rightarrow POM, the intermediate
step will be
SOM

A similarly -

If POS \rightarrow SOM, the intermediate
step will be POM

④ If you want to directly get

SOP \rightarrow POM, then convert the
given function into that form by
which you can directly get POM,
with the help of exclusive law.

Similarly \rightarrow If you want to directly

get POS \rightarrow SOM, then convert the
given func into that form by which
you can directly get SOM, with the
help of reverse of exclusive law

$$[S.F. - (xy + x').(xy + z) = xy + x'z]$$

$$= (x' + y + z)(x' + y + z') \cdot (x + y + z)(x + y + z')$$

$$P = xy + x'z$$

$$= (x.y + x.z) \cdot (x.y + z)$$

$$= (x + z)(y + z)(x + z)(y + z)$$

$$= 1 \cdot (x + y)(x + z)(y + z)$$

$$= (x' + y' + z' + z)(x + y + z)(x + y + z)$$

$$= (x' + y' + z)(x + y + z)(x + y + z)$$

$$(x + y + z)(x + y + z)$$

$$= (x' + y' + z)(x' + y' + z)(x + y + z)$$

$$= M_6 M_7 M_0 M_4 M_2$$

$$= (x' + y + z)(x' + y + z)(x + y + z)(x + y + z)$$

$$= M_4 M_5 M_0 M_2$$

using 2 variable how many func we can represent
(in form of sum)

m_0	x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}/F_{11}
(x,y)	0	0	0	0	0	0	0	0	0	1	1	1	
(x,y)	0	1	0	0	0	0	1	1	1	0	0	0	
(x,y)	1	0	0	1	1	0	0	1	1	0	0	1	
(x,y)	1	1	0	1	0	1	0	1	0	1	0	1	

$m_0 \rightarrow 2$ [absent/present $\rightarrow 2$ combination] \times

$m_1 \rightarrow 2$ (most from 0 to low bcd)

$m_2 \rightarrow 2$ $E = m_0 \cdot m_1 \cdot m_2 = (1 \cdot 0 \cdot 1) = 1$

$m_3 \rightarrow 2$ $E = m_0 \cdot m_1 \cdot m_2 \cdot m_3 = (1 \cdot 0 \cdot 1 \cdot 1) = 1 = 7 = 1$

$$2^4 = 16$$

$$F_0 = 0 = \text{Ground}$$

$$F_1 = x \cdot y = \text{AND}$$

$$F_2 = x \cdot y' = x \cdot \bar{y}$$

$$F_3 = x \cdot y + x \cdot y' = x$$

$$F_4 = x \cdot y' = x \cdot \bar{y}$$

$$F_5 = x \cdot y + x \cdot y = y$$

$$F_6 = (x \cdot y + x \cdot y') = x \cdot (\bar{y} + y) = x \cdot 1 = x$$

$$F_7 = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

$$F_8 = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

$$F_8 = x \cdot y' = \bar{x} \cdot y = \text{NOT gate}$$

$$F_9 = x \cdot y' + x \cdot y = x \cdot (\bar{y} + y) = x \cdot 1 = x$$

$$F_{10} = x \cdot y' + x \cdot y' = x \cdot y' = \bar{x} \cdot y = \text{NOT gate}$$

$$F_{11} = x \cdot y' + x \cdot y + x \cdot y = y + x \cdot y$$

$$(m_0 \oplus m_1 \oplus m_2 \oplus m_3) = 1 = 9$$

$$\text{if } y = 1, F_{11} = \bar{x} \cdot \bar{y} = \bar{x} = x$$

$$(\text{Inhibit}) \quad \text{If } y \text{ is true then } F_{11} = x$$

$$F_{12} = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

$$F_{13} = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

$$F_{14} = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

$$F_{15} = x \cdot y + (x \cdot y' + x \cdot y) = x \cdot y + x = x$$

F_{12}	F_{13}	F_{14}	F_{15}
1	1	1	1
1	1	1	1
0	0	1	1
0	1	0	1

7 basic gates are present

Supply (all one) / VDD = VCC

greater than
less than
Special

4 Special are present

$$F_{12} = x \cdot y' + x \cdot y$$

$$= x' = \text{NOT gate}$$

$$F_{13} = x \cdot y' + x \cdot y + x \cdot y$$

$$= x' + x \cdot y$$

$$= x' + y$$

$$= \frac{x \cdot y'}{x \cdot y} = \bar{y} = y$$

If n is true (that means $n=1$) then y is true
(Implementation)

$$F_{14} = x \cdot y + x \cdot y' + x \cdot y$$

$$= x' + x \cdot y'$$

$$= x \cdot y'$$

$$= \frac{x \cdot y}{x \cdot y} = \text{NAND gate}$$

$$F_{15} = 1 = \text{Supply}$$

$$[x \cdot y' + x \cdot y' + x \cdot y + x \cdot y]$$


$$= y' + y = 1$$

1) NAND	universal gate	7400
2) NOR		7402
3) NOT		7402
4) AND	Basic gate	7408
5) OR		7432
6) XOR		7486
7) XNOR		747266

- ① NAND gate (what is NAND gate)
- ② symbol
 - ③ IC (what)
 - ④ Boolean expression (what)
 - ⑤ Truth table (what)
 - ⑥ verification table (on/off) (what)

what to do in lab report

All NAND gate has the direction →

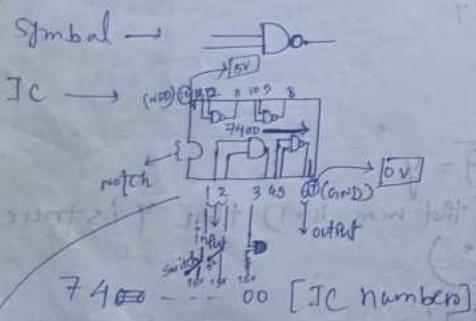

NAND IC (7400)

SW1	SW2	led
off	off	on
off	on	on
on	off	on
on	on	off


specification table

II

SW1	SW2	led
0	0	1
0	1	1
1	0	1
1	1	0

Step 10

NOR gate

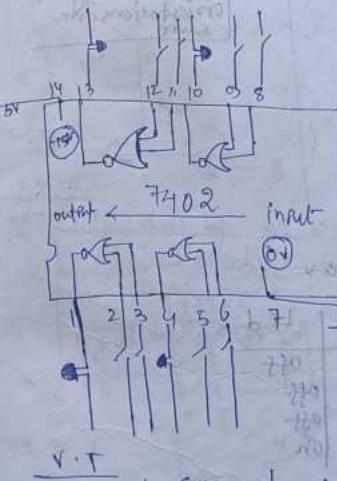

V.T


SW1	SW2	led
off	off	on
off	on	off
on	off	off
on	on	off

II

SW1	SW2	led
0	0	1
0	1	0
1	0	0
1	1	0


Step 10

NOT gate

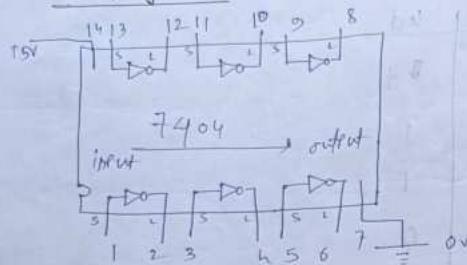


n	x1	V-T
0	1	sw1 red
1	0	sw1 off sw2 on

AND gate

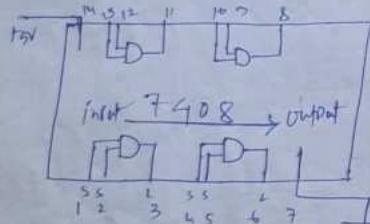


n	y	V-T
0	0	0
0	1	off
1	0	on
1	1	on

OR gate

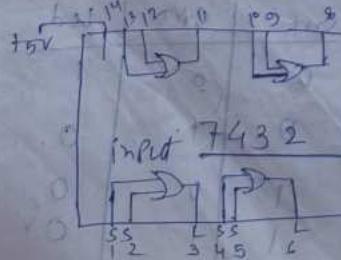

XOR

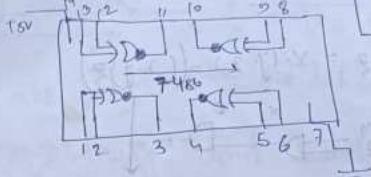


on	off	on
on	on	on
off	off	off




T-T

n	y	V-T
0	0	0
0	1	off
1	0	on
1	1	on

n	y	V-T
off	off	off
off	on	on
on	off	on
on	on	off

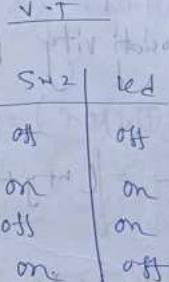

XNOR

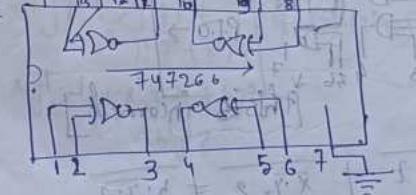

T-T

n	y	V-T
0	1	1
0	0	off
1	0	on
1	1	on





n	y	V-T
off	off	on
off	on	off
on	off	off
on	on	on







16/8/22

class

3 input gates

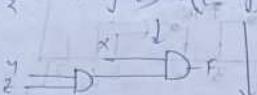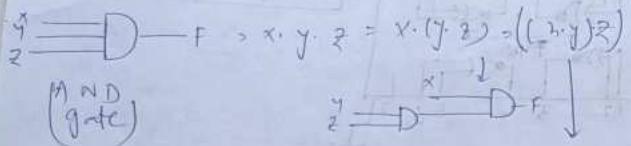

[Associativity holds]

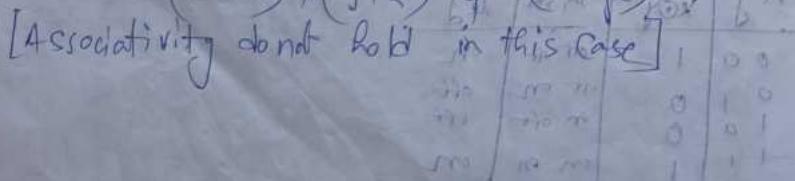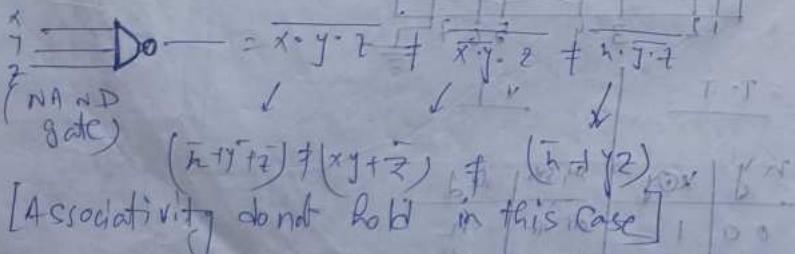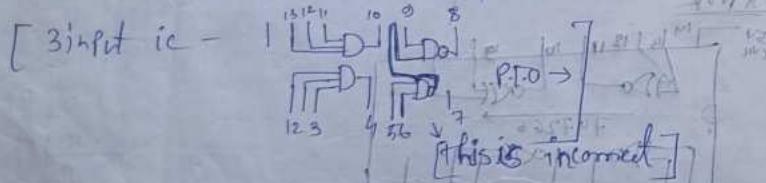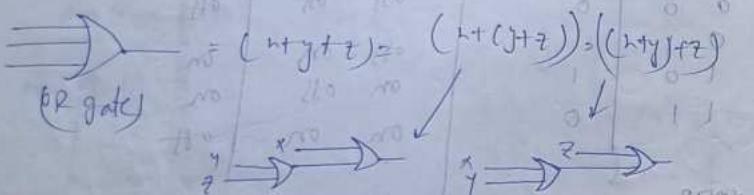

[Associativity does not hold in this case]

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \\ \text{---} \end{array} \text{---} \text{---} \text{---} \text{---} \text{---} \text{---}$$

$$F = x + y + z = \overbrace{(x + y)}^{\downarrow} + \overbrace{z}^{\downarrow} = \overbrace{(x + y)}^{\downarrow} + \overbrace{z}^{\downarrow}$$

(NOR gate)

[Associativity does not hold]

[NOT gate don't have any multiple input]

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \\ \text{---} \end{array} \text{---} \text{---} \text{---} \text{---} \text{---} \text{---}$$

$$F = x \oplus y \oplus z = (x \oplus (y \oplus z)) = ((x \oplus y) \oplus z)$$

(XOR gate)

[Associativity holds]

$$\begin{aligned} & n \oplus (y'z + yz') = (x \oplus (y \oplus z)) = ((x \oplus y) \oplus z) \\ & n(yz + y'z') + (x \oplus y \oplus z) \\ & = nyz + xy'z + x'y'z' + x'y'z + yz' \\ & = nyz + x'y'z + yz' \\ & = (ny + x'y)z + yz' \end{aligned}$$

$$\begin{aligned} & x \oplus y \oplus z = (x \oplus y) \oplus z = x'y'z + x'yz' + (xy + yz) \\ & = x'y'z + x'yz' + xy + yz \\ & = x'y'z + x'yz' + xy + yz \\ & = x'y'z + x'yz' + xy + yz \end{aligned}$$

$$\begin{aligned} & x \oplus y \oplus z = (x \oplus y) \oplus z = x'y'z + x'yz' + (xy + yz) \\ & \text{between the previous two process, can follow} \\ & \text{one process to get } x \oplus y \oplus z \end{aligned}$$

$$\begin{array}{c} \text{Inputs: } x, y \\ \text{Output: } F = \overline{x} \odot y \oplus x \odot \overline{y} \\ = \overline{x} \odot y + x \odot \overline{y} \\ = (\overline{x} \odot y) \oplus (\overline{x} \odot y) \end{array}$$

[Associativity of \oplus holds]

$\overline{x} \odot y \oplus x \odot \overline{y}$

$$\begin{aligned} &= x \odot (\overline{y} + y' \overline{z}) \\ &= x(\overline{y} + y' \overline{z}) + x'(y \overline{z} + y' \overline{z}') \\ &= \overline{y} z + \overline{y} y' \overline{z} + x' [(\overline{y} z)' \cdot (y' \overline{z}')]' \\ &= \overline{y} z + \overline{y} y' \overline{z} + x' [(\overline{y} + z') \cdot (y + z)] \\ &= \overline{y} z + \overline{y} y' \overline{z} + x' [\overline{y} + z] \\ &= \overline{y} z + \overline{y} y' \overline{z} + x' \overline{y} + x' z \\ &= (\overline{y} \odot z) \oplus x' \overline{y} \end{aligned}$$

$\overline{y} \odot z$

$\overline{y} z + \overline{y}' y' z$

$= (\overline{y} z + \overline{y}' y' z) + (\overline{y} z + x' y' z)$

$$= \overline{y} z + \overline{y}' y' z + [\overline{y} z]' \cdot [\overline{y}' y' z]' \cdot z / m (\overline{y} z + \overline{y}' y' z)$$

$= \overline{y} z + \overline{y}' y' z + [(\overline{y} z)' \cdot (\overline{y}' y' z)'] z'$

$= \overline{y} z + \overline{y}' y' z + [\overline{y}' y + \overline{y} z] z'$

$= \overline{y} z + \overline{y}' y' z + \overline{y}' y z + \overline{y} z$ [Proved]

$$\begin{aligned} &= \overline{y} z + \overline{y}' y' z + \overline{y}' y z + \overline{y} z \\ &= \overline{y} z + \overline{y}' y' z + \overline{y}' y z + \overline{y} z + \overline{y}' y z \end{aligned}$$

$\overline{y} \odot z = \overline{y} z + \overline{y}' y' z + \overline{y}' y z + \overline{y} z$

$$\begin{array}{l} \overline{x} \odot y = xy + x'y' \\ \overline{x} \odot y = \overline{x} \odot y \oplus \overline{x} \odot y \\ \text{Complement of } x \oplus y \\ \text{Complement of } x \oplus y \\ = x \oplus y \end{array}$$

$$1 \cdot 1 \cdot 1 = 1 \quad [\text{Identity of AND gate}]$$

$$0 + 0 + 0 = 0 \quad [\text{Identity of OR gate}]$$

$$\overline{1} \cdot \overline{1} \cdot \overline{1} = \overline{1} = 0 \quad [\text{Identity of NAND gate}]$$

$$\overline{0} + \overline{0} + \overline{0} = \overline{0} = 1 \quad [\text{Identity of NOR gate}]$$

x	y	z	XOR	XNOR
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

Universal gate

① NAND

② NOR



AND

OR

NOT

XOR


XNOR

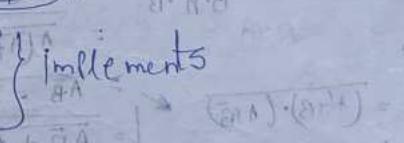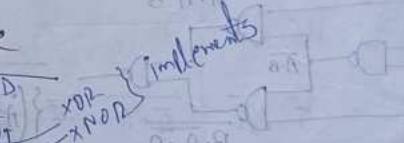


NOT gate implementation using NAND gate -

$$\begin{array}{ccc} A & \xrightarrow{\text{NAND}} & F = \overline{A} \cdot \overline{A} = \overline{A} \end{array}$$


* NAND \rightarrow AND

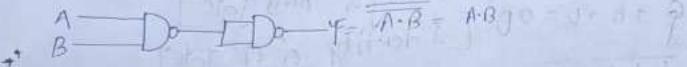


* NAND \rightarrow OR

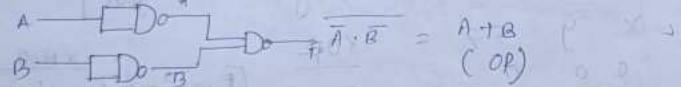

* NAND \rightarrow NOR

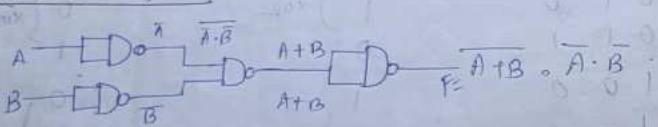


* NAND \rightarrow XOR

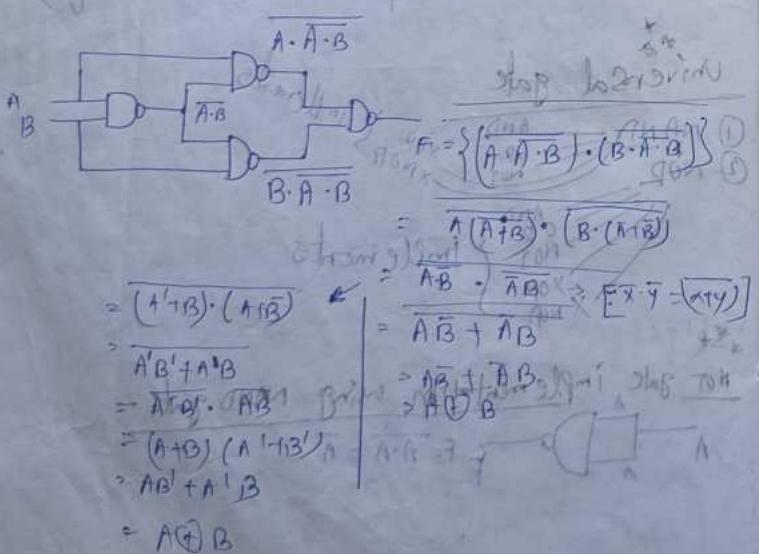

* NAND \rightarrow XNOR




* NOR \rightarrow OR

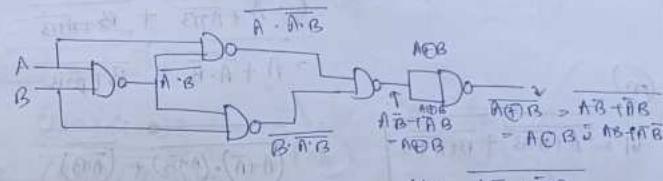


$$\begin{aligned} Y &= \overline{A \cdot \overline{B}} \\ &= (\overline{A} \cdot \overline{\overline{B}}) \cdot (\overline{A} \cdot B) \\ &= (\overline{A} + B) \cdot (\overline{A} + B) \\ &= \overline{A} \cdot B = A \oplus B \end{aligned}$$


* NOR \rightarrow AND

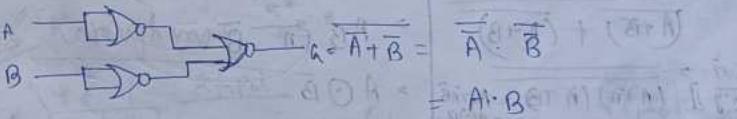

* NOR \rightarrow NAND

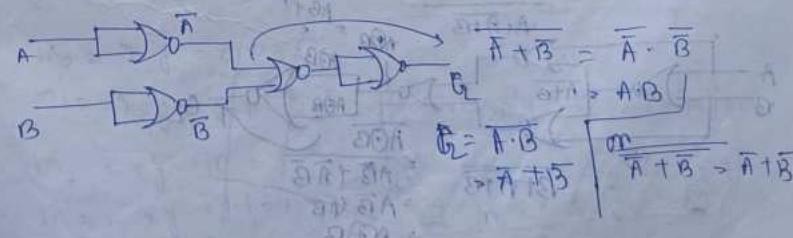

\rightarrow NOR \rightarrow SOP

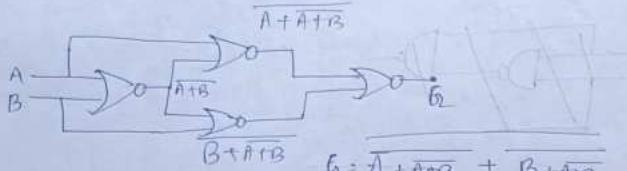


$$\begin{aligned} G_1 &= \overline{A + A'B} + \overline{B + A'B} \\ &= \overline{A} (\overline{A} + B) + \overline{B} (\overline{A} + B) \\ &= (\overline{A} \cdot \overline{A}) + (\overline{A} \cdot B) + (\overline{B} \cdot \overline{A}) + (\overline{B} \cdot B) \\ &= (\overline{A} \cdot B) + (\overline{B} \cdot \overline{A}) \end{aligned}$$

$$\begin{aligned} G_1 &= (\overline{A} \cdot B) + (\overline{B} \cdot \overline{A}) \\ &= (\overline{A} \cdot B) \cdot (\overline{A} \cdot \overline{B}) + (\overline{B} \cdot \overline{A}) \cdot (\overline{A} \cdot \overline{B}) \\ &= (\overline{A} + \overline{B}) \cdot (\overline{A} \cdot \overline{B}) \end{aligned}$$

$$\begin{aligned} &> AB + \overline{A} \cdot \overline{B} \\ &> A \oplus B \end{aligned}$$

NOP \rightarrow XOP

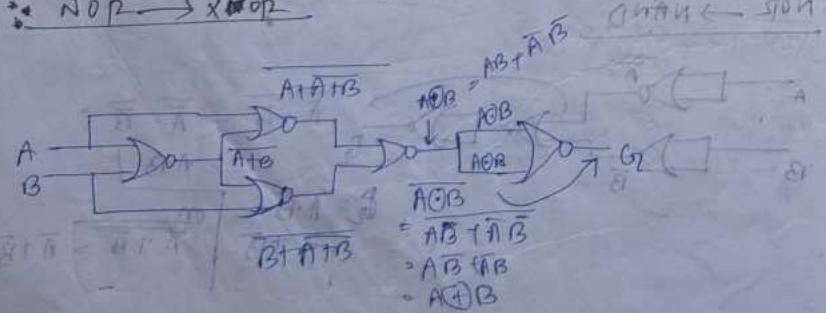

$$\begin{aligned} &A' + A \bar{B} \\ &= \overline{A} + \overline{A} \cdot \overline{B} \\ &= \overline{A} + \overline{A} \cdot \overline{B} \\ &= \overline{A} \cdot \overline{B} + \overline{A} \\ &= A \oplus B \end{aligned}$$

2 level function using NAND gate


$$F = \frac{AB + CD}{(\overline{AB} + \overline{CD})} \quad (\text{SOP})$$

$$\begin{aligned} &\frac{AB \cdot CD}{(\overline{AB} \cdot \overline{CD})} \\ &\quad (\text{By NAND gate}) \end{aligned}$$

$$\begin{array}{c} A \\ B \end{array} \rightarrow \begin{array}{c} D \\ C \end{array} \rightarrow F$$

$$G_2 = \frac{(A+B)(C+D)}{(A+B)(C+D)} E \quad (\text{POS})$$
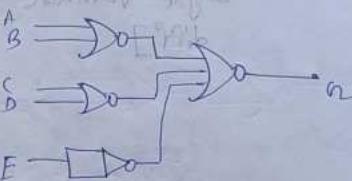
$$= \overline{A} \cdot \overline{B} + \overline{C} \cdot \overline{D} + F$$



Karnaugh map

		\bar{y}_1	y_1	2 input	
		0	1	m_0	m_1
		0	1	0	1
x_1	0	m_0	m_1		
x_1	1	m_2	m_3		

\bar{x}_1	\bar{y}_1	0	1
0	0	m_0	m_1
1	0	m_2	m_3

\bar{x}_1	\bar{y}_1	0	1	0	1	0	1
0	0	1	0	1	0	0	1
0	1	0	1	0	1	1	0
1	0	0	1	1	0	1	0
1	1	1	1	1	1	0	0

verify the position

3 input

	yz	0	1
0	00	m ₀	m ₁
1	01	m ₃	m ₂

	yz	00	01	10	11
x = 0	00	m ₀	m ₁	m ₃	m ₂
x = 1	01	m ₅	m ₇	m ₆	m ₄

$$m_0 = \bar{x} \cdot \bar{y} \cdot \bar{z}$$

$$m_3 = \bar{x} \cdot y \cdot z$$

$$m_2 = x \cdot y \cdot \bar{z}$$

$$m_4 = x \cdot \bar{y} \cdot \bar{z}$$

$$m_6 = x \cdot y \cdot \bar{z}$$

4 input

	yz	00	01	11	10	B.C.D
AB	00	m ₀	m ₁	m ₃	m ₂	MSD
CD	00	m ₄	m ₅	m ₇	m ₆	D2 LSD
A	00	m ₁₂	m ₁₃	m ₁₅	m ₁₄	row = AB
B	00	m ₈	m ₉	m ₁₁	m ₁₀	Column = CD

[All units contains single variable diff]

step function given without bool S
msd = x

$$m_{15} = A \cdot B \cdot C \cdot D$$


$$m_8 = A \cdot B \cdot \bar{C} \cdot \bar{D}$$

$$m_{11} = A \cdot \bar{B} \cdot C \cdot D$$

$$m_{12} = A \cdot B \cdot \bar{C} \cdot D$$



[3 input IC \rightarrow]

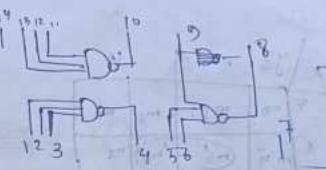

23/8/22

(2) $\star \star$

	yz	00	01
x	00	m ₀	m ₃
y	01	m ₅	m ₂

	yz	00	01
x	00	m ₁	m ₃
y	01	m ₂	m ₄

$$F = m_3 = \bar{x} \cdot y \text{ (AND)}$$

$$F(h,y) = \sum_m (1,2,3)$$

$$(constant term) \bar{h}y + h\bar{y} + (wy + \bar{w}\bar{y})$$

$$y(\bar{w} + \bar{x}) + x(w + \bar{y}) \\ \text{or gate } (\bar{y} + x)$$

(n) of terms


n=10

	yz	00	01
x	00	1	0
y	01	0	1

$$\bar{y} + \bar{z} = 1$$

$$z + \bar{z} = 1$$

$$\bar{z} + z = 1$$

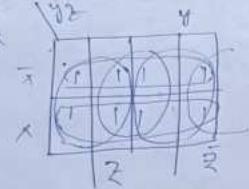


x	y2	y	
\bar{x}	m0	m1	m3
x	m4	$m_5 = \bar{m}_6$	m6
	\bar{z}	z	\bar{z}


$$\begin{aligned}
 F_1 &= \sum_m (5, 7) \quad [\text{Product of min terms}] \\
 &= \bar{x} \cdot \bar{z} (\bar{y} + y) \quad [\text{those are common}] \\
 &= \bar{y}z + x\bar{y}z \\
 &= xz(\bar{y} + y)
 \end{aligned}$$

(collection of adjacent minterms)

$$F_2(x, y, z) = \sum_m (2, 3, 4, 5)$$

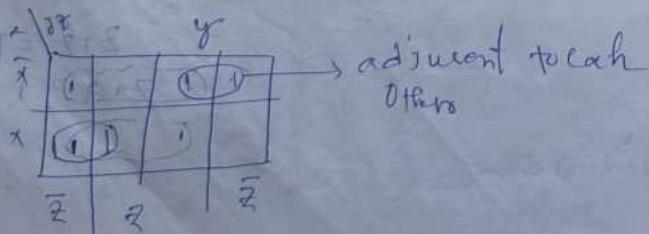
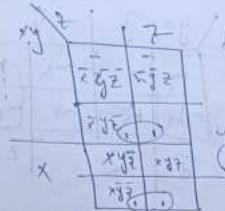
$$\begin{aligned}
 &= \bar{y}z + x\bar{y} \\
 &= \bar{x} \oplus y
 \end{aligned}$$



$$\begin{aligned}
 &= \bar{y} + x\bar{y} \\
 &= \bar{x} \oplus y
 \end{aligned}$$

$$F_2 = \sum_m (0, 2)$$


$$= \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} \quad (\text{common})$$

$$F_3 = \sum_m (4, 6)$$

$$= x\bar{z} \quad (\text{common})$$


$$F_4 = \sum_m (3, 4, 6, 7)$$

$$= y\bar{z} + x\bar{z}$$

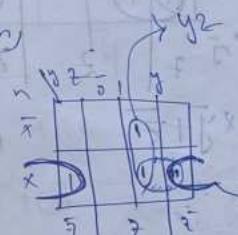

No overlapping
minimum collection
will find the
bigger non
overlapping
collection.

$$F_4(x, y, z) = \sum_m (0, 2, 4, 6)$$

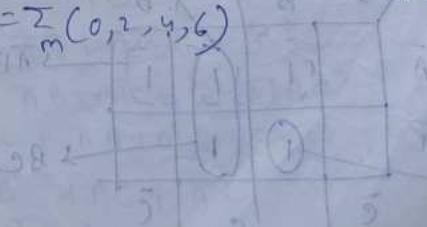

	$y_2 \bar{y}_1$	$\bar{y}_2 \bar{y}_1$	$y_2 \bar{y}_1 \bar{y}_0$	$\bar{y}_2 \bar{y}_1 \bar{y}_0$
x	m_0	m_1	m_3	m_2
\bar{x}	m_4	m_5	m_7	m_6
	\bar{z}	z	\bar{z}	z

$$= \bar{z} (x + \bar{x})(y_2 \bar{y}_1)$$

$$F = \sum_m (0, 2, 4, 5, 6)$$

	y_2	y_1	y_0	\bar{y}_2	\bar{y}_1	\bar{y}_0
x	1	1	1	1	1	1
\bar{x}	1	1	0	1	1	0
y_2	1	0	1	1	0	1
\bar{y}_2	0	1	1	0	1	1
y_1	1	1	0	0	0	1
\bar{y}_1	0	0	1	1	1	0
y_0	1	0	1	1	0	0
\bar{y}_0	0	1	0	0	1	1

$$= x\bar{y}_1 + \bar{z}$$

[y_2, \bar{y}_1 both present
that's why minimized]

$$\therefore F = \bar{A}C + \bar{A}B + A\bar{B}C + BC$$

What is sum of the four min term, minimal SOP?

$$F(A, B, C) = \sum_m (?)$$

	B	C	\bar{B}	\bar{C}
A	1	1	1	1
\bar{A}	1	0	0	1
	0	1	1	0

$$[y_2 \bar{y}_1 / z, \bar{z} / x, \bar{z}]$$

both present = minimized

$$F(A, B, C) = \sum_m (1, 2, 3, 5, 7)$$

minimal Sum of Product (non overlapping
figure calculation)

a	B	B	\bar{B}
\bar{a}	1	1	1
a	1	1	0
\bar{a}	0	0	1

1	1	1
0	1	1

overlapping minimality's formula
 $2^n = 1, 2, 4, 8, 16, \dots$

minimal SOP = $\bar{A}B + C$

$$F = \bar{A}BC + \bar{A}B + A\bar{B}C + BC$$

$$= \bar{A}C(\bar{B} + B) + \bar{A}(B\bar{C})$$

$$= \bar{A}B + \bar{A}C + C$$

$$= \bar{A}B + C(\bar{A} + 1)$$

$$= \bar{A}B + C$$

(*) \checkmark $\bar{A}C + \bar{A}B + A\bar{B}C + BC$

$$= \bar{A}C \bar{A}B + \bar{A}B + (\bar{A} + \bar{A})BC$$

$$= \bar{A}C + \bar{A}B + \bar{A}B + \bar{A}BC$$

$$= \bar{A}B + \bar{A}C + \bar{A}C$$

$$= \bar{A}B + C$$

$$F(x,y,z) = \sum m(0,2,4)$$

What is the value of common element

x	0	0	0
x	0	0	0
x	0	0	0

$$= x\bar{z}y + \bar{x}yz + xy\bar{z} + x\bar{y}z$$

for

Exclusive OR

exclusive OR, can take only thing common

Common, that means

no overlapping


$$F(x,y,z) = \sum m(0,3,5,6)$$

$x \oplus y \oplus z$
(XNOR gate)


$$= \bar{x}\bar{y}\bar{z} + x\bar{y}z + \bar{x}y\bar{z} + xy\bar{z}$$

$$= \bar{x}\bar{y}\bar{z} + x\bar{y}z + \bar{x}y\bar{z} + xy\bar{z}$$
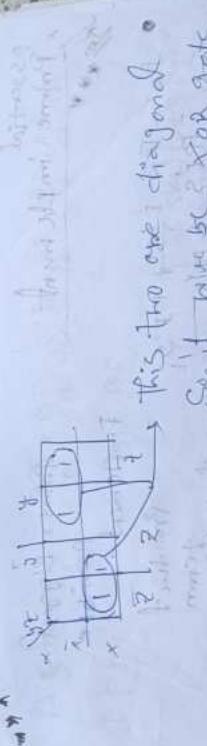
$$= \bar{x}\bar{y}\bar{z} + x\bar{y}z + \bar{x}y\bar{z} + xy\bar{z}$$










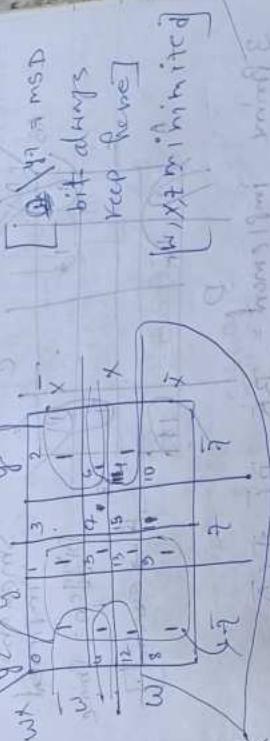This two are diagonal
So, it takes XOR gate



$$\bar{x}F(w,x,y,z) = \sum m(0,1,2,3,4)$$
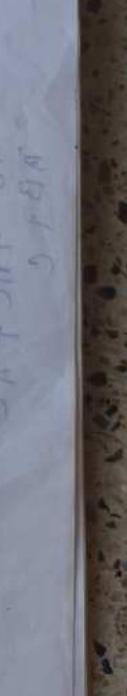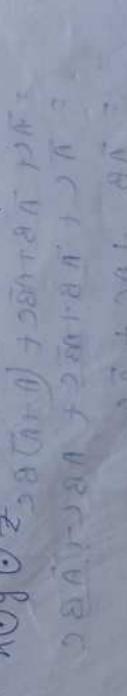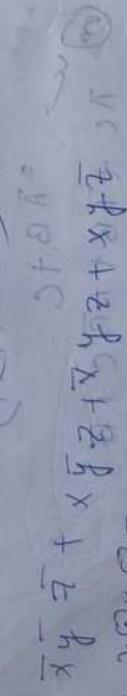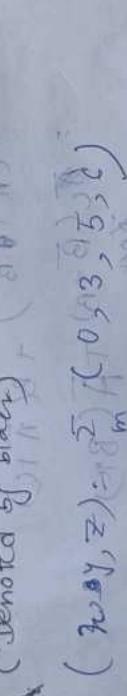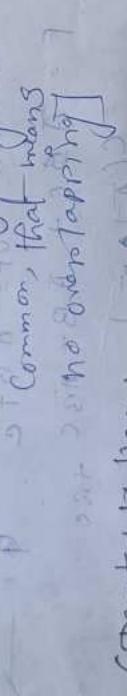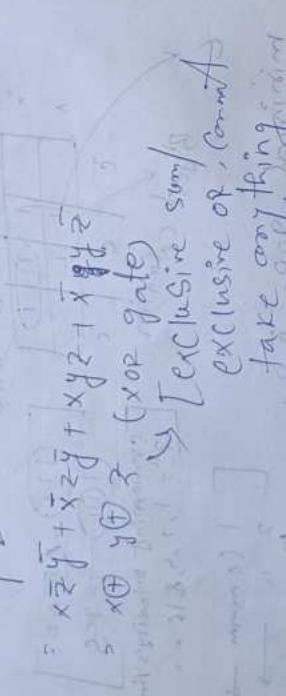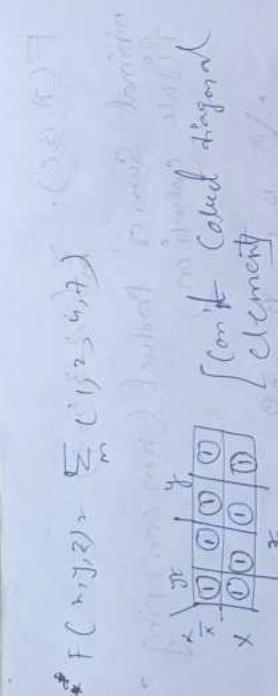
$$= \bar{x}w + \bar{x}w\bar{y} + \bar{x}w\bar{z} + \bar{x}w\bar{y}\bar{z}$$




Essential Prime implement

$$F = EP_1'S + PI'S_1$$

$$= EP_1'S + PI_2'S$$

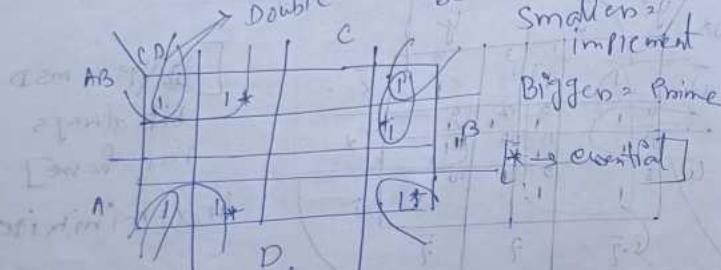
Double overlap if common term
be essential



$$3 \text{ Prime implement} = BD, BC, ACD$$

Essential = a prime implement that covers a specific minterm
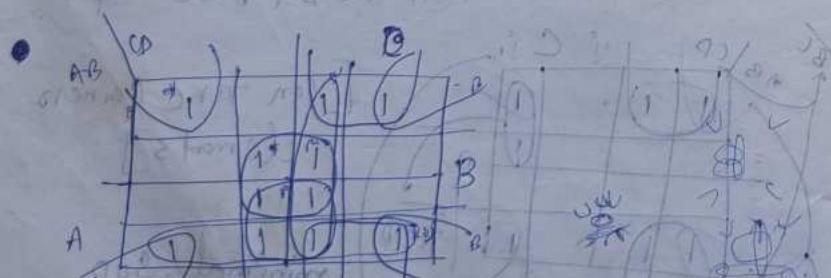
$$(Function) F = BD + BC + ACD \quad (\text{All are essential prime implement})$$



$$F(A, B, C, D) = \{1, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15\}$$

$$= BD + BD + CD + AD + BC$$

To cover min term 15
boundary case needed

Product = Biggest possible

Implement = Product

Product term

overlap if common

Smaller = implement

Biggest = Prime

essential

$$PI'S \rightarrow \overline{BD}, \overline{BD} \quad (1) \subset CM \quad (2) \subset PW \quad (3) \subset AD, \overline{AB} \quad (4) \subset CB$$

$$EP_1'S \rightarrow \overline{BD}, \overline{BD}$$

if of next

$$\rightarrow = \overline{BD} + BD + \overline{BC} + AB$$


$$= \overline{BD} + BD + CD + AB$$

$$= \overline{BD} + BD + CD + AD$$

F essentials are common, remaining will be com.

Product combination

$$1111 = 32 \text{ (variables)}$$

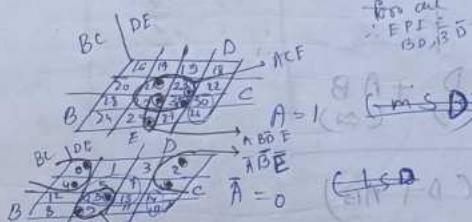

$$P_1 \bar{A} + P_2 A = P_1 (\bar{A} + A) \quad (\text{if common image then can reduce that variable})$$

$$P_2 \bar{A} + P_2 A = P_2 (\bar{A} + A) \quad (\text{then can reduce that variable})$$

$$= P_2$$

(Chittagong University)

$$F(A, B, C, D, E) = \sum_m (0, 2, 4, 6, 8, 13, 21, 23)$$

$$(1, 3, 5) S + (1, E, 1) Z - (5, 23, 31)$$

$$BD'E(\bar{A} + A) = BDE \quad (\text{minimun image})$$

$$F = AC\bar{A}E + BDE + \bar{A}\bar{B}E \quad (\text{SOP})$$

= 1 (obtained)
= 0 (removed)

= 0 (obtained)
= 1 (removed)

(Minimization)

$$F(A, B, C, D) = \sum_m (0, 1, 2, 3, 8, 9, 10)$$

		C		B	D	F
A	B	1	0			
0	0	1	0	0	0	0
0	1	0	1	1	0	1
1	0	0	0	0	1	0
1	1	1	0	1	1	1

[How to get
POS]

$$F = BD + CD + AB$$

$$F = (BD + CD + AB)$$

$$F = (B + D)(\bar{C} + D)(\bar{A} + \bar{B})$$

✓ ~~Don't care condition~~

(Output unspecified, input absent i.e. mean term is not present)

X → 0 [Not specified]

$$(F = \sum m(1, 3, 10) + \sum d(0, 2, 8, 12))$$

		C		B	D	F
A	B	1	0			
0	0	1	0	0	0	0
0	1	0	1	1	0	1
1	0	0	0	0	1	0
1	1	1	0	1	1	1

[x = Don't care]
[Consider 1 as covered
Consider 0 as not covered]

$$F = \bar{x}\bar{z} + \bar{x}z$$

$$F = \sum_m (1, 3, 7, 11, 15) + \sum_d (0, 2, 5)$$

[Any collection
should atleast
contain 1 (minimum)]

w	x	y	z	F
0	0	1	1	0
0	1	1	1	1
1	0	1	1	0
1	1	1	1	1

$$F = \bar{w}\bar{z} + \bar{w}z + yz$$

[z is essential,
as it has to cover
1 must have to take,
if don't take z, as, 0 and 1 covers
that doesn't matter. (the remaining (1, 1) of
to take 1 must have to take z, which covers 1, i.e. essential to cover)]

SOP can be implemented in 2 level

NAND

[Stop don't]

→ D0 → D0

→ D0


→ D0

POS → → → → 2 level NOR

(most minimum stop don't)


$$F = A(CD + B) + BC \bar{C} \rightarrow \text{both SOF and POS present}$$

= ACD

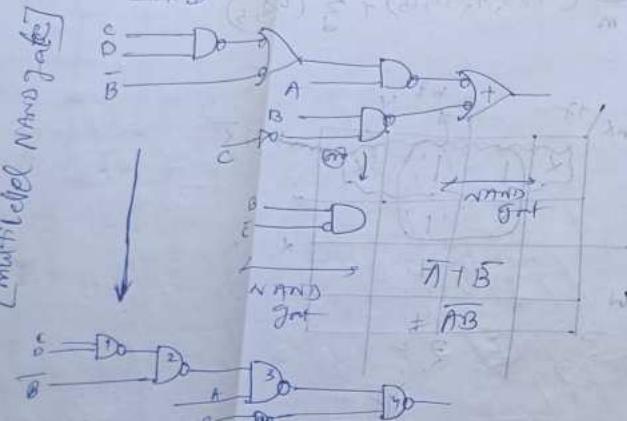

[multilevel NAND gate]


NAND implementation

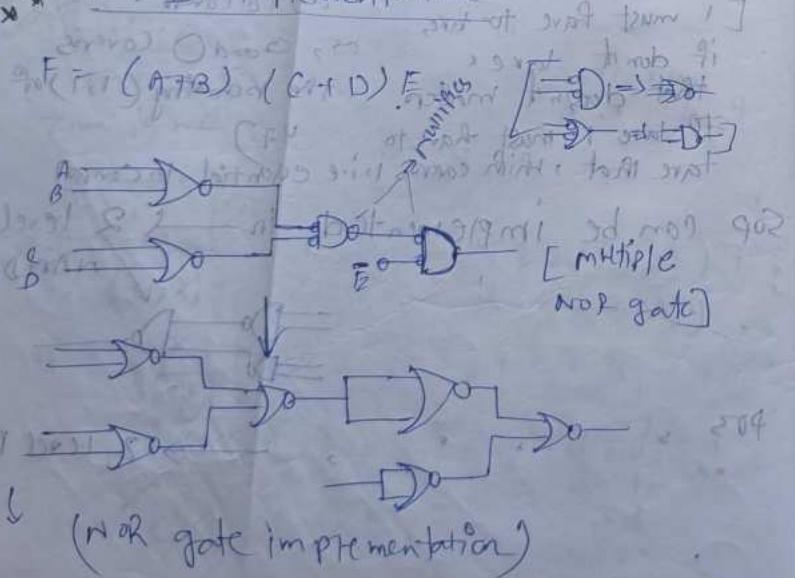


[multiple NOR gate]

(NOR gate implementation)
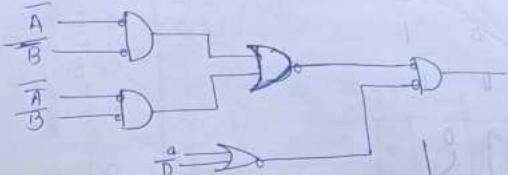
$$F = (A\bar{B} + \bar{A}\bar{B}) (C + D')$$



NOR implementation

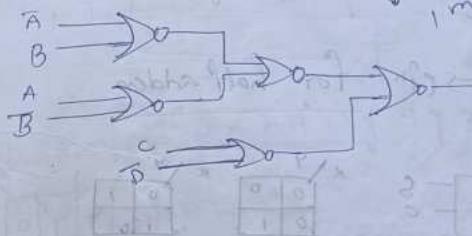

UN

Boolean Algebra \rightarrow Binary Arithmetic

$$x+x=x$$


OR





$$x+y = \bar{c}s' (\text{arry bit } f. \text{ sum bit})$$


Add

2 bit

half adder

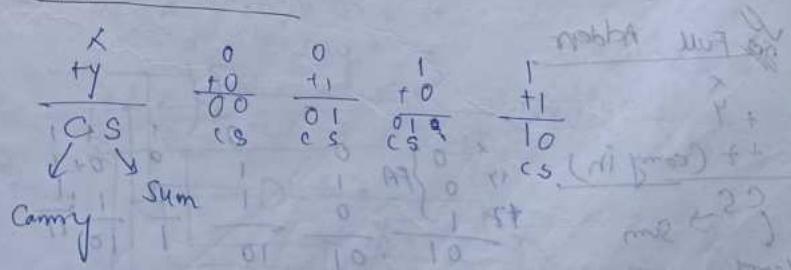

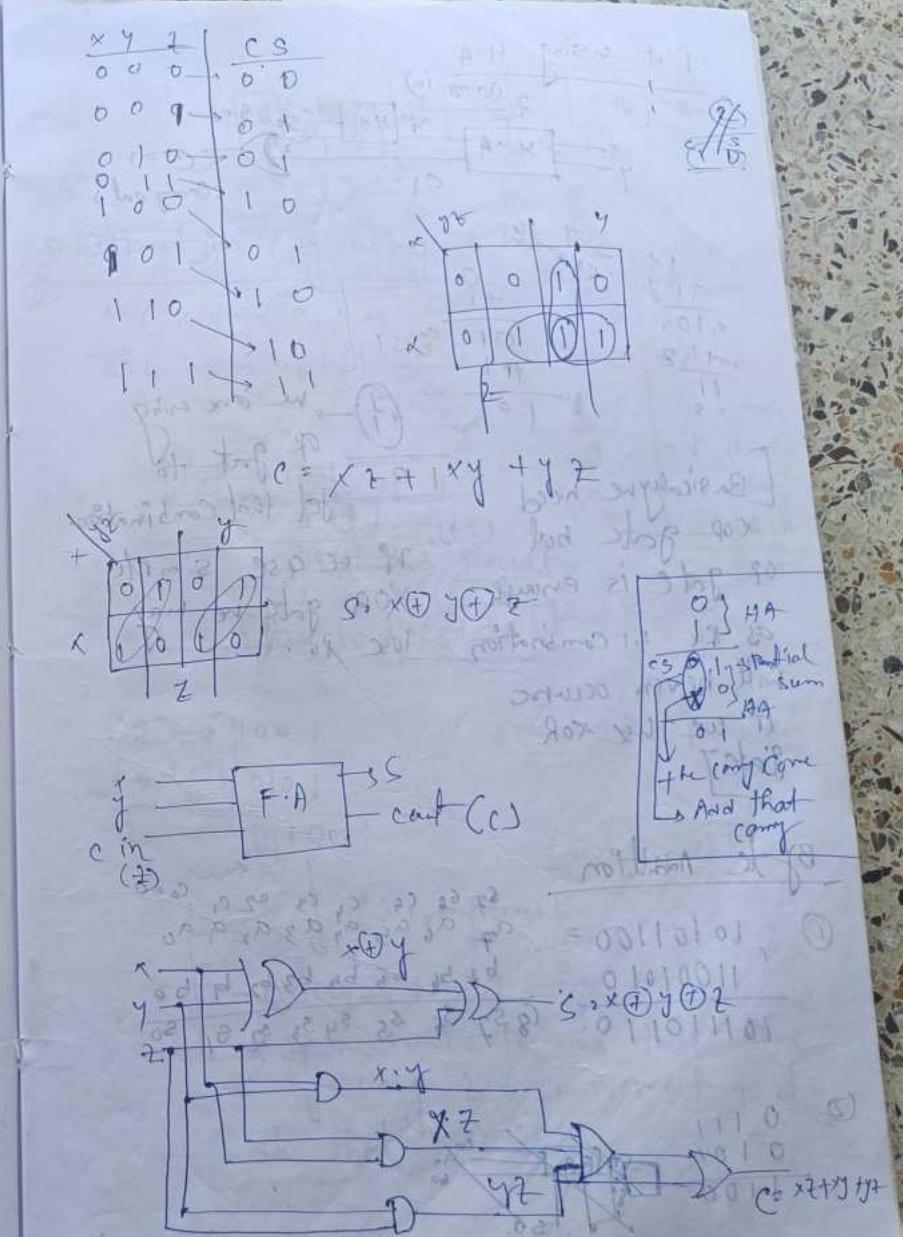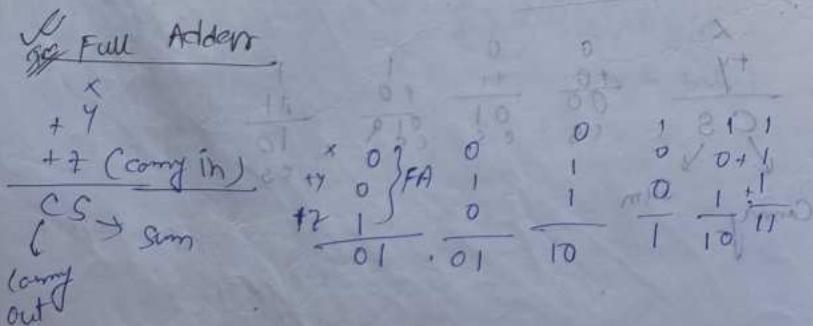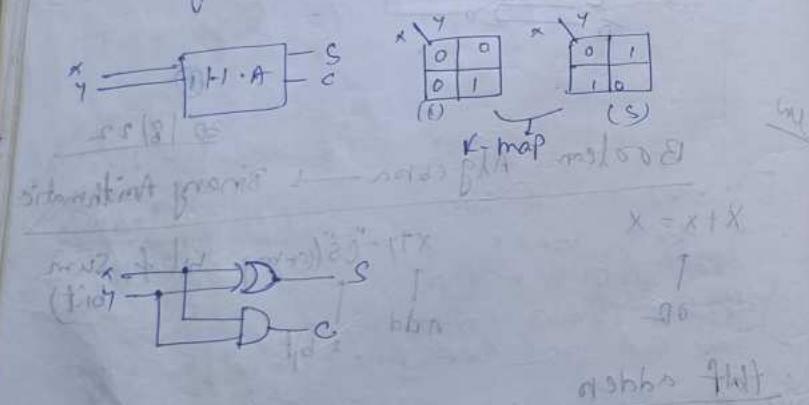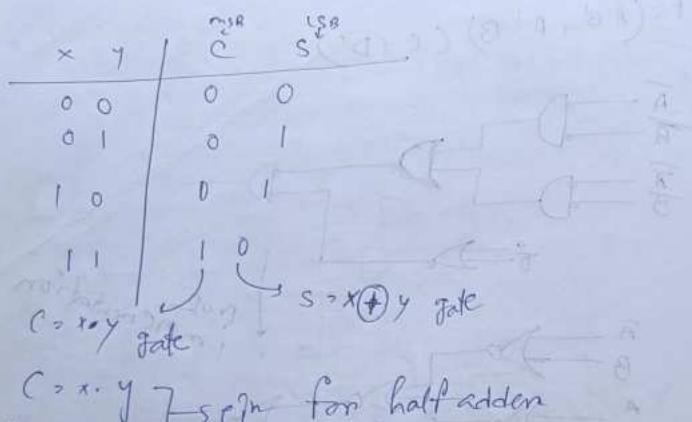

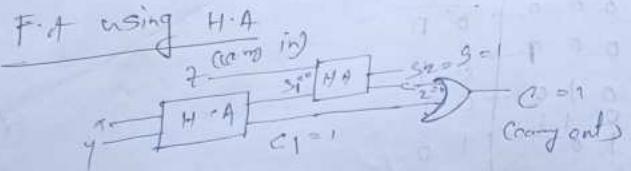

example

$$\begin{array}{r} 11 \\ + 10 \\ \hline 101 \\ \text{count } 1/2 \\ \hline 11 \\ \text{c.s} \end{array}$$

(1) \rightarrow we are using OR gate to get that combination.

[Basically we need XOR gate but OR gate is enough as its 1,1 combination will never occur]

If we use XOR gate]





By the Addition

$$\begin{array}{r} 10101100 = \\ + 11001010 \\ \hline 101110110 \end{array}$$

$a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0$
 $b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1 \ b_0$

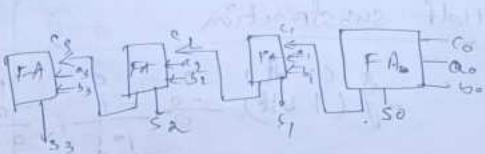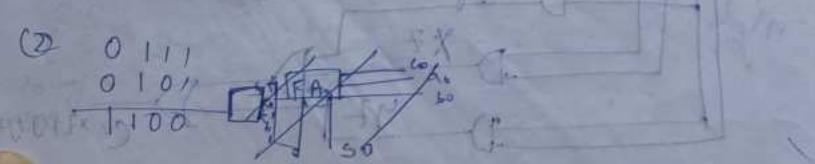$s_7 \ s_6 \ s_5 \ s_4 \ s_3 \ s_2 \ s_1 \ s_0$



Subtraction (by using 4 bit)

A (a₃ a₂ a₁ a₀)

- B (b₃ b₂ b₁ b₀)

$$\begin{array}{r} 1101 \\ - 1011 \\ \hline 0010 \end{array}$$

Result

Have to discard it

$$\begin{array}{r} 1001 \\ - 0101 \\ \hline 1100 \end{array}$$

not working D111
 \downarrow
 $\begin{array}{r} 1001 \\ - 0001 \\ \hline 1000 \end{array}$

$$\begin{array}{r} 1000 \\ - 0010 \\ \hline 1110 \end{array}$$

1's complement

If we want to do that same by using 2's complement that do that process.

Half subtraction

$$\begin{array}{r} x \quad (1 \text{ bit}) \\ - y \quad (1 \text{ bit}) \end{array} \begin{array}{c} 0 \\ -0 \\ \hline 1 \end{array} \begin{array}{c} 0 \\ -1 \\ \hline 1 \\ 0 \\ 1 \end{array}$$

Borrow
bit Difference

x	y	B	D
0	0	0	0
0	1	1	$D = x \oplus y$
1	0	0	$B = \bar{x}y$
1	1	0	

$K-mab$

Full subtractor

$$\begin{array}{r} x \\ -y \\ -z \end{array} \begin{array}{c} 0 \\ -0 \\ -1 \\ -0 \\ -1 \\ -0 \\ -1 \\ -1 \\ \hline 1 \\ 1 \\ 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$

Borrow in


to get borrow in - 2's place
2's complement of 1010 is 1101

$$\begin{array}{r} x \quad y \quad z \\ \hline 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \end{array} \begin{array}{c} B \\ D \end{array}$$

(borrow in)

$$B = \bar{x}(\bar{y}+z)+yz$$

$$D = x \oplus y \oplus z$$

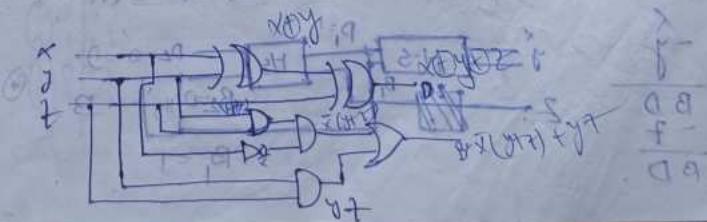

Subtraction (1's complement)

$$\begin{array}{r} 00000111 \\ -11111011 \\ \hline 100001100 \end{array}$$

in
1's
subtraction

$$\begin{array}{r} 0111 \\ +1010 \\ \hline 0001 \end{array}$$

(If we get a carry then add it in next)

$P.F = 1$
 $C_{out} = 1$
 Then, add $10010 + 2$
 This addition is called end-around carry

$$\begin{array}{r} 0101 \\ +1000 \\ \hline 1101 \end{array}$$


(If we don't get a C then

$$\begin{array}{r} 0111 \\ +1000 \\ \hline 1000 \end{array}$$

1's 1's comp)
 $\rightarrow -0010 \rightarrow (-2)$

Carry 1 and 0 → -ve (1's/2's)
 1 → add/discard
 2's → discard, 1's → add

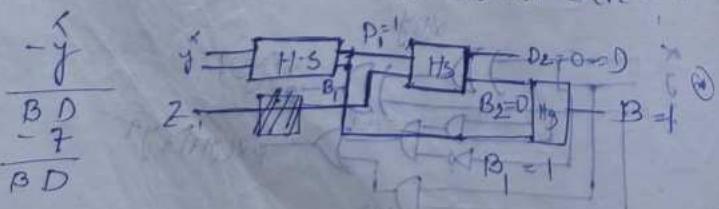
FS in the form of HS on the alternative
priorities for each of them



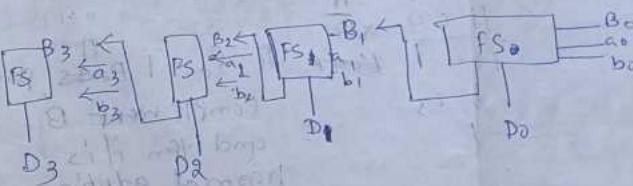
Q1 How to solve the borrow function

$$\begin{array}{r} 10101100 \\ -11001010 \\ \hline 00111110 \end{array}$$


$$\begin{array}{r} 0111 \\ -0101 \\ \hline 010 \end{array}$$



Adder / Subtractor $\rightarrow (A + B)$

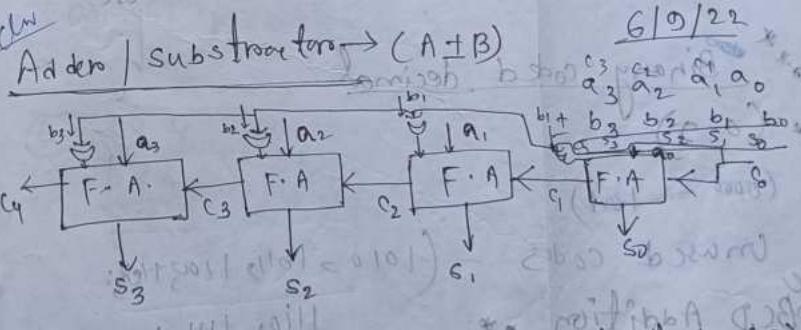

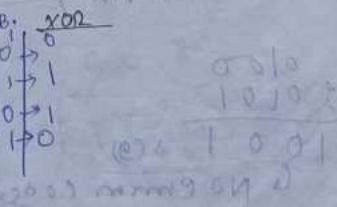* waiting A
 complement bit wise (B)
 \downarrow
 1's complement!



6/9/22

$C_0 = 0$ addition (Pass B)

$C_0 = 1$ 9's subtraction

bitwise complement (B)

↓ 1's Complement +1

$$\begin{array}{r} 2 \longrightarrow 0\ 1\ 0 \xrightarrow{+3} \\ +3 \longrightarrow 0\ 0\ 1 \xrightarrow{\text{B}} \\ \hline 0\ 1\ 0 \end{array}$$

If $C_0 = 0$, pass
B and it will be
simple addition

$$\begin{array}{r} 2 \longrightarrow 0\ 1\ 0 \xrightarrow{+3} \\ +3 \longrightarrow 0\ 0\ 1 \xrightarrow{\text{B}} \\ \hline 1\ 1\ 1 \end{array}$$

If $C_0 = 1$, pass
complement B
and then it is
normal addition

Binary coded decimal

(0-9)

(0000 - 1001)

6 unused codes $\frac{1}{2}(1010, 1011, 1100, 1101, 1110, 1111)$

BCD Addition

$$\begin{array}{r} 9 \\ + 5 \\ \hline 14 \end{array}$$

\downarrow 1000
 \downarrow 0101
 \hline 1001 $\Rightarrow (9)$

6 No error codes
a proper code

$$\begin{array}{r} 4 \longrightarrow 0\ 1\ 0 \\ + 8 \longrightarrow 1\ 0\ 0\ 0 \\ \hline 12 \end{array}$$

\downarrow (0001 0010) $\xrightarrow{\text{Binary (12)}}$ 0110
 \hline 00100100

0000 / 0 100
0009 / 1 000

this is unused
code so we have
to convert the
unused code
So we have to
convert it
In all the cases
we have to add
6 (0110)

$$\begin{array}{r} 8 \longrightarrow 1000 \\ + 9 \longrightarrow 1001 \\ \hline 17 \end{array}$$

10000! (in BCD $\rightarrow 11$, but unused 17 so
add 6)
 \downarrow 10110
 \hline 101011 (7)
 \downarrow in K Coding (K)

(carry generation (carry is 1))

D 18

576

00011000 * 0100

+ 01010111 * 0110

01101111 * 01000000

+ 00100001 * 0110

01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000



01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000

01110110 * 000000

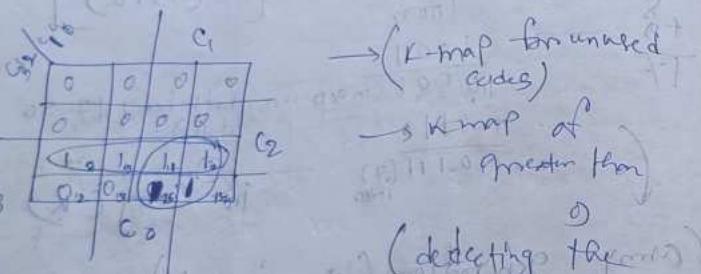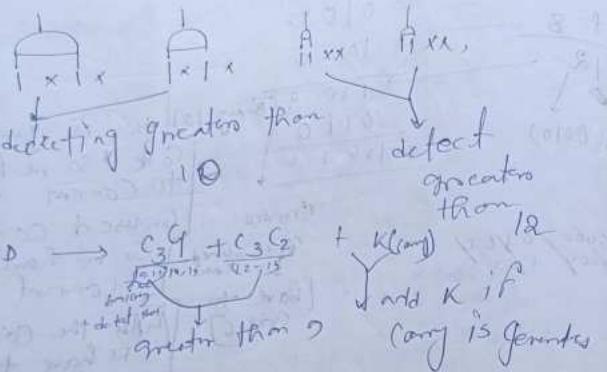

$$(C_3 + C_3 G_2) + K$$

↓ ① ↓ carry ②
unused code

partial product by 1-bit
 $A \times B$



a_1, a_0 (multiplicand)

b_1, b_0 (multiplicand)

$(A \times B) \times b_0$

$c = \frac{a_1 b_0 + a_0 b_0}{a_1 b_1 + a_0 b_1} \times P.P.$

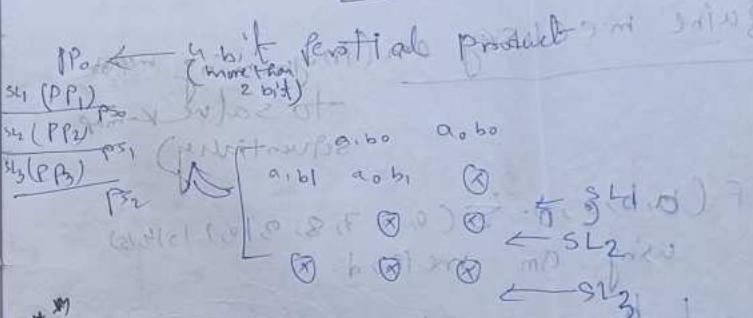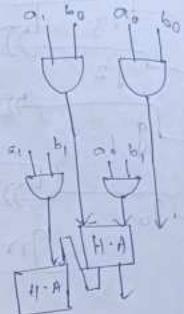
$P.P. = \frac{a_1 b_0 + a_0 b_0}{a_1 b_1 + a_0 b_1}$



* Gray code ↔ Binary

Binary	Gray code
0000	0000
0001	0001
0010	0011
0011	0010
0100	0110
0101	0111
0110	0101
0111	0100

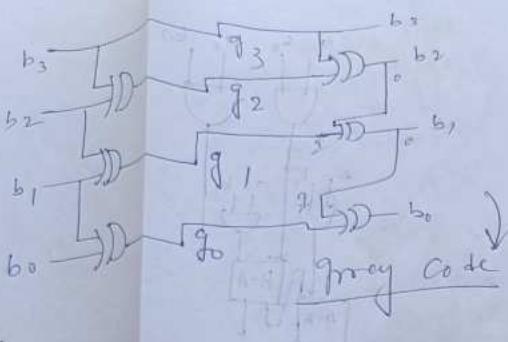$b_3 = b_3$
 $b_2 = b_3 \oplus b_2$
 $b_1 = b_2 \oplus b_1$
 $b_0 = b_1 \oplus b_0$



Quine McCluskey om (Programming method to solve K-map sequentially)

$$F(\text{Out}, \text{B}) = \sum(0, 3, 7, 8, 9, 10, 11, 13, 15)$$

using Sm method.

	b	c	d
0	0	0	0
1	0	0	1
2	1	0	0
3	1	0	1

- ① Gate testing → Sm
- ② Universal gate
- ③ FA
- ④ F.S

		Sm			
		Group 0			
		0	1	0000	0001
1110				(0, 8)	-000
1011					
0111					
0000					
1000		1	8	1000	(8, 9)
0101					
0001					
1000		2	5	0101	(3, 7)
0101					
0001					
1000		3	7	1001	(9, 11)
0101					
0001					
1000		4	10	1010	(10, 11)
0101					
0001					
1000		5	7	0111	(10, 11)
0101					
0001					

11	1011	(0, 8)	-111
14	1110	(0, 8)	-111
15	1111	(0, 8)	-111

0	(0, 8)	bcd	-000	(0, 8), (10, 11)	10 - - (a, b)
1	(8, 9)	100-	(10, 11), (14, 15)	1-1 - (a, c)	
	(8, 9)	10-0	(10, 11), (14, 15)	1-1 -	
2	(5, 7)	01-1	(a, b)		
	(5, 7)	10-			
	(5, 7)	1010			
3	(2, 15)	-111	(b, c)		
	(2, 15)	1-11			
	(2, 15)	111-			

$$P_1 = 0 \cdot 5 + 8 \cdot 9 + 10 \cdot 11 + 14 \cdot 15$$

$$\star ac (ab \cdot ad) \cdot (bc = 18) = 1 \cdot 1 \cdot 1 \cdot 1$$

$$abc \quad 0 \cdot 1 \cdot 1 \cdot 1 = (1 \cdot 1 \cdot 1) \cdot 1 \cdot 1 = 1 \cdot 1 \cdot 1 \cdot 1$$

$$bcd \quad 1 \cdot 1 \cdot 1 \cdot 1 = 1 \cdot 1 \cdot 1 \cdot 1$$

$$\star \bar{a}bd (ad \cdot bc) \cdot (ab > 1d) = 1 \cdot 1 \cdot 1 \cdot 1$$

$$\star \bar{b} \bar{c} \bar{d} (ab \cdot ad) \cdot 1 \cdot 1 = 1 \cdot 1 \cdot 1 \cdot 1$$

(As no product term can collect 0, so it is essential prime implicant)

for function is - $ac + ab\bar{t} + \bar{a}bd + \bar{t}\bar{b}d$
 (FPE) v/e

13/9/22

dr
 1-bit magnitude compensation

x_i	y_i	$x_i = y_i$	$x_i > y_i$	$x_i < y_i$
0 0	1	0	0	0
0 1	0	0	1	0
1 0	0	1	0	0
1 1	1	0	0	0

[At a time
 only one output
 $(E/F/L)$ is active,
 not all or none
 from can be active]

$E_i = x_0 y_i$ (E = equality function) [XNOR gate]

$G_i = x_i \bar{y}_i$ (G = greater than)

$L_i = x_i \bar{y}_i$ (L = less than)

1-bit Compensation

2-bit Compensation

$x_i x_0 \quad y_i y_0 \quad F \quad G \quad L$

$$E = (x_i = y_i) \text{ and } (x_0 = y_0) = F_i \cdot F_0$$

$$G = (x_i > y_i) \text{ and } (x_0 > y_0)$$


$$\Rightarrow (x_i \bar{y}_i + E_i \cdot (x_0 \bar{y}_0)) = G_i + F_i F_0$$

$$E_i = x_i \oplus y_i$$

$$L = (x_i < y_i) \text{ or } (x_i = y_i) \cdot (x_0 < y_0)$$


$$= \bar{x}_i \bar{y}_i + E_i \cdot (\bar{x}_0 \bar{y}_0) = L + E_i F_0$$

Block diagram

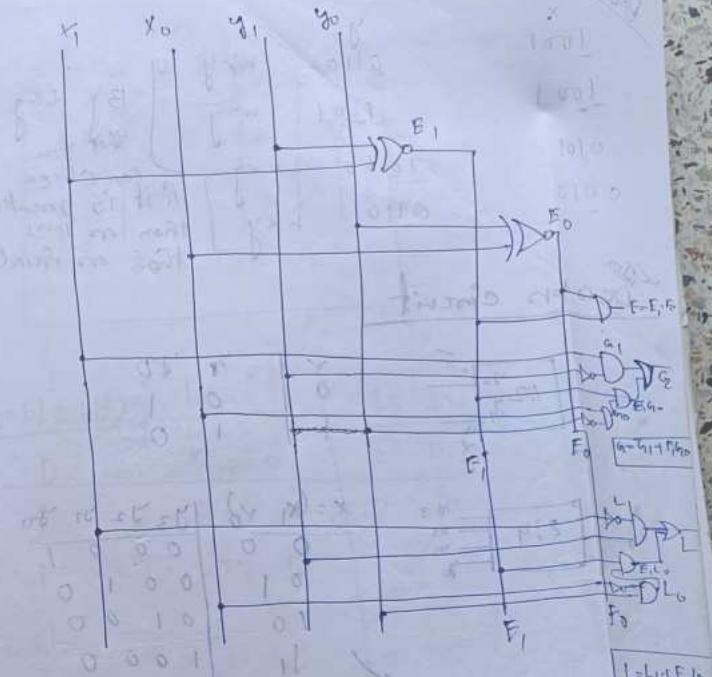

$$x_i \bar{y}_i + E_i \cdot (x_0 \bar{y}_0) = E_i = G_i + F_i$$

$$x_i \oplus y_i = E_i = G_i + F_i$$

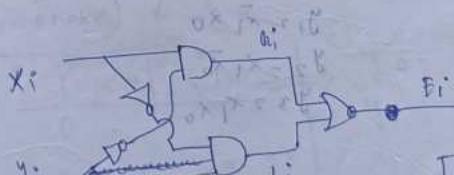

$$E = E_3 \cdot E_2 \cdot E_1 \cdot E_0$$

$$G = L_3 + E_3 \cdot G_2 + E_3 \cdot E_2 \cdot G_1 + E_3 \cdot E_2 \cdot E_1 \cdot G_0$$

$$L = L_3 + E_3 \cdot E_2 + E_3 \cdot E_2 \cdot L_1 + E_3 \cdot E_2 \cdot E_1 \cdot L_0$$

If all bits same
 Equal or not you can
 decide
 from the last
 bit)

$$\text{Eulerian form is } ac + ab\bar{t} + \bar{a}bd + \bar{b}\bar{c}\bar{d} \quad (2)$$

(EPI) ✓

lure compensation

$x_i = y_i$	y_i	$\ln y_i$
1	0	0
0	0	1
0	1	0
0	0	0

- \triangleright y_i ($E =$ equality function)
- \triangleright f_i (\geq greater than)
- \triangleright L_j (\leq less than)

Comparators


Perceptrons

$$y_1, y_0 \quad F \quad G \\ \text{and } (x_0 = y_0) =$$

$$+ \left[\sum_{i=1}^n (x_i - \bar{x}_0) \right] = \underline{\underline{G}}$$

$$\textcircled{1} \quad y_i \\ h_1 \leq y_j \text{ or } (h_1, y_j)$$
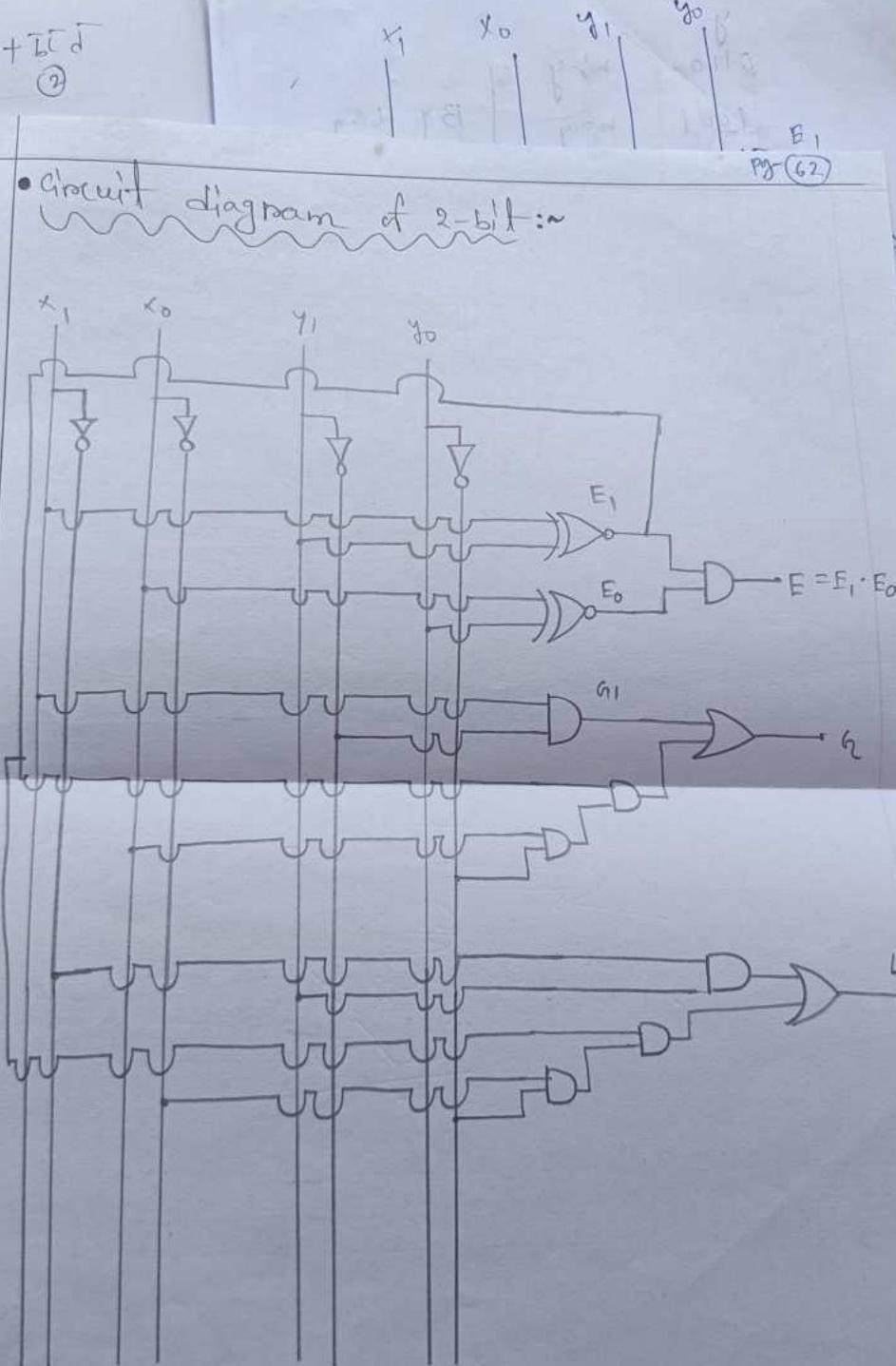
$$\bar{u}_1 + E_1 \cdot (\bar{x}_0, \bar{y}_0)$$



$$L = L_1 \cap F, L$$

- better one
- o not you can decide
- 2 F. G. o from the lot
- C
- F. I. L. 20 o big)

Forward	E-bit	x	y
1001	0110	n/y	
1001	1001	n/y	
0101	1010	n/y	
0010	0110	n/y	

By doing
that you
can check
if it is greater
than or less
than or equal.

Decoder circuit



$x = (x_1, x_0)$	y_3	y_2	y_1	y_0
00	0	0	0	1
01	0	0	1	0
10	0	1	0	0
11	1	0	0	0



(It is a diagonal matrix)

$$y_0 = \bar{x}_0 \bar{x}_1 + 1$$

$$y_1 = \bar{x}_0 x_1$$

$$y_2 = x_1 \bar{x}_0$$

$$y_3 = x_1 x_0$$

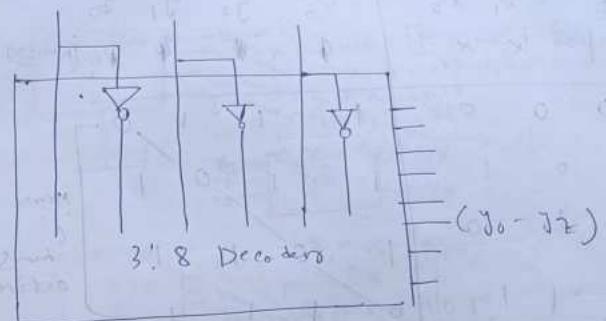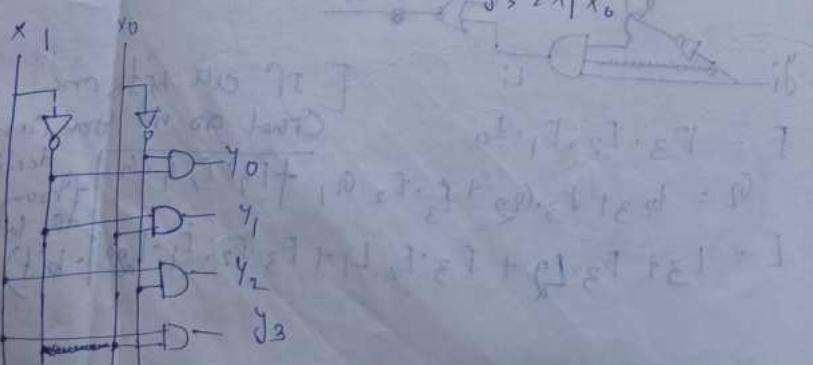

(E-bit)		x_1	x_0	y_3	y_2	y_1	y_0
①	D	0	0	0	0	0	0
		1	0	0	0	0	1
		0	1	0	1	0	0
		1	1	1	0	0	0

High
Enable

② $\overline{E} \cdot \overline{x}_1 \cdot \overline{x}_0 \Rightarrow y_0 = \overline{E} \cdot \overline{x}_1 \cdot \overline{x}_0$

$y_1 = \overline{E} \cdot \overline{x}_1 \cdot x_0$

$y_2 = \overline{E} \cdot x_1 \cdot \overline{x}_0$

$y_3 = \overline{E} \cdot x_1 \cdot x_0$

Enable
decoder

① $y_0 = E \cdot \bar{x}_1 \cdot \bar{x}_0$

$y_1 = E \cdot \bar{x}_1 \cdot x_0$






$y_2 = E \cdot x_1 \cdot \bar{x}_0$

$y_3 = E \cdot x_1 \cdot x_0$

E	x_1	x_0	y_3	y_2	y_1	y_0	PC (initial)
1	X	X	0	0	0	0	0000
0	0	0	1	1	1	0	0001
0	1	0	1	0	1	1	0110
0	1	1	0	1	1	1	0111

More 0 means active

2:4 enable decoder (active low)

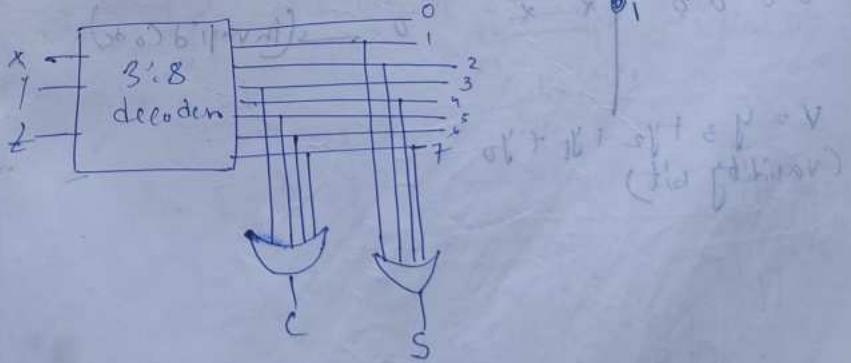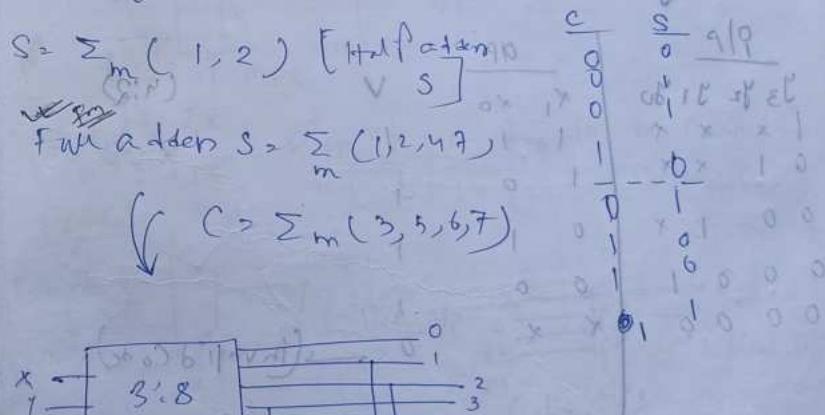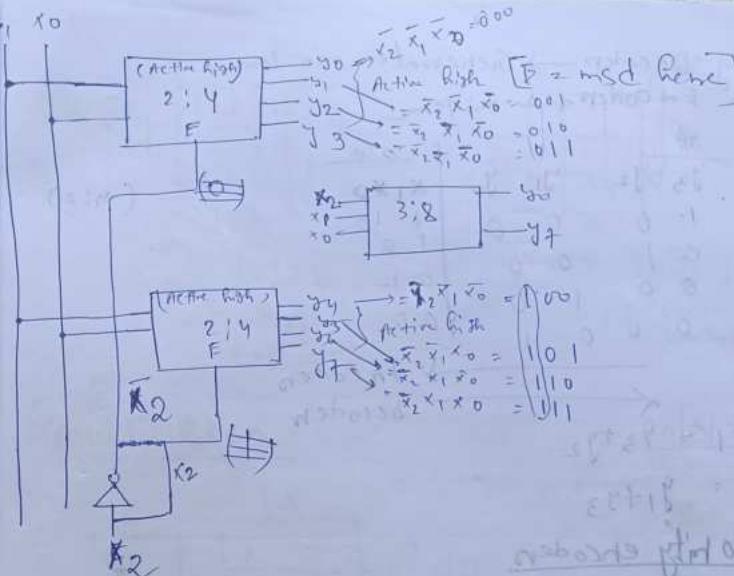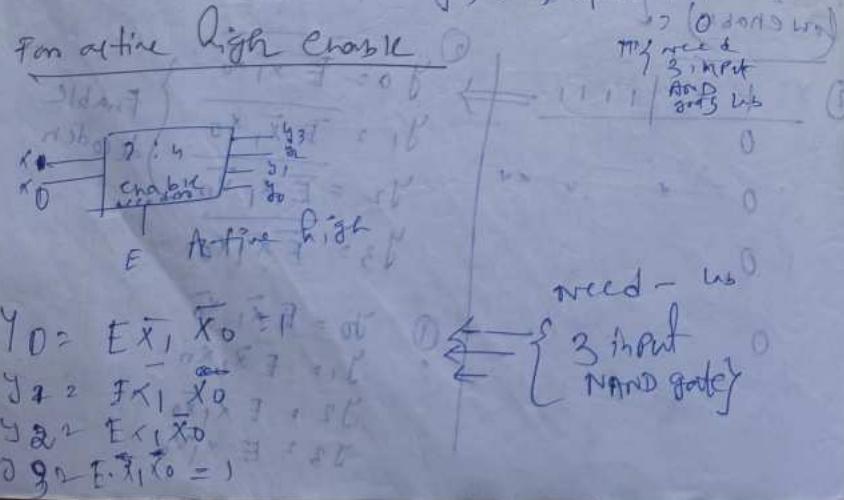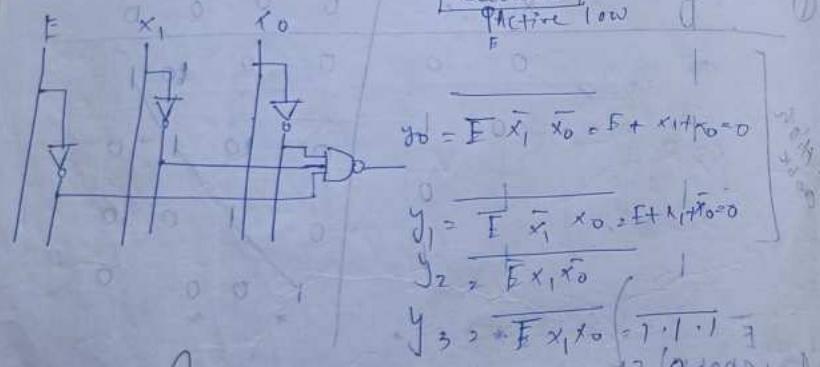

Binary \rightarrow Decoder \rightarrow Generate min term
 & Encoder \leftarrow min term

J_0	y_3	y_2	y_1	y_0	$x_1 x_0$	$y_3 y_2 y_1 y_0$	$(y_1 y_2)$
1 - 0	0	0	0	1	1 - 1	0 1 0	
0 1	0	0	0	1	0	1 1 0	
0 0	1 - 0	0	0	1	0 - 1	0 1 -	
0 0	0	0	0	1	0 0	0 0 1	

$\xrightarrow{\text{Encoder}}$ Decoden


$$x_1 = y_3 + y_2$$

$$x_0 = y_1 + y_3$$

Priority encoder

Q/P	y_3	y_2	y_1	y_0	x_1	x_0	$(y_1 y_2)$
1 x x 1	1	1	1	1	1	1	1 1 1
0 1 x x	0	1	0	1	0	1	0 1 1
0 0 1 x	0	0	1	0	0	1	0 0 1
0 0 0 1	0	0	0	1	0	0	0 0 0
0 0 0 0	1	x	x	x	0	0	0 0 0
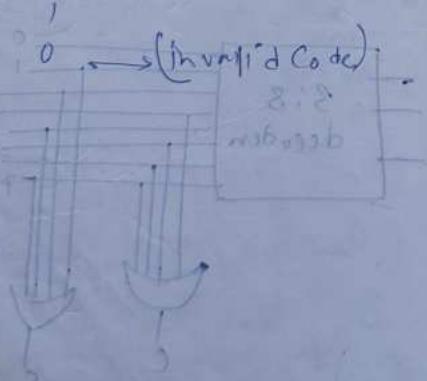
$$V = y_3 + y_2 + y_1 + y_0 \quad (\text{validity bit})$$



J_0	y_3	y_2	y_1	y_0	$(y_1 y_2)$
1 - 0	1	1	1	1	1 1 1
0 1	1	1	0	1	0 1 1
0 0	1	0	1	0	0 0 1
0 0	0	1	0	0	0 0 0
0 0	0	0	1	0	0 0 0
0 0	0	0	0	1	0 0 0


$$x_1 = y_2 + y_3 \\ (\text{Priority encoder})$$

J_0	y_3	y_2	y_1	y_0	$(y_1 y_2)$
1 - 0	1	1	1	1	1 1 1
0 1	1	1	0	1	0 1 1
0 0	1	0	1	0	0 0 1
0 0	0	1	0	0	0 0 0
0 0	0	0	1	0	0 0 0
0 0	0	0	0	1	0 0 0

$$x_0 = y_3 + y_2 + y_1 \\ (\text{Priority encoder})$$


Multiplexers

20/03/22

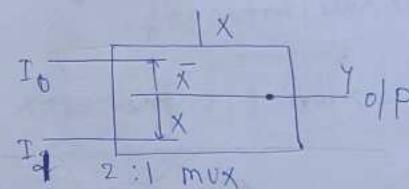

$I_2 I_0 X$
 $I_2 I_1 X$ when $X = 0$ forward be connected / " " $X = 1$ I_1 . . . I_n

Symbol-

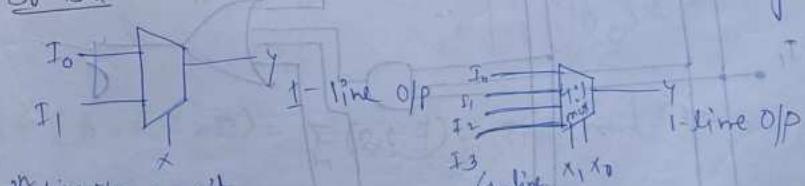

$\ln 4 : 2$

$$\Rightarrow \log_2 4 = 2$$

$$Y = I_0 \bar{x}_1 \bar{x}_0 \text{ (00)} \quad Y = I_2 x_1 \bar{x}_0 \text{ (10)} \quad \begin{cases} x = 0 \\ x = 1 \end{cases}$$

$$Y_2 = I_1 \bar{x}_1 x_0 \text{ (01)} \quad Y = I_3 x_1 x_0 \text{ (11)} \quad \begin{cases} x = 0 \\ x = 1 \end{cases}$$


During making boolean exp.

The base of $\ln 4 : 2$
 it is normal
 \log

x_1	x_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

when $(0, 0)$, then $y = I_0$
 $\therefore x_1 = 0, x_0 = 0$.
 Boolean expr: $y = I_0 \bar{x}_1 \bar{x}_0$

Implementation

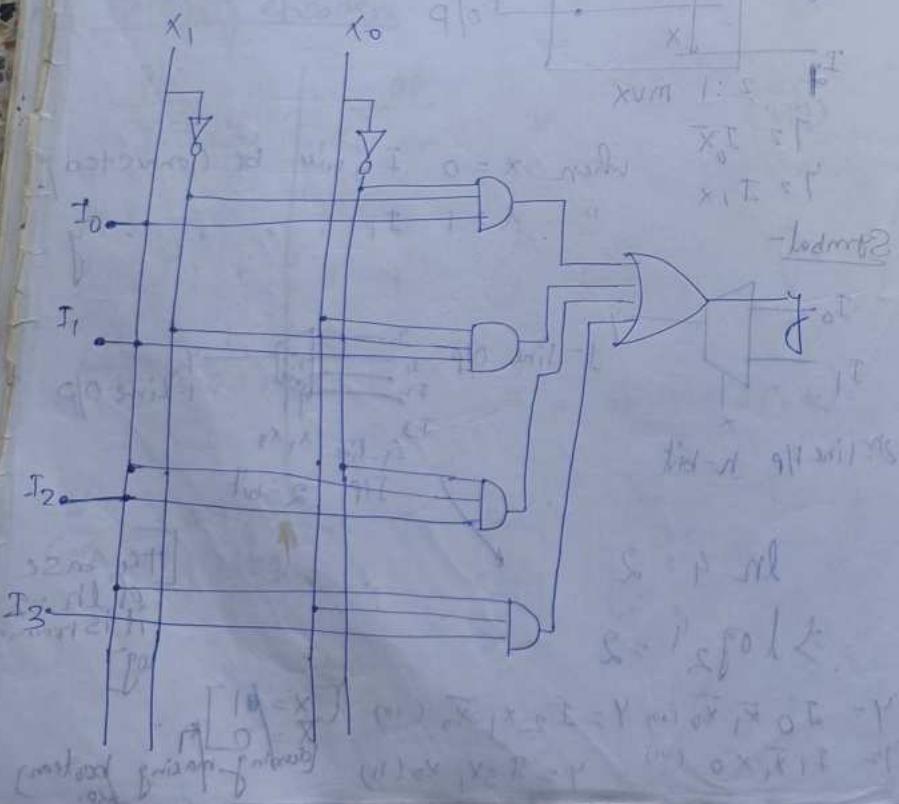


Let's show those (previous) 4 terms.
 that it's one 2-to-1.


$$Y = I_0 \bar{x}_1 \bar{x}_0 + I_1 \bar{x}_1 x_0 + I_2 x_1 \bar{x}_0 + I_3 x_1 x_0$$

How to implement function using mux

Implement a XOR gate using mux -

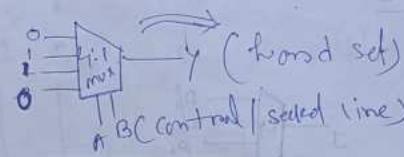

XOR using 2:1 mux

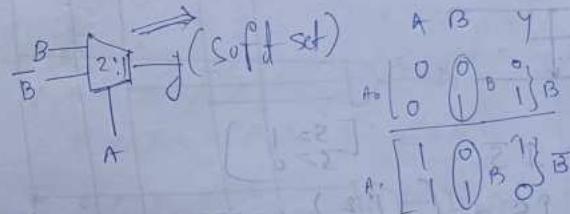



Q) $F(A, B, C) = \sum_m(2, 6, 7) \leftarrow$ Implement this F using mux.

3 input \rightarrow 8 minterms
 so, we have to use 4:1 mux

Control line			F
A	B	C	0
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

msd \rightarrow control line

11 V. U

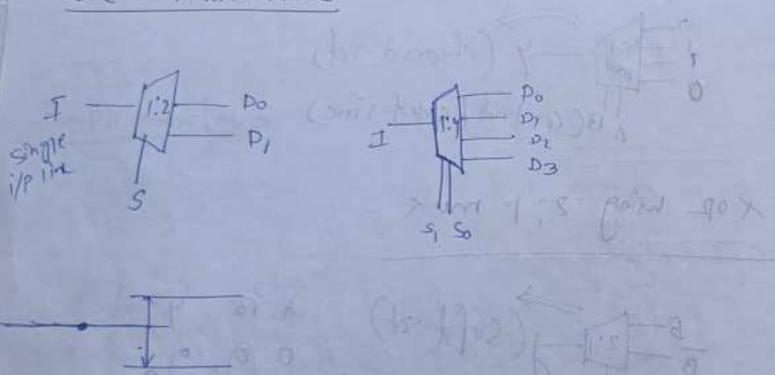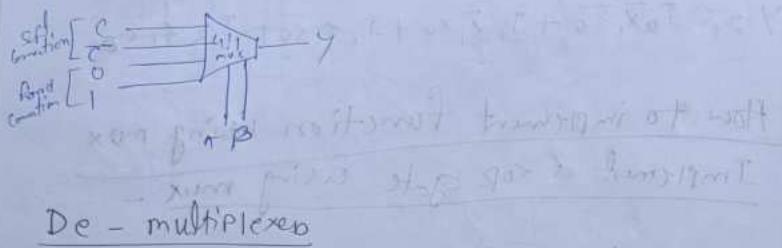

$$D_0 = I \bar{S} \quad (1:2)$$


$$D_1 = I S \quad (1:2)$$

$$D_2 = I \bar{S}_1 \bar{S}_0$$

$$D_3 = I S_1 \bar{S}_0$$

1:2 de-mux		1:4 de-mux			
S	P	D ₀	D ₁	D ₂	D ₃
0	0	I	0	0	0
1	0	0	I	0	0
0	1	0	0	I	0
1	1	0	0	0	I

Block diagram of a 1:2 de-multiplexer:

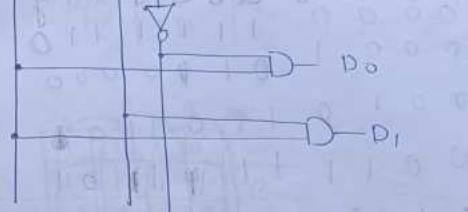


Block diagram of a 1:4 de-multiplexer:




BCD to 7 segment decoder

$f \bar{f}$	a	How to show				b	c	d	e	f	g
f	\bar{f}	b	c	d	e	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1	0
0	0	1	1	1	1	1	1	1	0	1	1
0	1	0	0	1	1	0	1	1	0	1	1
1	1	1	1	1	1	1	1	1	1	1	1
2	1	1	0	1	1	0	1	0	1	1	1
3	1	1	1	1	1	1	1	1	1	1	1
4	1	1	1	1	1	1	1	0	1	1	1
5	1	1	1	1	1	1	0	1	1	1	1
6	1	1	1	1	1	1	0	0	1	1	1
7	1	1	1	1	1	1	0	0	0	1	1
8	1	1	1	1	1	1	1	1	1	1	1
9	1	1	1	1	1	1	1	1	1	1	0


Code is absent (common code)

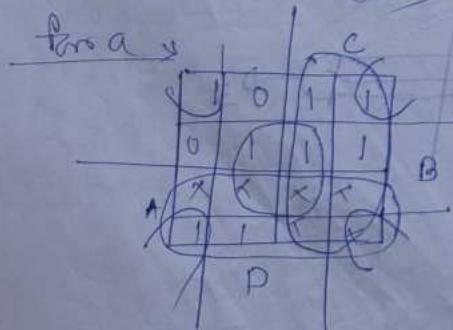


$$a = A + ct(BD + B'D')$$

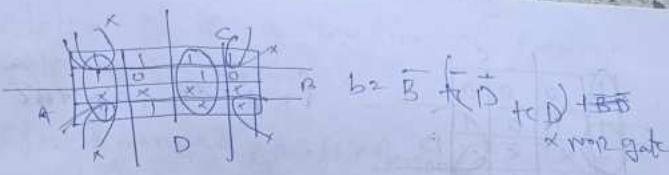


$$b = B + ct(D + BD)$$

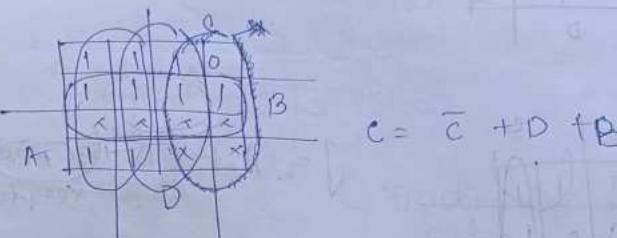

$$c = \bar{C} + D + B$$

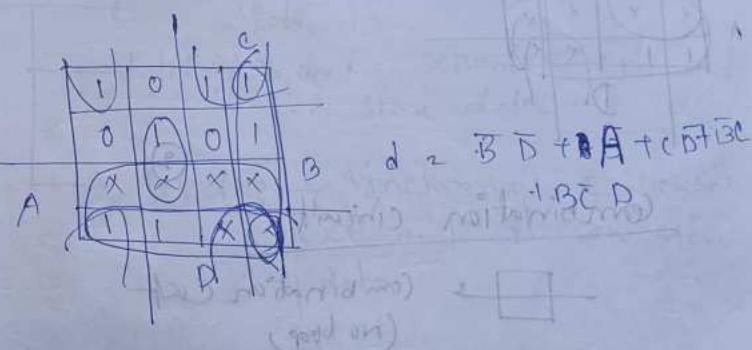

$$d = BD + A + ct(BD + BC)$$

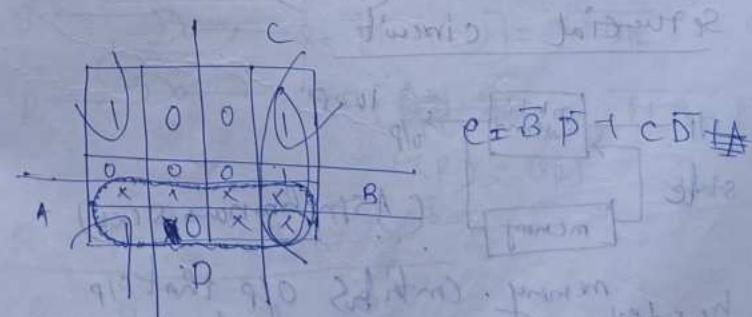

$$e = B'D + CD + ct$$

	0	0	0	c
D	0	0	0	1
A	0	0	1	0
B	0	1	0	1
C	1	1	1	0


$$f = A + CD + B\bar{D} + B\bar{C}$$

	0	0	1	c
D	0	0	0	1
A	0	1	0	0
B	1	1	1	0
C	1	0	1	1


$$J = A + \bar{C}D + BC + \bar{B}C$$

XOR gate

Combination circuit

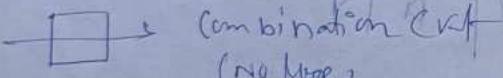


Sequential circuit

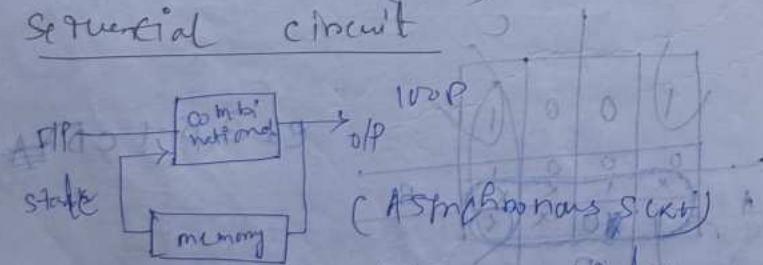

is needed memory contains O/P, that O/P by combinational circ.
O/P = function (I/P, state)

present state > It is a function of previous state and input.

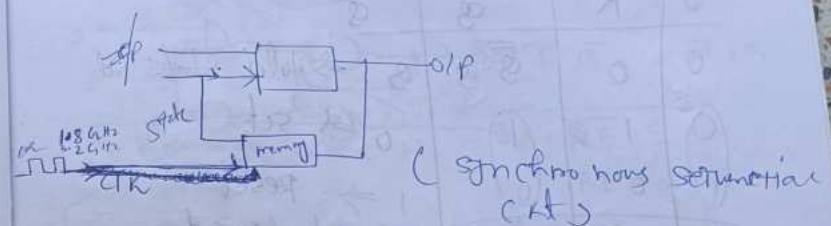synchronous / Asynchronous
clock no clock



memory
latch → it can store data
flip-flop → synchronous sequential circuit and it can store data

$$S \rightarrow Q_S [f(S, R, S)] = \overline{S + Q_R} = \overline{S} \cdot \overline{Q_R}$$

$$R \rightarrow Q_R [f(R, S)] = \overline{R + Q_S} = \overline{R} \cdot \overline{Q_S}$$

$$F(R) = Q_R$$

S	R	$\overline{S + Q_S}$	$\overline{Q_R}$	Q _S	Q _R	?
0	0	$\overline{Q_R}$	$\overline{Q_S}$	0	0	0
0	1	$\overline{Q_R}$	0	0	1	0
1	0	0	$\overline{Q_S} = 1$	1	0	1
1	1	0	0	0	0	not allowed

By rewriting the $d_m = S[\alpha] = S + \bar{R}[\alpha] = S$


$$S[\alpha] = \bar{R}[\alpha] = \bar{R} \cdot S$$

S	R	S	\bar{S}
0	0	$\bar{S} \cdot S$	\bar{S}
0	1	0	$\bar{S} \rightarrow$ Hold state set
1	0	0	0 \rightarrow Set
1	1	0	1 \rightarrow Reset not allowed

NOR based SR Latch

NOR SR the relation between S and \bar{S} is complement so we can write

NOR SR

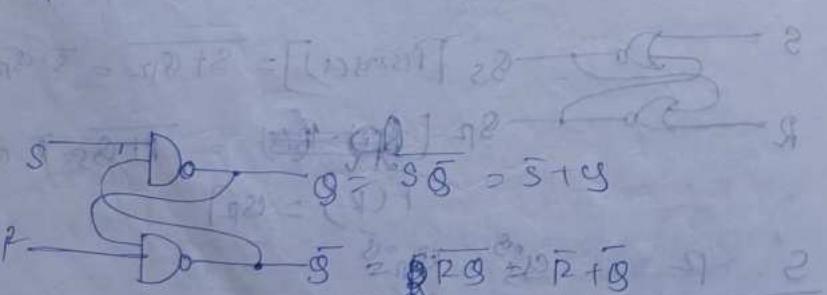


S	R	S	\bar{S}
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

NA \rightarrow Not Applicable
Set \rightarrow 0
Reset \rightarrow 1
 \bar{S} Hold state

NAND based SR latch

27/9/22


Enabled SR Latch

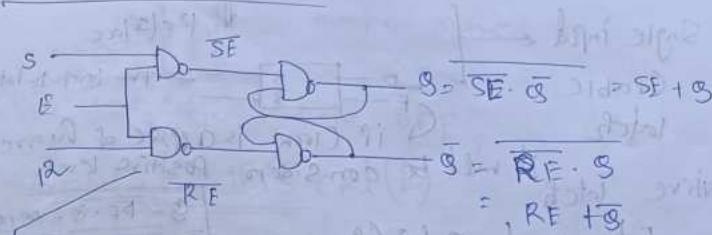

E	S	R	S	\bar{S}
0	x	x	\bar{S}	$S \rightarrow$ Hold
1	0	0	\bar{S}	$\bar{S} \rightarrow$ hold
1	0	1	0	1 \rightarrow Reset
1	1	0	1	0 \rightarrow Set
1	1	1	1	1 \rightarrow N.A.

(function table)

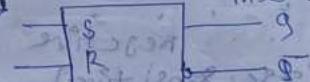Level triggered \rightarrow Enabled SR latch
A level to which material rises and triggers some action either falls or




For high level enables

Without flop it's a latch.


When clock is applied it will be level sensitive flip flop.

clock
High level

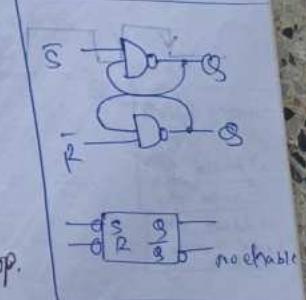

D latch (Don't have N/A condition)



↳ Structure of SR latch

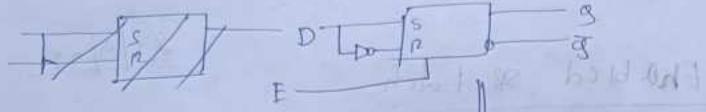

Single input →
enable latch →
if clock is applied because
it will be considered positive level

E	D	S	Q (function table)
0	X	0	→ hold
1	0	1	→ reset
1	1	0	→ set

$$S = \overline{DE} \cdot \overline{S} = \overline{DE} \cdot \overline{S}$$

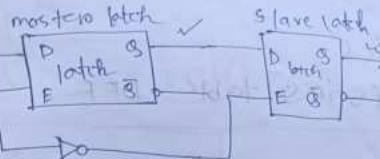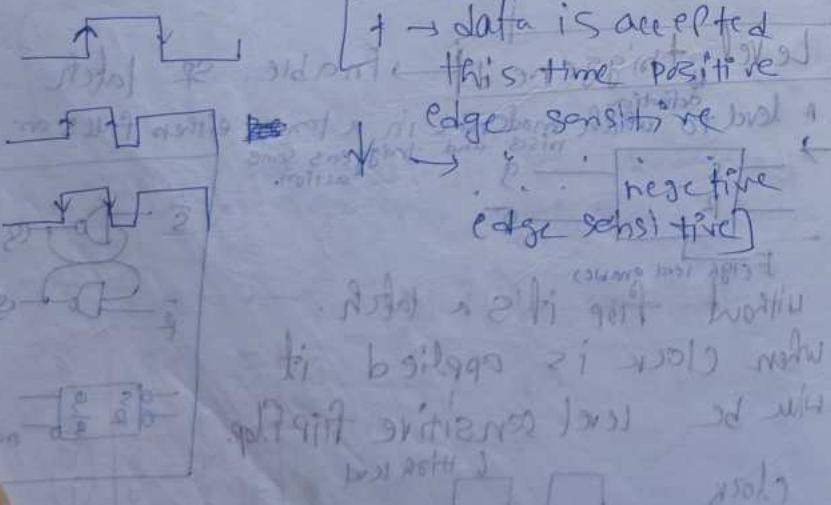
$$\bar{S} = DE \cdot S = DE \cdot S$$


→ out will be available after this time
↳ master-slave
- ve edge sensitive DFF

Symbol of this (cnt(1))




- ve edge sensitive DFF

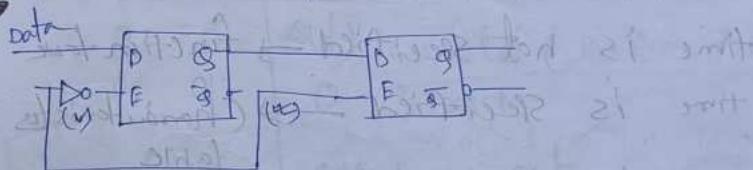

→ master-slave and delay time
↳ data will be available during this time

Symbol of this (cnt(1))

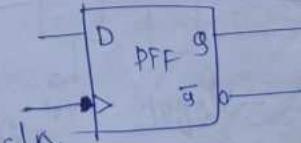

→ the edge sensitive

only one terminal bubble, arrow → for +ve
No bubble arrow → for -ve
edge sensitive

Characteristics

characteristics table DFF

D	$S(t+1)$	$S(t)$	Previous Step
0	0	reset	$S(t+1) \rightarrow$ next step
1	1	set	

Characteristics eqn - $S(t+1) = D(t) = 0$


only present input determine the

next step

time is not specified \rightarrow function table

time is specified \rightarrow characteristics table

One reset can be added in diagram


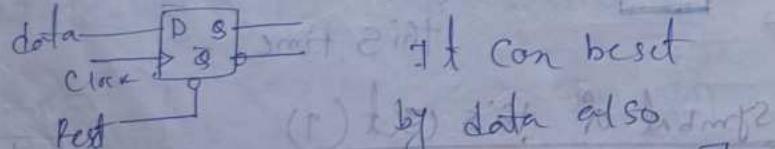


[function table]


D	R	S
0	0	0
1	1	1

JK-FF
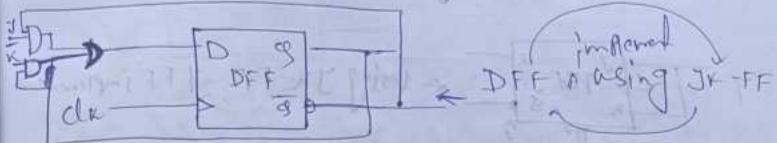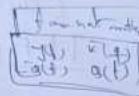
$$S(t+1) = J\bar{S} + K\bar{S}$$
 (Characteristics)



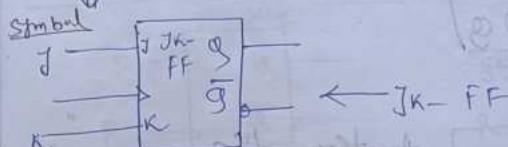
+ve edge sensitive DFF \rightarrow (t+1) = (t)t



Char. table of JK-FF

J	K	$S(t+1)$
0	0	$S(t)$ \rightarrow hold (Previous step)
0	1	0 \rightarrow reset
1	0	$S(t) + S = 1 \rightarrow$ set
1	1	$S(t) \rightarrow$ complementary (next state)


The benefit of complementary function.

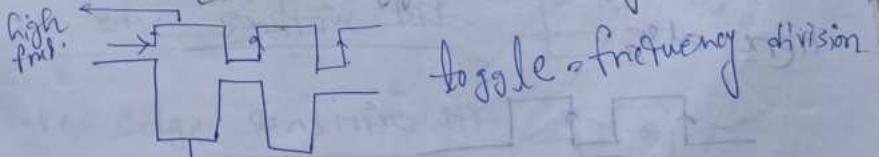

toggle - specifically to change between usually two states of an electronic device by means of a simple hardware or software control.


(such as button, switch etc)

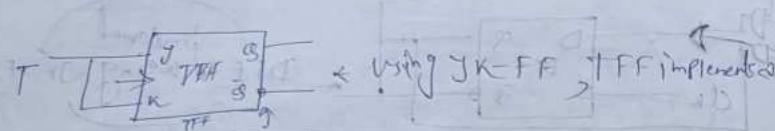TFF (T) has state and complement state only



$$Q(T) = T \bar{Q} + \bar{T} Q \quad (\text{char. eqn})$$

$$Q(T\bar{T}) = T \oplus Q$$

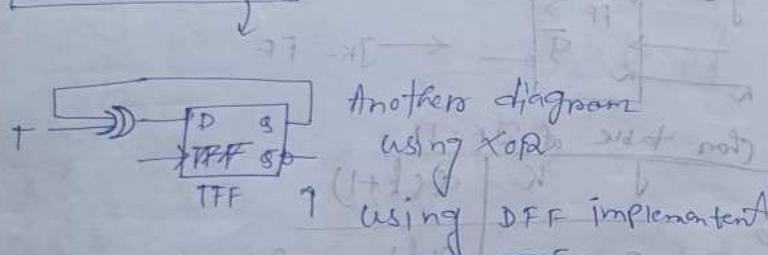


char. table of TFF


T	Q(T)
0	Q (hold)
1	Q (complement/toggle mode)

When $T = 1$, then toggle mode is present


Here also a clock

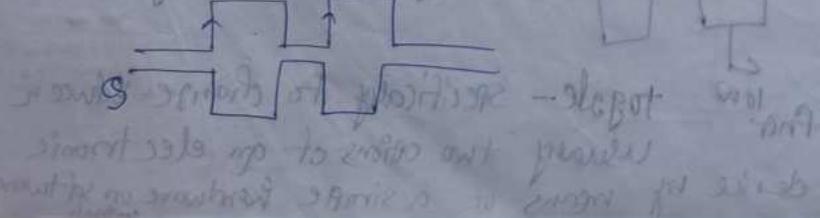

Symbol of TFF

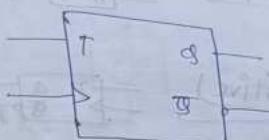

SR latch

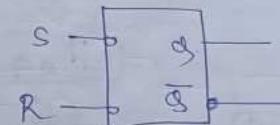


SR latch

(low logic)

(input low)

SR latch

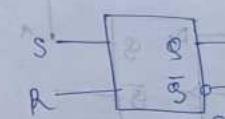


(high logic)
(input high)

Enable SR latch



A clock is present in flip flop


re edge sensitive DFF

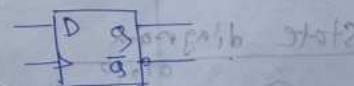


-re edge sensitive DFF




JK-FF (+ve edge sensitive)

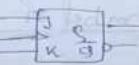

TFF (+ve edge sensitive)

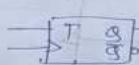


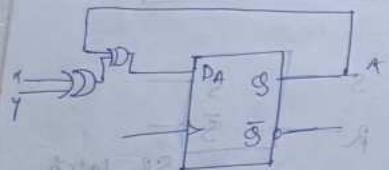How to implement this an using TFF
 $D(A+1) = A \oplus X \oplus Y = D_A$ (A = State, x, y = Input)
 [next state
 D_A = Assign this in DFF]




State table:


$A(t)$	X	Y	$A(t+1)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

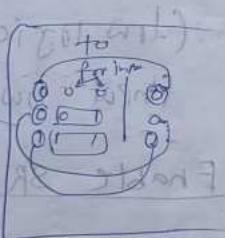


State diagram

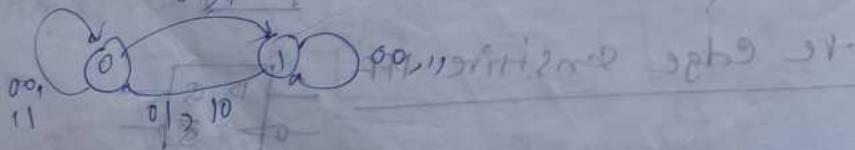



4-bit register

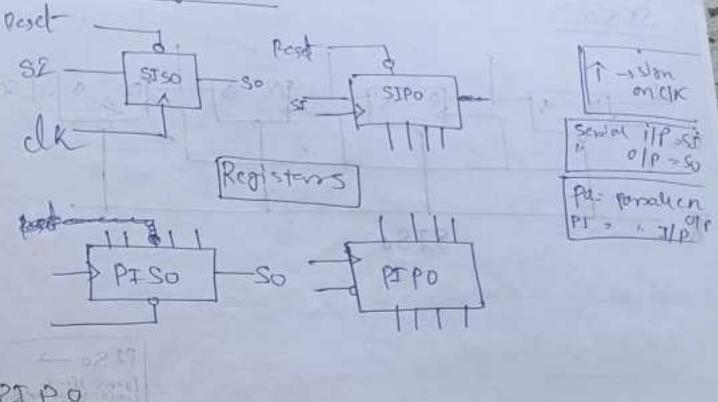

PIPO

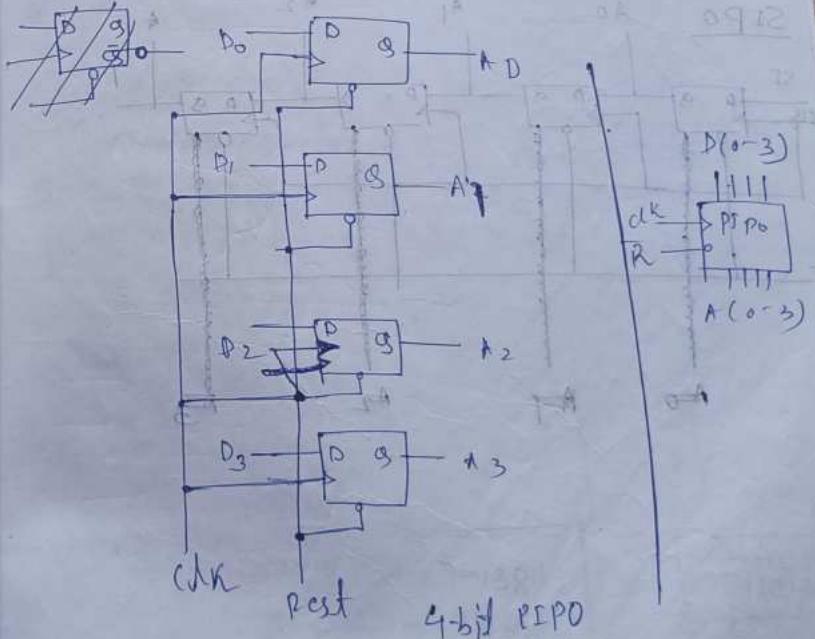


SISO

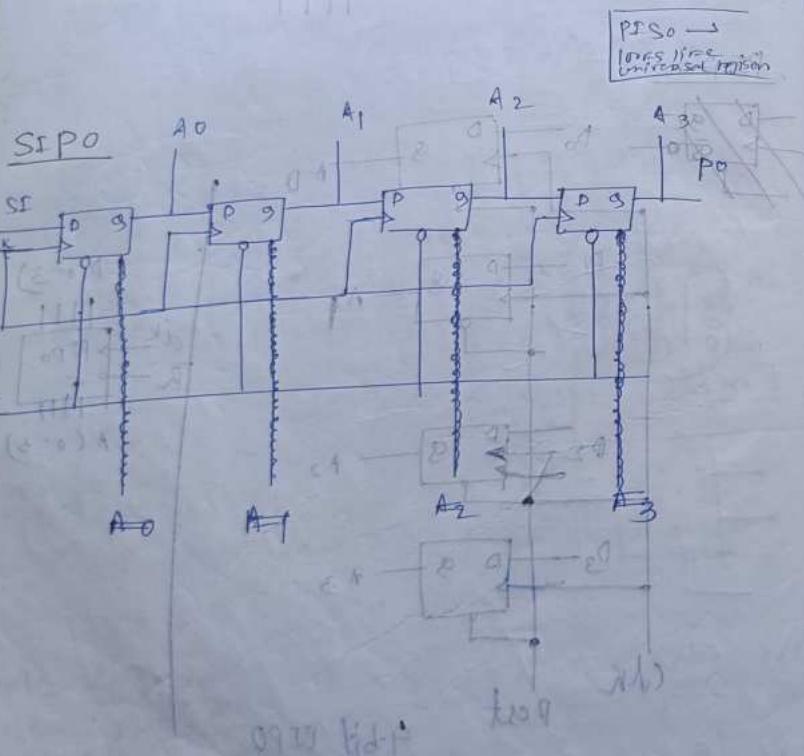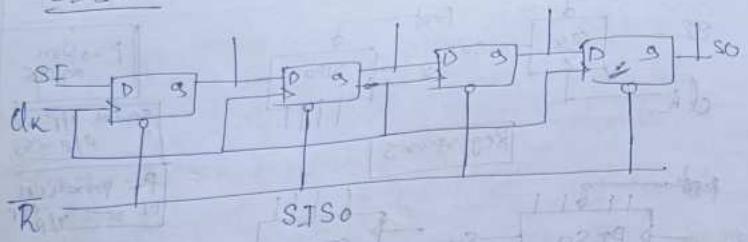

PISO →
long life
universal register

Universal registers

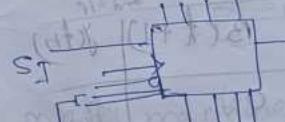

2 control
pin to
control
the operation

✓ 3:8 decoder → 8 → 74138

4 bit comparison → " → 7485

✓ 8:1 mux → 1 → 7415

✓ DFF → " → 7474

✓ 4:1 → 1, → 74153

✓ JFET logic state → 1, → 7476

in
Syllogism

Implementation of
Fin to table, state diagrams, circuit/machine

11/10/22

State eqn

$$A(t+1) = AB(t)x(t) + B(t)x(t) \quad [2\text{-bit state}]$$


$$B(t+1) = A'(t)x(t) \quad [4\text{ steps}]$$

[next step depends upon input]

$$A(t+1) = Ax + Bx \quad [A+B]x$$

$$B(t+1) = A'x \quad \} \text{ next step}$$

state diagram

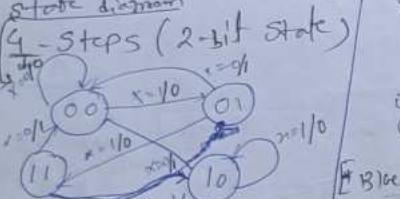

Defending upon the present state. What is next step
and output

A	B	X	A(t+1)	B(t+1)	y(t)
0	0	0	0	0111	0
0	0	1	0	1001	0
0	1	0	0	0111	0
1	0	1	1	1001	0
1	0	0	0	0111	1
1	0	1	0	0111	0
1	1	0	0	0111	0
1	1	1	1	1001	1


Present state

1. $y(t+1) = \text{output function}$
2. $y(t+1) = \text{output function}$
3. $y(t+1) = \text{output function}$
4. $y(t+1) = \text{output function}$


state table

output state machine


→ next state function
→ output function

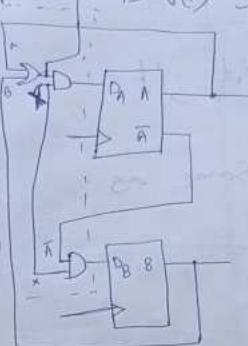

If $A(t+1) = Ax + Bx$
then

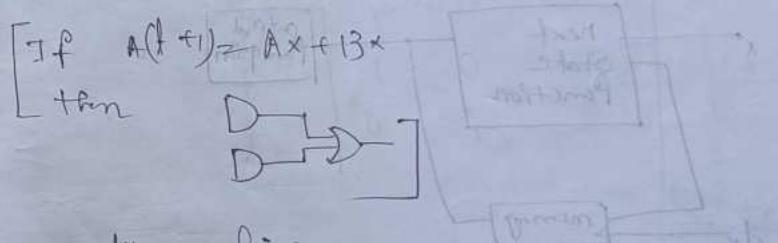

mealy machine

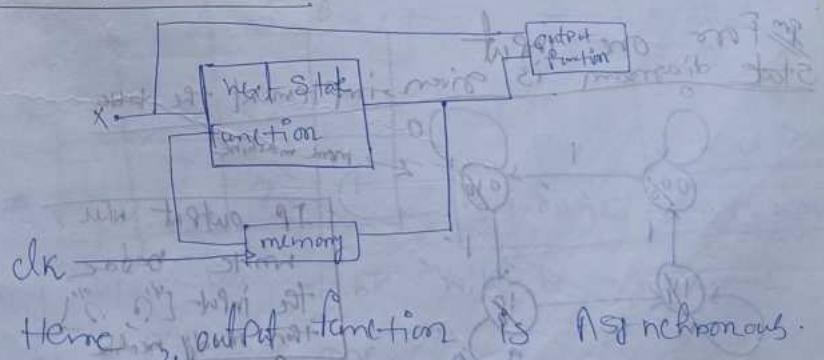


Hence, output function is asynchronous.
And output function depends & upon the
input & state

Morse machine


It don't depend upon input, it depends upon state only -
the eqns for this are same as previous except

$$Y(t+1) = A\bar{x} + Bx = (A+B)$$

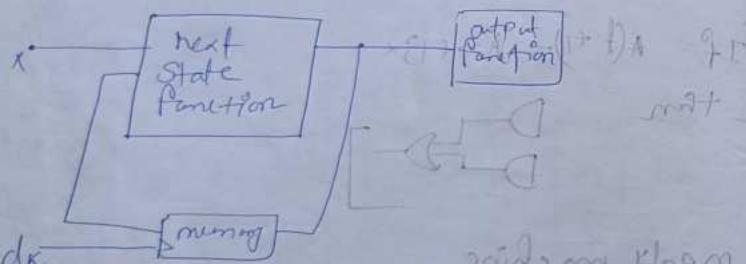

using D flip-flop

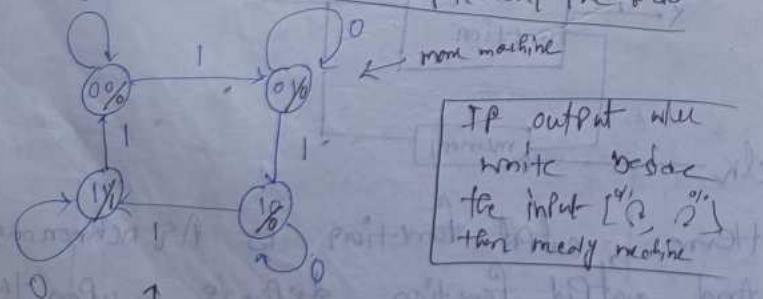For one input
State diagram is given, implement the table



If output will write below the input $[S_0, S_1]$ then morse machine

Output don't depend on input. Black x indicates the present state.

State table

Present State		x	A(t+1)				B(t+1)				Y(t+1)			
A	B		0	0	0	0	1	0	0	1	0	0	1	0
0	0	0	0	0	0	0	1	0	0	1	0	0	1	0
0	0	1	0	0	0	0	1	0	0	1	0	0	1	0
0	1	0	0	0	0	0	1	0	0	1	0	0	1	0
0	1	1	1	1	1	1	0	1	0	0	0	1	0	0
1	0	0	1	0	0	0	1	0	0	1	1	1	1	1
1	0	1	1	0	0	0	1	0	0	1	1	1	1	1
1	1	0	1	1	0	0	1	0	0	1	0	0	1	0
1	1	1	0	1	0	1	0	1	0	1	0	1	0	1

AB/x		S0	S1	S2	S3	B
0	0	0	1	0	0	
0	1	1	0	0	0	
1	0	0	1	0	1	
1	1	1	0	1	1	

excitation table of TFF
for A(t+1) | A
0 → 0 → 0
0 → 1 → 1
1 → 0 → 1
1 → 1 → 0

$$PA = A\bar{B} + \bar{A}\bar{B} + ABx + \bar{A}\bar{B}x$$

using DFF the table will be as same as that upper one.

DA will be implemented by the circuit diagram (machine)

	A	B	X
A	0	0	0
B	0	0	1
X	0	1	1


$$D_B = \bar{B}X + B\bar{X} \\ = B \oplus X$$

	B	B	X
A	0	0	0
X	0	0	1
	0	0	1

$$Y(t+1) = A \cdot B$$

Here v ~~is~~ output is not
dependent on X . So, its
more machine.

Circuit diagram -

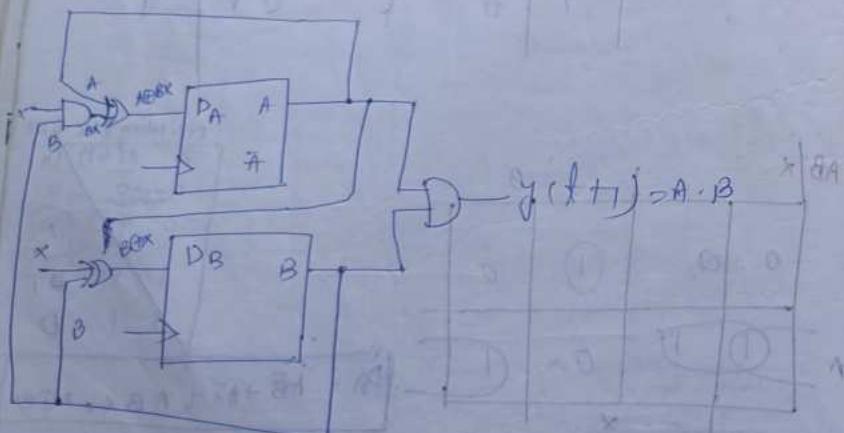

V-maps for (T_A, T_B)

	A	B	X
T_A	0	0	0
T_B	0	0	1
X	0	1	0


$$T_A = BX$$

$$T_B = X$$

output =

$$\text{more machine} \\ Y(t+1) = A \cdot B$$

Circuit diagram for (T_A, T_B)

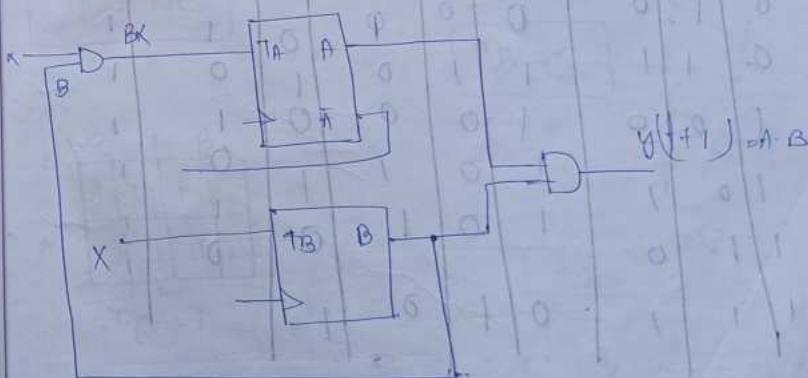

	A	B	X
T_A	0	0	0
T_B	0	0	1
X	0	1	0


$$T_A = BX \\ T_B = X$$

$$T_A = BX \\ T_B = X \\ Y(t+1) = A \cdot B$$

	A	B	X
T_A	0	1	0
T_B	1	0	1
X	0	1	1

$$T_A = BX \\ T_B = X \\ Y(t+1) = A \cdot B$$

Comparative DFF as well as DFF

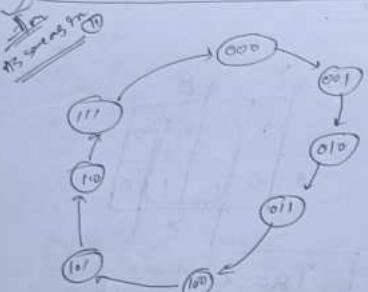

A	B	c	A(t+1) T _A	B(t+1) T _B	C(t+1) T _C
0	0	0	0 0	0 0	1 1
0	0	1	0 0	1 1	0 0
0	1	0	D 0	Φ 0	1 1
0	1	1	1 1	0 0	0 0
1	0	0	1 0	0 0	1 1
1	0	1	1 0	1 1	0 0
1	1	0	1 0	1 0	1 1
1	1	1	0 1	0 1	X

BC	B
0 0 1 0	
1 1 0 1	

$$P_A = AB + A\bar{C} + \bar{A}BC$$

$$P_A = A \oplus BC$$

BC	B
0 0 1 0	
0 1 0 1	

$$P_B = \bar{B}C + BC$$

$$P_B = B \oplus C$$

BC	B
1 0 0 0	
1 0 0 0	

$$D_C = \bar{B}\bar{C} + B\bar{C}$$

$$D_C = \bar{C}$$

for(T_A, T_B, T_C)

BC	B
0 0	1 0
0 0	1 0
0 1	0 0

$$T_A = BC$$

BC	B
0 0	1 1
0 0	1 1

$$T_B = C$$


BC	B
1 1 1 1	
1 1 1 1	

$$T_C = 1$$




rcf diagram (for T₀ T₁ T₂) [using DFF]

DFF

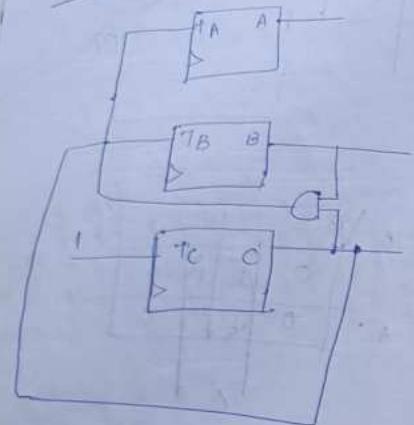

DFF₃

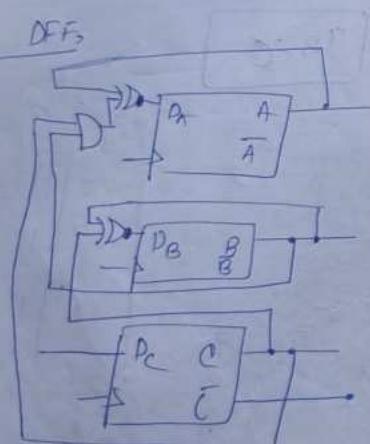

(reset) or



S0 = 101


S1 = 011

S2 = 100

S3 = 011

18/10/22
Parallel load and refresh (register)

load

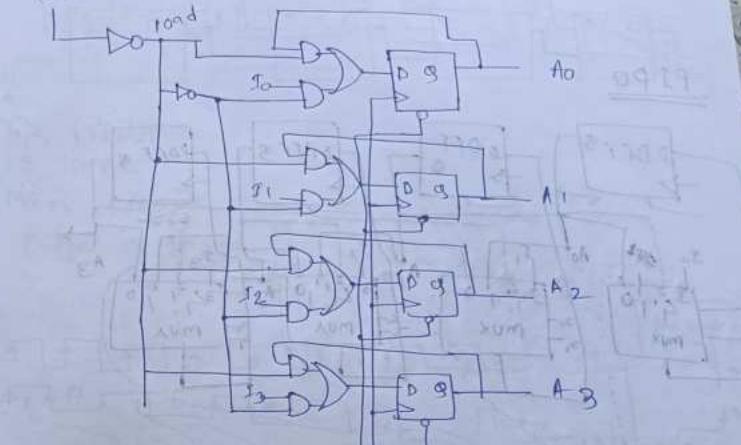

clear


clk

A0 + A1

The opposite of load is refresh

Universal register

Shift left + shift right

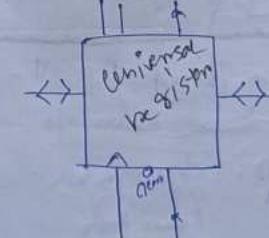

Refresh
shift + Right
shift + Left +
P2PO



S, S0

0 0


0 1

1 0


1 1

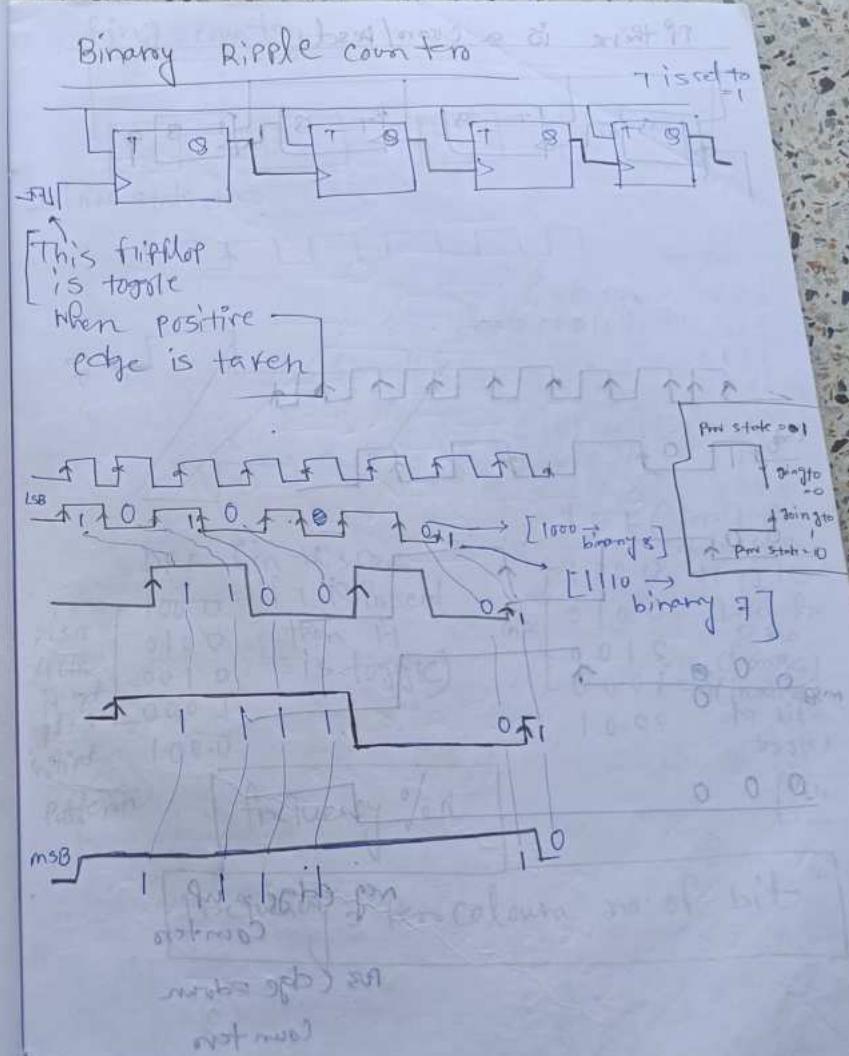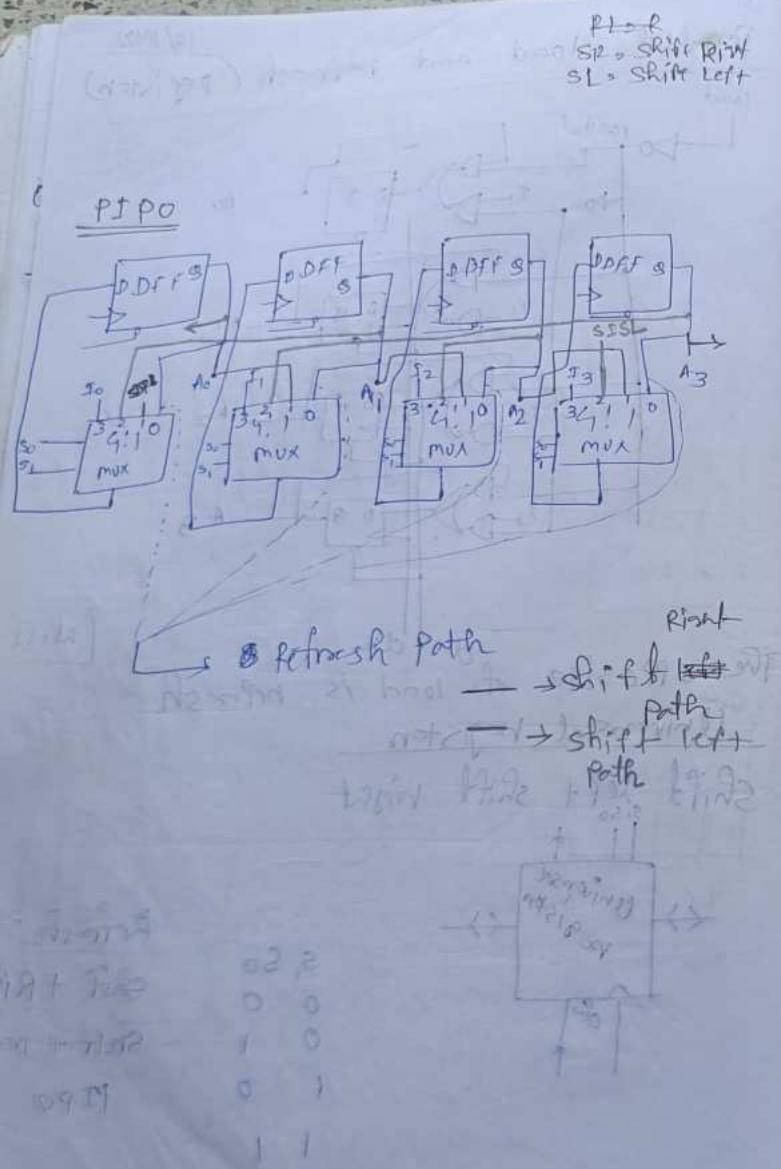

If there is a clear/preset

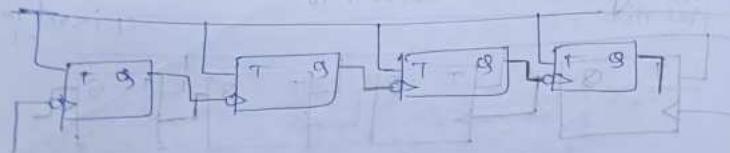

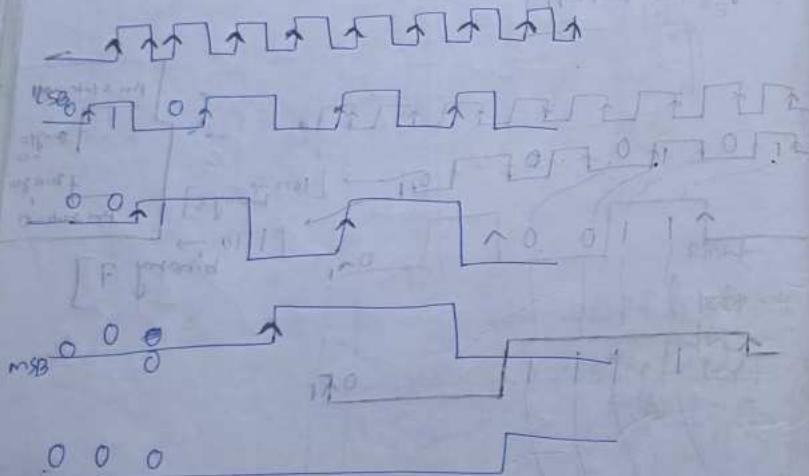
Initial state - 1000
1000 1001 1010 1011 1100 1101 1110 1111




neg edge = up
Counters

pos edge = down
Counters

Ring counter

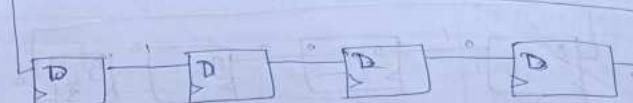

Initial state - 1000

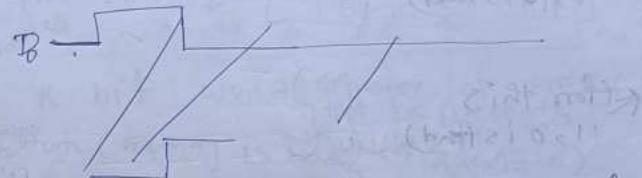


DFF (in this case
if 1 is present
then it
is toggle)
After 4 Cycles
it gets
1100
initial
pattern
1000

TFF (For 1 the
data will
1000 toggle
0100 and for
0 no
change)
case
1000 → (initial = 1
1st bit -
toggle)

frequency %

Frequency = per column no. of bit

Johnson Counter

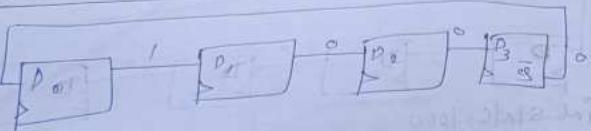

DFF

Look (for this)
1100 ↗ D₃ (0 is lead)

state
1110
0111 ↗ for this
0001 ↗ 0 is lead
0001
0000

input 0001
at bit 0 001
at bit 1 010
at bit 2 100
at bit 3 000
at bit 4 001
at bit 5 000


at bit 6 001
at bit 7 000
at bit 8 001
at bit 9 000
at bit 10 001
at bit 11 000
at bit 12 001
at bit 13 000
at bit 14 001
at bit 15 000

not present

lead to all inputs 0 and = present

③

Read only memory

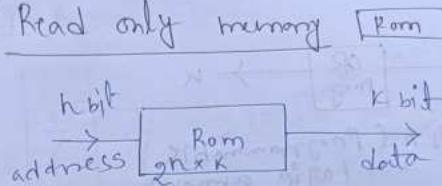

10/10/22

FPR Rom = Electrically
Erasable
Programmable
Rom
EEProm also exist.

n bit
address
is 1x
= 2^{10} byte [1 Byte = 8 bit]
= 1024 byte [bit of the data]

K bit word (sequence of 1 and 0 = word)
of Rom (memory is read data)


Programmable node (in sequence)

Basically it's sum of product form of logic function
you can read memory in any sequence






PROM (Programmable Rom)

Basically it is a decoder

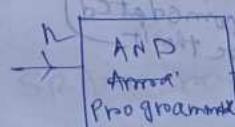

PAL (Programmable array logic)

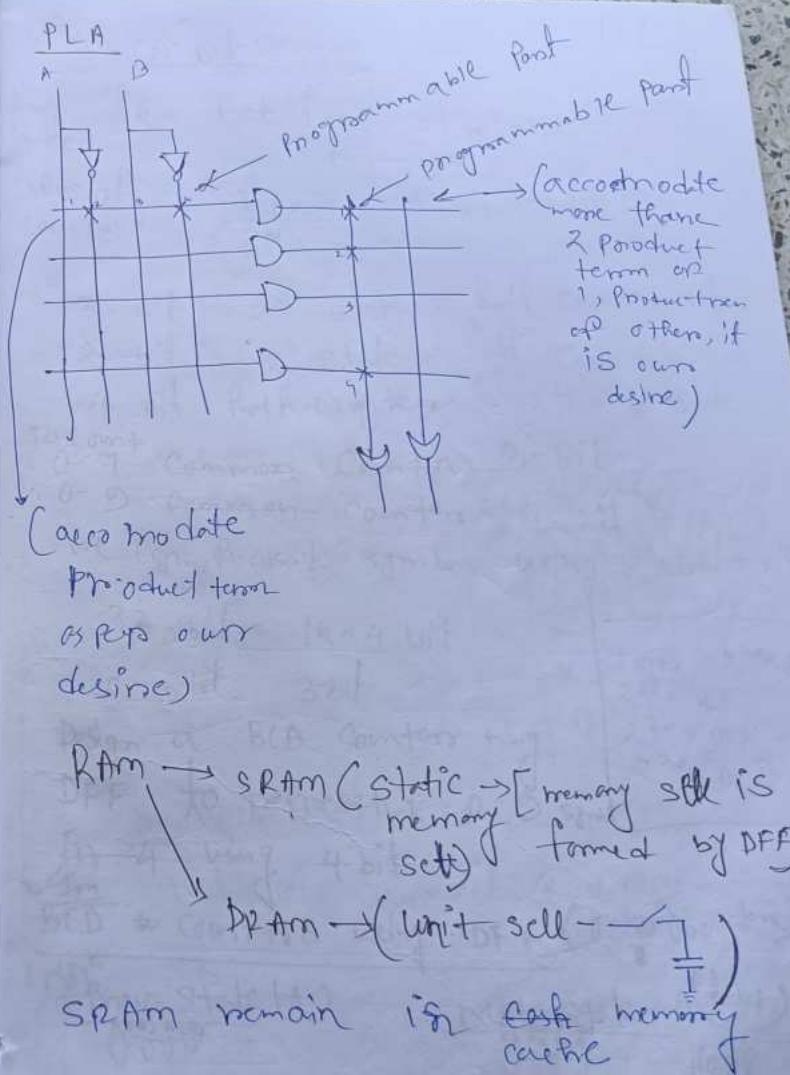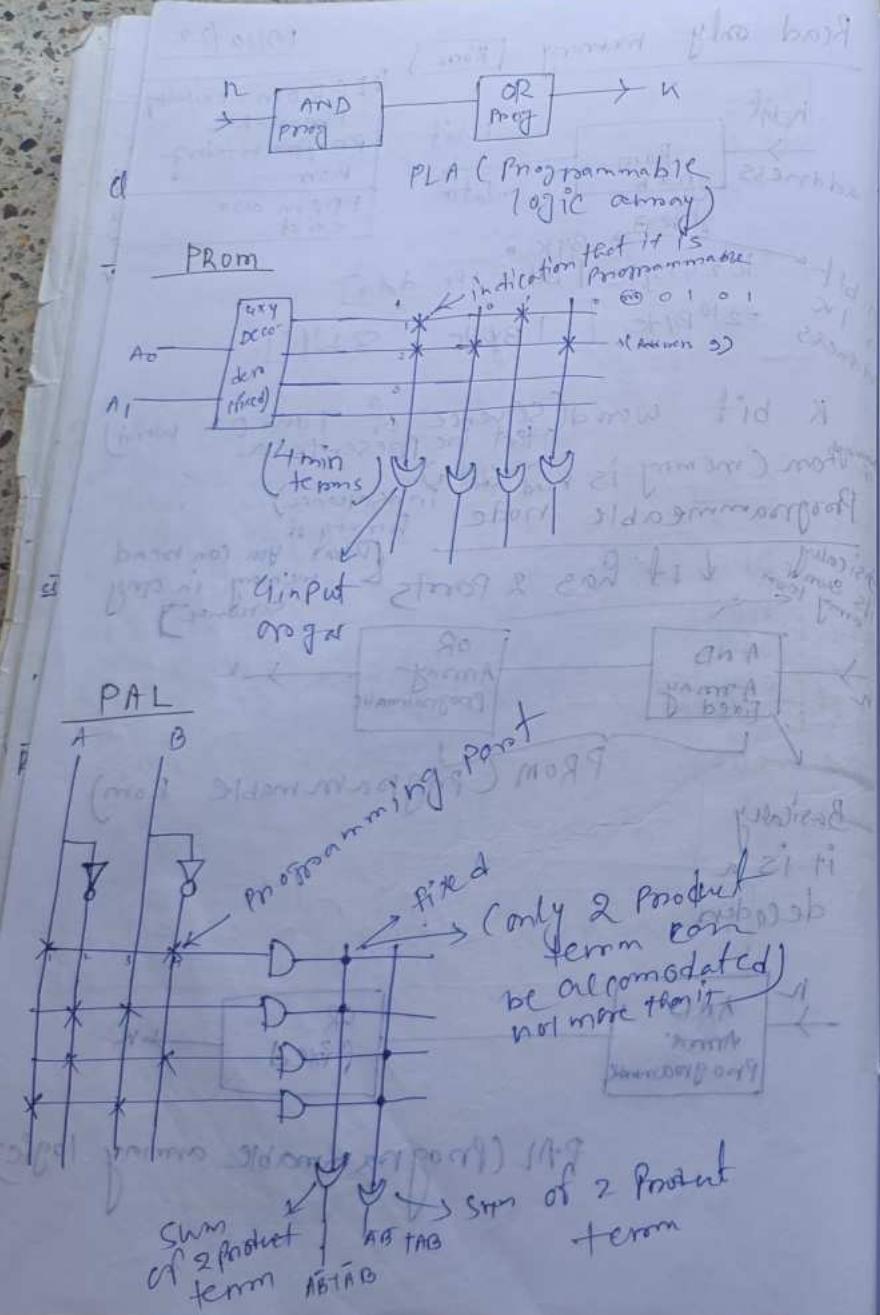

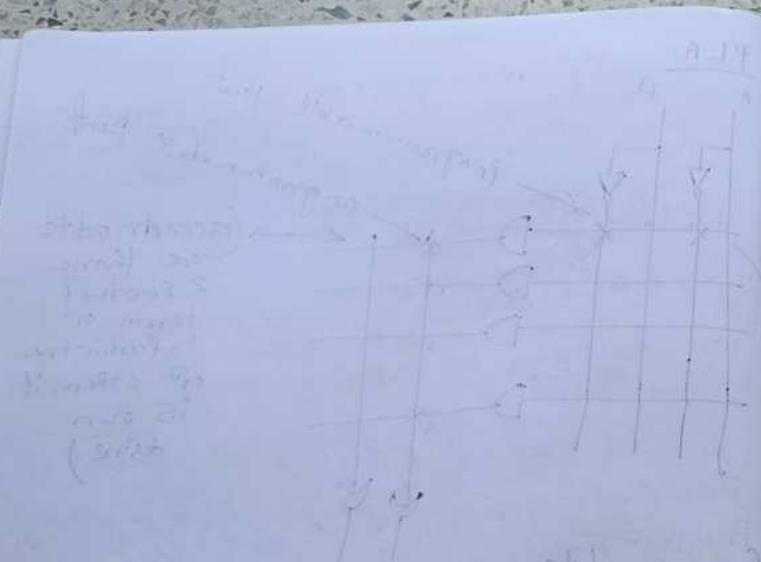

state 0110
next state 1111
000 0111
011 0000

21 We want to state (mt+32) ← mt9
0000 0000 0000 0000 0000 0000 0000 0000
0000 0000 0000 0000 0000 0000 0000 0000
0000 0000 0000 0000 0000 0000 0000 0000
0000 0000 0000 0000 0000 0000 0000 0000

Ring Counter

$$f_R = \frac{f_{clk}^N}{N} \quad (N \text{ states})$$

Johnson Counter

$$f_J = \frac{f_{clk}^N}{2N} \quad (2N \text{ states})$$

3-bit = 2^3 state = half counter set

2-bit = 2^2 state = half counter set

4-bit half Counter = $2^4 = 16$ State

To Count

" 0-7 Common Counter = 3-bit

" 0-9 Common Counter = 4-bit

We can represent symbol using 8 bit = 2^8 up

32 symbol = 16×2 bit

0-5 bit = 3-bit

Design a BCD Counter using DFF

to represent 0-9 symbol

in 4 using 4-bit

BCD to counters using DFF (0-9 counter)

Prev State (A)	Next State A(t+1)	Comp
0000	0001	0 → 1
0001	0010	0 → 0
0010	0011	0 → 0
0011	0100	9 → 0
0100	0101	
0101	0110	

	0 110	0 111	1 000	1 001
d	0 111	1 000	1 001	0 110
	1 000	1 001	0 110	0 111
	1 001	0 110	0 111	1 000
	0 110	0 111	1 000	1 001

1 010 undefined state

1 011 xxxx don't care

1 100 xxxx don't care

1 101 xxxx don't care

1 111 xxxx don't care


Using DFF			
A ₃	A ₂	A ₁	A ₀
0	0	0	0
0	0	0	0
x	x	x	A ₁ = x + A ₂ A ₃ + A ₃ A ₀
A ₃	D	0	X
	A ₀	D = A ₃ A ₂ + A ₂ A ₁ + A ₁ A ₀	

D=0 Q=0 C, DFF & TFF both present

D=1 Q=1

How to move 0 from 0 is called
excitation table to given state at Q₀

Q ₁	T=0	T=1	Q ₀	(A) State with 0's
0	0	1	0	0000
0	1	0	1	1000 TFF
0	0	0	0	0000
1	1	0	1	1010
1	0	1	0	0110
1	1	1	1	1010
0	1	1	0	0110
0	0	0	1	1010

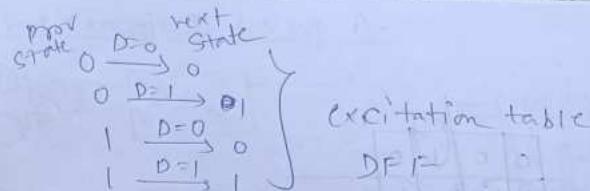

In case of TFF we have to use slow table

	T ₃	T ₂	T ₁	T ₀
0	0	0	1	1
0	0	1	1	1
0	0	0	1	1
0	0	1	1	1
0	0	0	1	1
0	0	1	1	1
0	0	0	1	1
0	0	0	0	1
1	0	0	0	1
1	0	1	1	1
0	0	0	0	1
1	0	0	1	1

All 0 and don't care = T₀ = 1

Slow table

	T ₃	T ₂	T ₁	T ₀
0	x	x	x	x
0	x	x	x	x
0	x	x	x	x
1	x	x	x	x
1	x	x	x	x
0	x	x	x	x
0	x	x	x	x
1	x	x	x	x
1	x	x	x	x

	A_3	A_2	A_1	A_0
D_0	1	0	0	1
	x	x	x	x
	1	0	x	x
	1	0	x	x

$D_0 = (A_2 \bar{A}_0) + (\bar{A}_0 \bar{A}_2)$


	A_3	A_2	A_1	A_0
D_1	0	1	0	1
	x	x	x	x
	0	0	x	x
	0	1	x	x

$D_1 = () + ()$

	A_3	A_2	A_1	A_0
D_2	0	0	1	0
	1	1	0	1
	x	x	x	x
	0	0	x	x



$D_2 = () + ()$

Implement D using A -

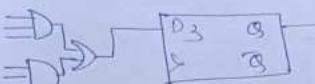



Complexity

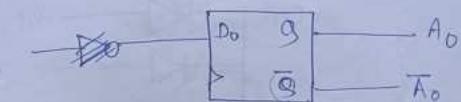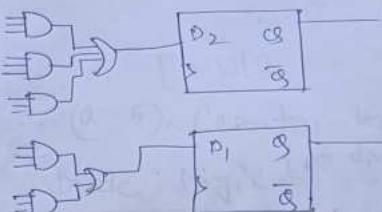7 AND gates (3 if AND gates),
3 OR gates
(R, 3 - inorgate)
4 DFF



Implement X using A -

using TFF

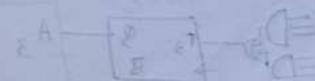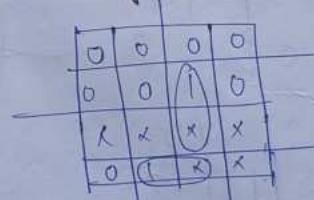


$$T_3 = () + ()$$

	A_3	A_2	A_1	A_0
T_3	0	0	0	0
	0	0	1	0
	x	x	x	x
	0	1	x	x




	A_3	A_2	A_1	A_0
T_2	0	0	0	0
	0	0	1	0
	x	x	x	x
	0	1	x	x

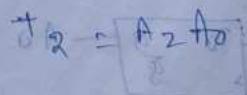

A₂ gives 36 from 1001

0	1	1	0
0	1	1	0
X	X	X	X
A ₃	0	0	X

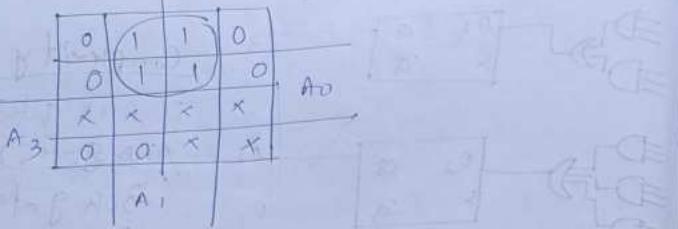

$$T_1 = \bar{A}_3 A_0$$

$$T_0 = 1 \text{ As all are } 1.$$

Complexity




4 AND gate

1 OR gate

Implement T using A



0	0	0	0
0	1	0	0
X	X	X	X
X	0	0	0

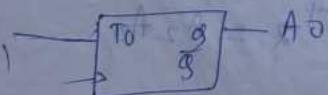
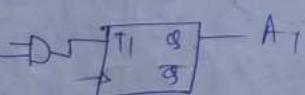
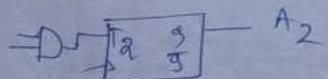



HNL [3-bit]

(0-5) n Counters using DFF / TFF

Diode logic (no deadline, But nstop)

Droop = 0.7V = (at in voltage)

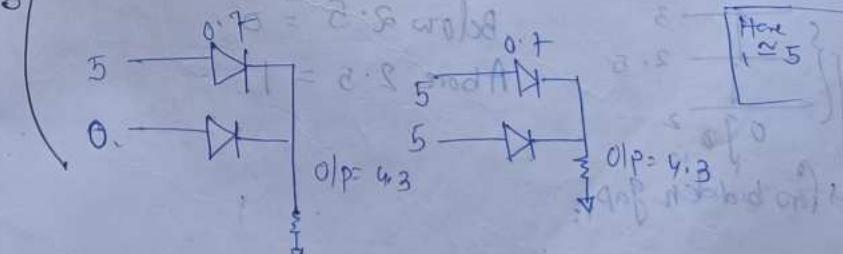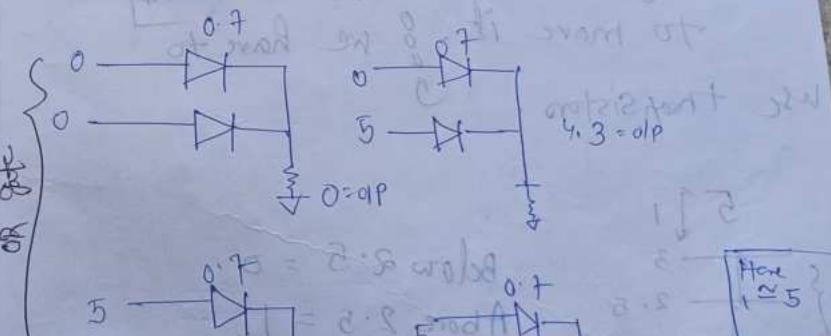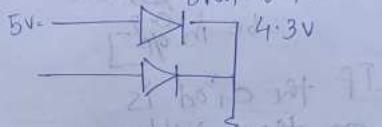

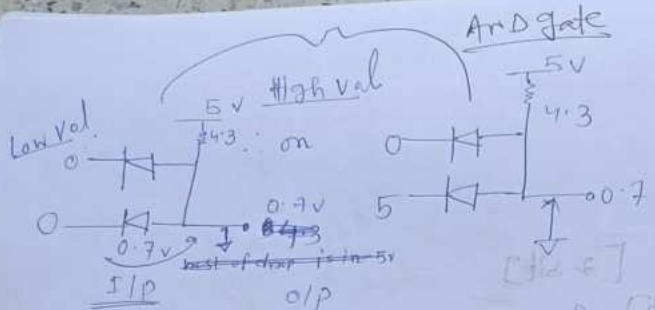

$(\text{on}) \quad 0 \quad 0 \quad 0.7$

$0 \quad 5 \quad (\text{off}) \quad 0.7$


$5 \quad 0 \quad 0.7$

$5 \quad 5 \quad 5$

If any path is shorted then it will be in $0.7V$

If the diod is on then voltage will be divided

To move it we have to use transistors

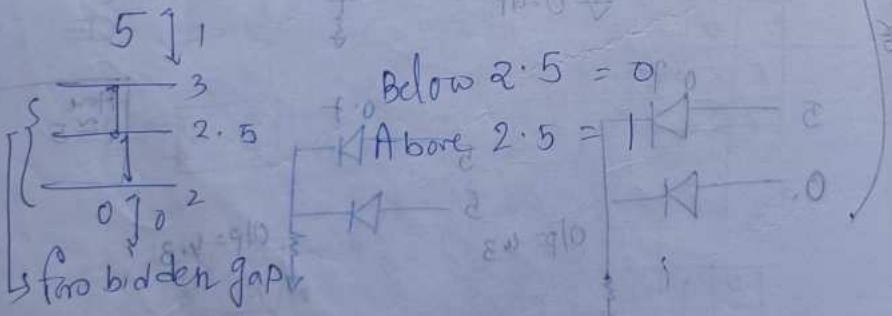

PL Prev Year Qn

Q) How do you compare the following numbers?

a) $(1.10)_2$,

b) $(1.10)_5$,

c) $(1.10)_8$,

d) $(1.10)_{10}$,

e) $(1.10)_{16}$.

→ add more weight at lower bits

→ shorter form hence $2^{10} < 2^8$

→ $2^{10} > 2^8$

→ $2^{10} > 2^8$

Comparison between the following numbers

The 1st one is in binary

The 2nd one is

1st 3rd , , , octal

2nd 4th , , , decimal

3rd 5th , , , hexadecimal

a) $(1.10)_2 = 2^0 + 2^{-1} = 1 + 0.5 = (1.5)_{10}$

b) $(1.10)_5 = 5^0 + 5^{-1} = 1 + 0.2 = (1.2)_{10}$

c) $(1.10)_8 = 8^0 + 8^{-1} = 1 + 0.125 = (1.125)_{10}$

d) $(1.10)_{10} = 1 + 10^{-1} = (1.10)_{10}$ (it is in decimal already)

e) $(1.10)_{16} = 16^0 + 16^{-1} = 1 + 0.0625 = (1.0625)_{10}$

$\begin{array}{r} 16^0 \\ 16^{-1} \\ \hline 1 + 0.0625 \end{array}$

$\begin{array}{r} 16^0 \\ 16^{-1} \\ \hline 1 + 0.0625 \end{array}$

$\begin{array}{r} 16^0 \\ 16^{-1} \\ \hline 1 + 0.0625 \end{array}$

$\begin{array}{r} 16^0 \\ 16^{-1} \\ \hline 1 + 0.0625 \end{array}$

- 2) Represent the decimal number (-25)₁₀ into
- 8-bits signed magnitude form.
 - 8-bits signed 1's complement form
 - 8-bits signed 2's complement form.

a)

$$\begin{array}{r} 0.0 \quad 0 \quad 1 \quad 1 \quad 00 \quad 1 \\ \hline 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \quad 1 \end{array}$$

$-25 = 0.0011001$

b) $(-25)_{1's} = 11100110$

c) $(-25)_{2's} = 11100111$

- 3) Perform the addition in BCD code of 2 numbers 875 and 653.

$875 + 653 = 101101110101$

$$\begin{array}{r} 875 \\ + 653 \\ \hline 1528 \end{array}$$

$$\begin{array}{r} 1000 \quad 0111 \quad 0101 \\ + 0110 \quad 0100 \quad 0111 \\ \hline 1110 \quad 1100 \quad 1000 \\ + 0110 \quad 0110 \\ \hline 0001 \\ \hline 10101 \quad 0010 \quad 1000 \end{array}$$

[If you want to remove a term from multiplying outside the (abc) or $(a\bar{c})$ brackets]

- u) Prove the equality, $ab + \bar{a}c = (a+c)(\bar{a}+b)$

LHS

$$\begin{aligned} & ab + \bar{a}c \\ &= ab(c + \bar{c}) + \bar{a}c(b + \bar{b}) \\ &= abc + ab\bar{c} + \bar{a}bc + \bar{a}\bar{b}c \\ &= bc(a + \bar{a}) + \end{aligned}$$

$$\begin{aligned} & LHS \\ & ab + \bar{a}c \\ &= (ab + \bar{a}) \\ &= (\bar{a} + b) \\ &= (a + b) \end{aligned}$$

RHS


$$\begin{aligned} & (a+c)(\bar{a}+b) \\ &= ab + \bar{a}c + bc \end{aligned}$$

$$\begin{aligned} & LHS \\ & ab + \bar{a}c \\ &= (a + \bar{a})(\bar{a} + b) \\ &= ab + \bar{a}b + \bar{a}c + bc \\ &= ab + \bar{a}b + \bar{a}c + bc \\ &= ab + \bar{a}c + bc \end{aligned}$$

a	b	c	$a \cdot b$	\bar{a}	$\bar{a} \cdot c$	$a + \bar{a}$	$\bar{a} + b$	P.g	x+y
0	0	0	0	1	0	1	1	0	0
0	0	1	0	1	0	1	1	1	1
0	1	0	0	1	1	1	1	1	1
1	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	1	0	0	1
1	1	0	1	0	0	1	1	1	1
1	1	1	1	0	1	1	1	1	1

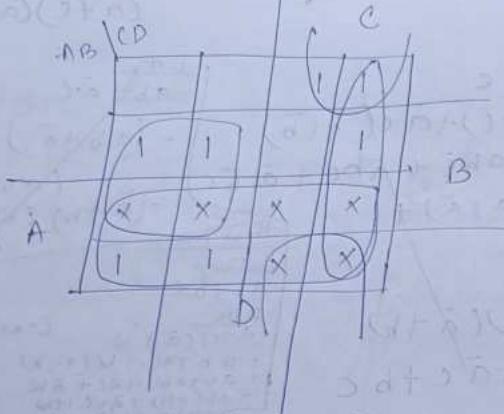- 5) Draw the K-map, solve and implement a Optimum circuit of the following function.


$$G_2 = \sum_m (2, 3, 4, 5, 6, 8, 9) + \sum_d (10, 11, 12, 13, 14, 15)$$



$$F = A + \overline{B}C + \overline{C}\overline{D} + \overline{B}\overline{C}$$

$$= A + \overline{B}C + B\overline{C} + \overline{C}\overline{D}$$

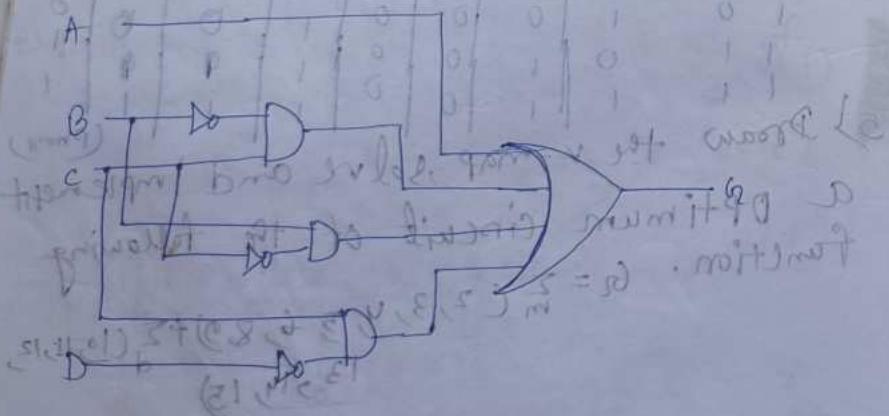the final form for this is $G = A + \overline{B}C + B\overline{C} + \overline{C}\overline{D}$



Q) Perform the subtraction ($P-Q$) in 2's complement form, where $P=11100101$ and $Q=11101101$.

$$\begin{array}{r} 11100101 \\ 11101101 \end{array} \rightarrow P = 229 \quad \rightarrow Q = 237$$

$$\begin{array}{r} 237 = 11101101 \\ - 237 = 00010011 \\ \hline \text{now,} & 11100101 \\ & - 11101101 \\ \hline & 01010010 \end{array} \quad \begin{array}{l} P-Q \\ 11100101 \\ - 11101101 \\ \hline 01010010 \end{array}$$

∴ the result of $P-Q$ in 2's complement

$$237 = 11101101$$

$$\downarrow 2^7 S$$

$$-237 = 00010011$$

∴ now,

$$\begin{array}{r} 11100101 \\ 00010011 \\ \hline 11110000 \end{array}$$

$$\downarrow 2^7 S$$

$$-00001000 (-8)$$

∴ the result is -00001000
magnitude = $-00001000 = (-8)$

7. Design a full-subtractor using two

4:1 multiplexers.


full substitution.

$$\begin{array}{ccccccccc} & 0 & 0 & 0 & 0 & 1 & 1 & 1 \\ \text{R(B) ini} & 0 & 0 & -1 & -1 & 0 & 0 & 1 \\ \text{BD} & 00 & 11 & 11 & 10 & 01 & 02 & 11 \end{array}$$

↙ same ↘ difference

x	y	z	w	B	D	
0	0	0	0	0	0	
0	0	1	0	1	10110111	= PES
0	1	1	0	11111111	10010000	= PES
0	1	1	1	11111111	10010000	= PES
1	0	0	0	01111111	01000011	
1	0	1	0	01111111	01000011	
1	1	1	1	11111111	11111111	

K-maps

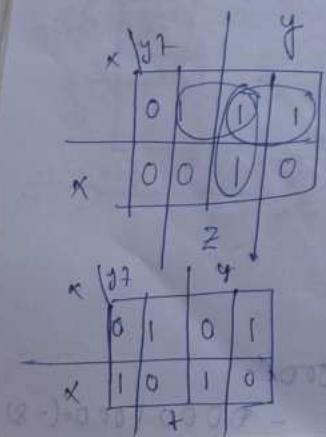


$$B = -x^2 + y^2 + 1$$


$$B = \frac{-x^2 + y^2 + 1}{11110000}$$

DE & DJ 710000-
100000 = 21 then add
shorter

Cytodiagnose

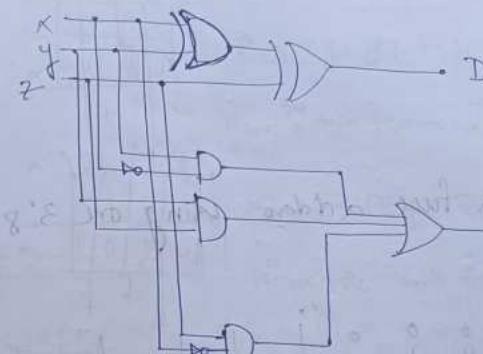


Symbol-

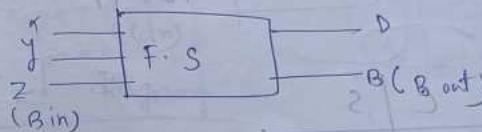


full subtractor using 2, 4:1 multiplexers

	T_0	T_1	T_2	T_3
T_0	0	1	1	1
T_1	0	0	0	1
T_2	0	1	1	1
T_3	1	1	1	1

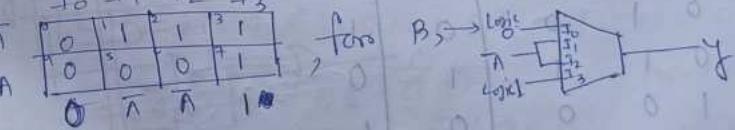



	T_1	T_2	T_3
T_1	0	1	1
T_2	1	0	1

四

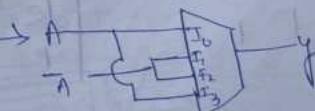

8) Design a full adder using one 3:8 decoder.

full adder

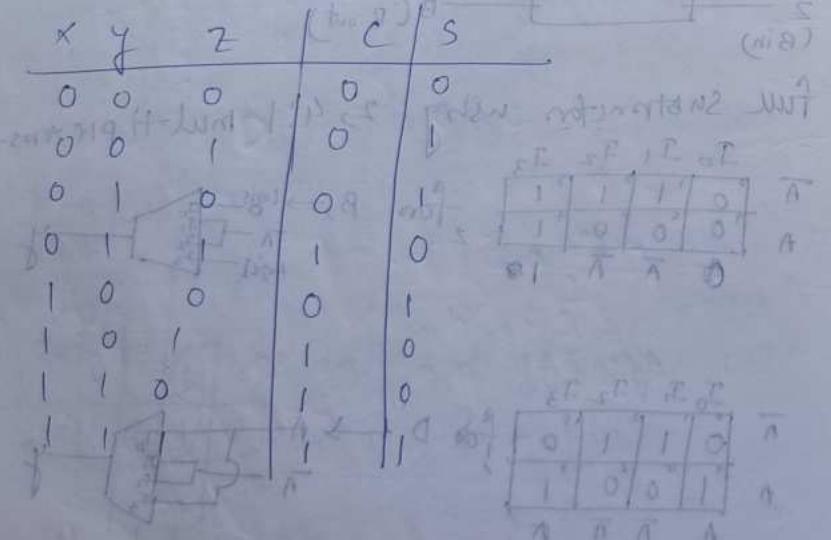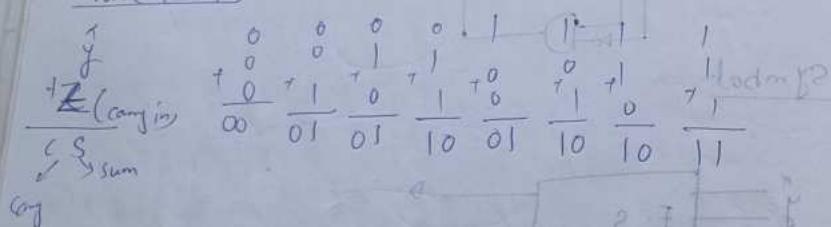

K-maps

x	y	z	0	0	1	1
x	y	z	0	0	0	1
x	y	z	0	1	0	1

$$C = \bar{x}\bar{y} + \bar{x}y + x\bar{y}$$

Hence the min terms are $\Sigma_m(3, 5, 6, 7)$

x	y	z	0	1	0	1
x	y	z	0	1	0	0
x	y	z	1	0	1	0


$$S = x\bar{y} + \bar{y}z + xz$$

Hence the min terms are $\Sigma_m(1, 2, 4, 7)$


Symbol



Ort diagram

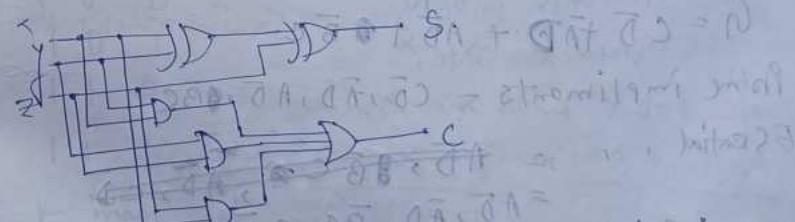


a full adder using one 3:8 decoder

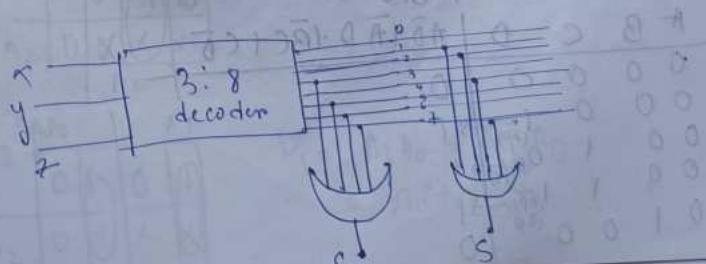

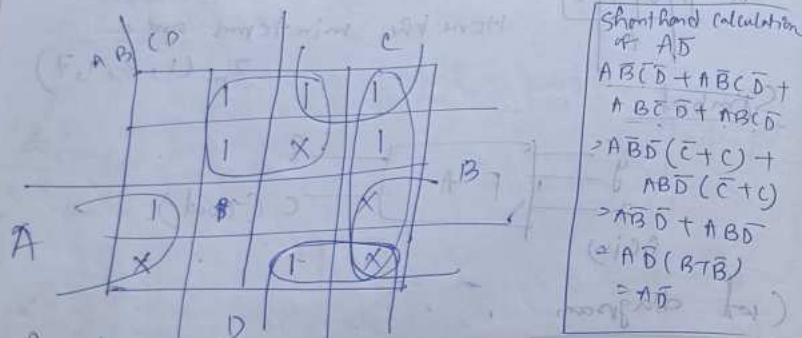9) Solve the prime implicants using Kmap and draw essential prime implicants table of the following.

$$G = \sum_m (1, 2, 3, 5, 6, 11, 12) + \sum_d (7, 8, 10, 14)$$



the function is,

$$G = \bar{C}\bar{D} + \bar{A}\bar{D} + \bar{A}\bar{B}\bar{C}$$

Prime implicants - $\bar{C}\bar{D}$, $\bar{A}\bar{D}$, $\bar{A}\bar{B}\bar{C}$

$$\begin{aligned} \text{Essential } \text{PI} &= \bar{A}\bar{D}, \bar{B}\bar{C} \\ &= \bar{A}\bar{D}, \bar{A}\bar{D}, \bar{B}\bar{C}, \bar{C}\bar{D} \end{aligned}$$

Essential prime implement = $\bar{A}\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{C} + \bar{C}\bar{D}$

table-

A	B	C	D	$\bar{A}\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{C} + \bar{C}\bar{D}$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	0

0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

table is

E.P.F

10) Design a up counter using DFF that repeats the sequence 000, 001, 010, 011, 100 in infinite loop.

BCD UP counters using DFF to represent 0-4 symbol using 3-bit -

A_2	A_1	A_0	$[A(t)]$	D_2	P_1	D_0	$[A(t+1)]$
0	0	0	000	0	0	1	[001]
0	0	1	001	0	1	0	[010]
0	1	0	010	0	1	0	[011]
0	1	1	011	1	0	0	[100]

1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1
1	1	0	1	0	1	0	1
1	1	0	1	1	0	0	1
1	1	1	1	1	0	0	1


K-maps

D_2	P_2	$A_1 A_0$	A_1
0	0	0 0	0
0	1	0 1	1

$$P_2 = A_1 A_0$$


D_1	A_2	$A_1 A_0$	A_1
1	0	0 1	1
1	1	0 0	0
0	0	1 0	0
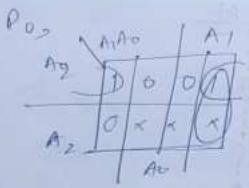
$$\begin{aligned} P_1 &= A_1 \bar{A}_0 + \bar{A}_1 A_0 \\ &\Rightarrow A_1 (+) A_0 \end{aligned}$$



$$D_0 = A_1 \bar{A}_0 + \bar{A}_2 \bar{A}_0$$

Implementation

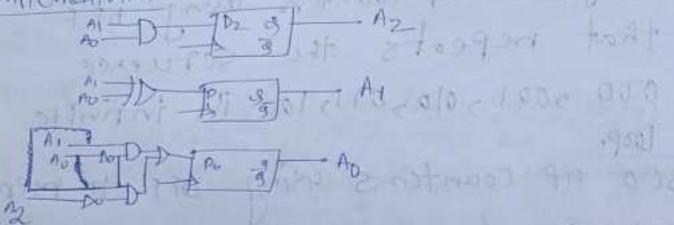

Complexity - 4 AND, 1 OR, 1 XOR, 3 DFF

Q1 Design a State machine using TFF that implements a 2-bit down counter when input $x=1$, otherwise holds its current state.

State table with excitation table -

Present State		Next State		Excitation	
				A_2	A_1
0 0		0 1	1 0	1	1
0 1		0 0	0 1	0	1
1 0		0 1	1 1	1	0
1 1		1 1	0 0	0	0

K-map


T_2	Q_2
0	0 0
1	1 0

$$T_2 = \bar{Q}_1$$

T_1	Q_1
0	1 1
1	1 1

$$T_1 = 1$$

Implementation

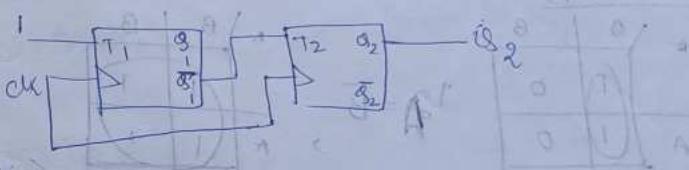

(Q1)

$A_2 \ A_1 \ [A_1 \oplus]$ Present State $A_2 \ A_1 \ [A_1 \oplus]$ Next State $T_2 \ T_1$

0 0	1 1	1 1
0 1	0 0	0 0
1 0	0 1	1 0
1 1	1 1	1 1


Implementation of State machine

(Q2)


P.T.O

Present State		next state			
A	B	A(H1)	B(H1)	T _A	T _B
0	0	1	1	1	1
0	1	0	0	0	1
1	0	0	1	1	1
1	1	1	0	0	1

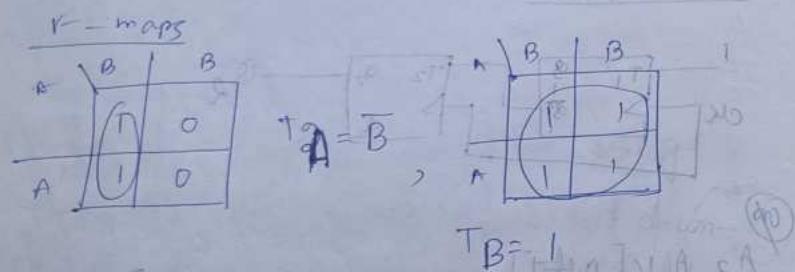
K-maps as same as previous
Implementation of state diagram



Implementation of State diagram machine

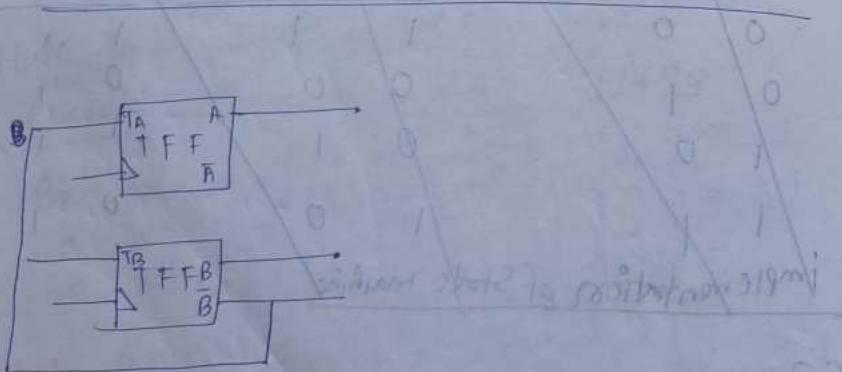

FIFO
state diagram

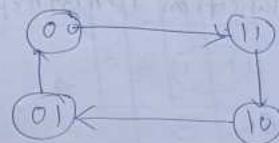

(00) in and out




0	1	1	0
1	1	0	0

DL Previous Years Ques (2021)


↓ minimize the Boolean function $F = AB + A'C + BC$

$$\begin{aligned} F &= AB + A'C + BC(A+A') \\ &\Rightarrow AB + A'C + ABC + A'BC \\ &\Rightarrow AB + ABC + A'C + A'BC \\ &= AB(C+1) + A'C(1+B) \\ &\Rightarrow AB + A'C \end{aligned}$$

the func is $= AB + A'C$

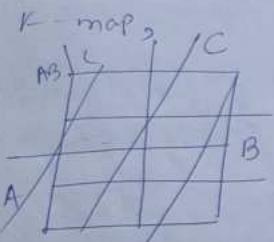

$$\text{for SOP} = F = AB + A'C + BC$$

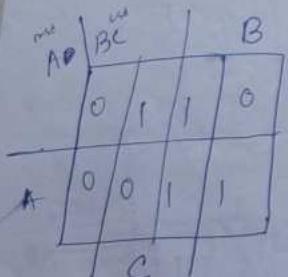

$$\begin{aligned} \text{the sum (sum of minterms)} \\ &= \sum_m (1, 3, 5, 7) \end{aligned}$$

$$\begin{aligned} \text{other process, } F(A, B, C) &= AB(C+C') + \\ &A'C(B+B') + \\ &BC(A+A') \end{aligned}$$

$$\begin{aligned} &\Rightarrow ABC + AB'C + A'BC + A'B'C + ABC + A'B'C \\ &\Rightarrow ABC + A'BC + A'BC + A'B'C \\ &= \sum_m (1, 3, 5, 7) + \sum_m (6, 7) \end{aligned}$$

$$\therefore F = \sum_m (1, 3, 5, 7) + \sum_m (6, 7)$$

		B		C	
		0	1	0	1
A	0	1	1	0	0
	1	0	0	1	1

$$F = A'C + AB$$


other process,

$$\begin{aligned} F &= AB + A'C + BC(A+A') \\ &= AB + A'C \end{aligned}$$

$$\Rightarrow F = AB + A'C + BC$$

$$\begin{aligned} F &= \sum_m (1, 3, 5, 7) [\text{SOP}] \\ &= \sum_m (0, 2, 4, 5) [\text{POM}] \end{aligned}$$

other process,

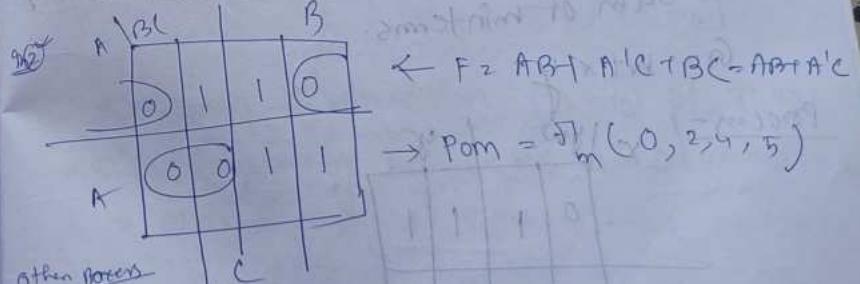

$$\rightarrow \text{POM} = \sum_m (0, 2, 4, 5)$$

other process

$$F = \overline{AC} + AB$$

$$F = \overline{AC} \cdot \overline{AB}$$

$$\Rightarrow (\overline{AC}) \cdot (\overline{AB})$$

$$\Rightarrow (A+C) \cdot (A+B)$$

$$\begin{aligned} \text{the pos is } &= (A+C) \cdot (A+B) \\ F &= \overline{A} \cdot \overline{C} \end{aligned}$$

The other process to get \oplus sum -

$$F(A, B, C) = (A+C)(\bar{A}+B) \quad [\text{POS}]$$

$$(A+B\bar{B}+C) \cdot (\bar{A}+B+\bar{C}\bar{C})$$

$$= (A+C+B) (\bar{A}+\bar{B}+0) (\bar{A}+\bar{B}+\bar{C})$$

$$(\bar{A}+\bar{B}+\bar{C})$$

$$= m_6 \cdot m_2 \cdot m_5 \cdot m_4$$

$$\therefore F = \prod_{m_i} (0, 2, 4, 5)$$

2) Express the Boolean function $g_2 = A'B'C'$ as product of maxterms.
done (a)


3) Express the Boolean function $g_2 = wxy$ as sum of minterms.

$$g_2 = w + x'y$$

		x	y	w	g_2
		0	1	0	0
x	0	0	1	1	1
		1	0	0	0
		1	1	0	0

$$g_2 = \sum (1, 2, 3, 5, 7) \quad [\text{Sum}]$$

Process - II

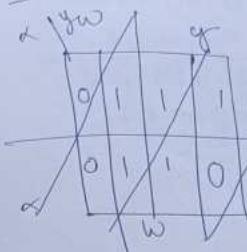

$$g_2 = w + x'y \quad (\text{Sop})$$

$$= w(x'+x)(y'+y) + x'y(w+y)$$

$$= \emptyset w [x'y + xy + xy' + xy] + x'yw + x'yw'$$

$$= x'yw + x'yw + xyw + x'yw + x'yw$$

$$= m_1 + m_3 + m_5 + m_2 + m_7$$

$$\therefore g_2 = \sum (1, 2, 3, 5, 7) \quad [\text{Sum}]$$

4) Perform subtraction $(A - B)$ of two unsigned binary numbers $A = 010010$ and $B = 010100$ using 2's complement method.

$$A = 010010$$

$$B = 010100$$

$$010100 \downarrow \text{2's complement}$$

$$B' = 101010$$

$$\begin{array}{r} 12 \\ -14 \\ \hline -2 \end{array}$$

: A - B is

$$\begin{array}{r} 010\ 010 \\ 101\ 100 \\ \hline 1\ 1\ 1\ 110 \end{array}$$

↓ 2's complement

$$-000\ 010 \quad (-2)$$

∴ the result is = -0000₁₀

5) Convert the Hexadecimal numbers (306.E)₁₆ into octal numbers (Base 8).

$$(306.E)_{16} = (001\ 100000110.\ 1110)_2$$

[most (F.E) = 1111] = (1406.70)₈

6) Add 2 decimal no. 182 and 598 using BCD addition method.

$$\begin{array}{r} 182 \\ + 598 \\ \hline 780 \end{array}$$

182 → 0001 1000 0010
598 → 1010 1101 1000 01

$$\begin{array}{r} 0111 0001 1010 \\ + 0001 0110 \\ \hline 0111 0010 0000 \\ \hline (7\ 2) \end{array}$$

$$0.111\ 0010\ 0000$$

$$+ 0110$$

$$\hline 0111\ 10000000$$

$$+ (7\ 8) \quad \text{from left}$$

7. Convert the decimal number (153.513)₁₀ into octal numbers (Base 8).

$$(153.513)_{10}$$

$$\begin{array}{r} 153 \\ 8 \left[\begin{array}{r} 19 \\ -1 \\ \hline 24 \\ \left[\begin{array}{r} 3 \\ -1 \\ \hline 4 \end{array} \right] \end{array} \right] \\ \hline 024\ 3 \end{array}$$

$$(153)_{10} = (231)_8$$

$$.5183 \times 8 = 0.104 \quad \text{Carry}$$

$$0.104 \times 8 = 0.832$$

$$0.832 \times 8 = 0.656$$


$$0.656 \times 8 = 0.248$$

$$0.248 \times 8 = 0.984$$

$$(0.513)_{10} = (40651)_8$$

$$(153.513)_{10} = (231.40651)_8$$

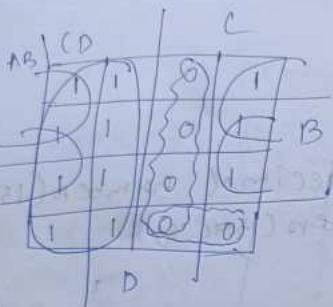- 8) Find the complement of a Boolean function $F(A, B, C, D) = \sum_m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ using K-map method.



Process - I

$$F = C' + A'D' + BD'$$

$$\text{If } 1 = \text{the function is } F = C + \bar{A}D + BD \\ = A\bar{D} + B\bar{D} + C(\bar{A} + D) \\ = A\bar{D} + B\bar{D} + C(A + D)$$


$$\begin{aligned} F &= \bar{C} + \bar{A}D + BD \\ &= C \cdot (A + D) \cdot (\bar{B} + D) \end{aligned}$$

Process - II

$$F = C\bar{D} + \bar{A}C\bar{B}$$

$$\begin{aligned} C(A+D)(\bar{B}+D) &= (AC+CD)(\bar{B}+D) \\ &\Rightarrow A\bar{B}C + ADC + \bar{B}CD + CD \\ &\Rightarrow A\bar{B}C + ADC + \bar{B}CD + A + BCD \\ &\Rightarrow A\bar{B}C + CD(1+A+\bar{B}) \\ &\Rightarrow A\bar{B}C + CD(1+AB) \\ &\Rightarrow A\bar{B}C + CD \end{aligned}$$

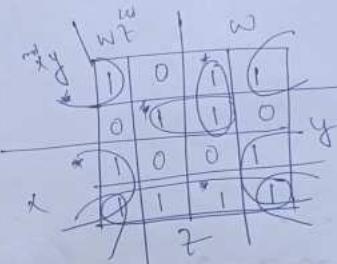- 9) Find the essential prime implicants of the Boolean function $F(w, x, y, z) = \sum_m(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$
- K-map for the function,



$$F = \bar{x}\bar{y} + x\bar{z} + \bar{y}\bar{z} + \bar{x}yz + \bar{x}wz$$


$$\text{P.I. are } = \bar{x}\bar{y}, x\bar{z}, \bar{y}\bar{z}, \bar{x}yz, \bar{x}wz$$

$$\text{E.P.I. } = \bar{y}\bar{z}, x\bar{z}, \bar{x}\bar{y}, \bar{x}yz, \bar{x}wz$$

$$\text{the func for E.P.I. } = \bar{x}\bar{y} + x\bar{z} + \bar{y}\bar{z} + \bar{x}yz + \bar{x}wz - F$$

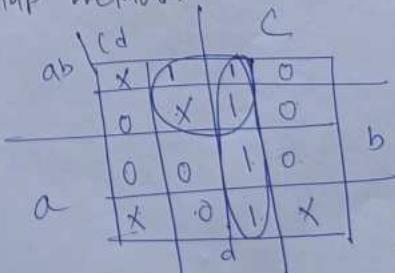10. minimize the Boolean function $F(a, b, c, d)$

$$= \sum_m(1, 3, 7, 11, 15) + \sum_d(0, 5, 8, 10) \text{ using K-map method.}$$



$$F = Cd + \bar{a}d$$

the function is $F = cd + \bar{a}d$
After minimizing the function is $F = d(\bar{a} + c)$